

Overview

◆ Last lecture

- Introduction to finite-state machines
 - ↳ Moore versus Mealy machines
 - ↳ Synchronous Mealy machines
 - ↳ Example: A parity checker

◆ Today

- Example: A sequence detector FSM
- Example: A vending machine FSM
- FSMs in Verilog

FSM design

◆ FSM-design procedure


1. State diagram and state-transition table
2. State minimization
3. State assignment (or state encoding)
4. Minimize next-state logic
5. Implement the design

Example: Sequence detector

◆ Design a circuit to detect 3 or more 1's in a bit string

- Assume Moore machine
- Assume D flip-flops
- Assume flip-flops have a reset

 1. State diagram and state-transition table




reset	current state	input	next state	current output
1	-	-	A	0
0	A	0	A	0
0	A	1	B	0
0	B	0	A	0
0	B	1	C	0
0	C	0	A	0
0	C	1	D	0
0	D	0	A	1
0	D	1	D	1

2. State minimization & 3. State encoding

◆ State diagram is already minimized

◆ Try a binary encoding

 

reset	current state	input	next state	current output
1	-	-	00	0
0	00	0	00	0
0	00	1	01	0
0	01	0	00	0
0	01	1	10	0
0	10	0	00	0
0	10	1	11	0
0	11	0	00	1
0	11	1	11	1

4. Minimize next-state logic

MSB+

In	M			
	0	0	0	0
	0	1	1	1
	L			

$$\text{MSB}^+ = L'n + M'n$$

LSB+

In	M			
	0	0	0	0
	1	0	1	1
	L			

$$\text{LSB}^+ = L'n + M'n$$

OUT+

In	M			
	0	0	1	0
	0	0	1	0
	L			

$$\text{Out}^+ = ML$$


Notation

M := MSB

L := LSB

In := Input

5. Implement the design

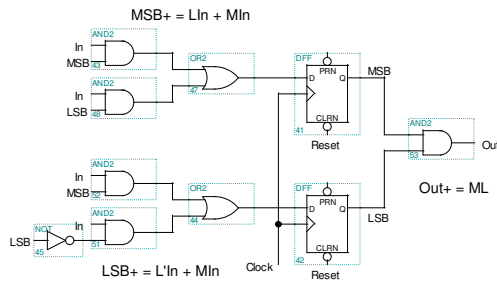


CSE370, Lecture 21

7

Design example: A vending machine

 - ◆ Release item after receiving 15 cents
 - Single coin slot for dimes and nickels
 - ↳ Sensor specifies coin type
 - Machine does not give change




CSE370, Lecture 21

8

1a. State diagram

 - ◆ Consider input sequences
 - 3 nickels
 - 2 nickels, dime
 - nickel, dime
 - dime, nickel
 - two dimes
- ◆ Draw state diagram
 - Assume Moore machine
 - Inputs: N, D, reset
 - Output: Open



CSE370, Lecture 21

9

1b. Symbolic state-transition table


present state	inputs		next state	present output
	D	N		
0¢	0	0	0¢	0
	0	1	5¢	0
	1	0	10¢	0
	1	1	—	—
5¢	0	0	5¢	0
	0	1	10¢	0
	1	0	15¢	0
	1	1	—	—
10¢	0	0	10¢	0
	0	1	15¢	0
	1	0	15¢	0
	1	1	—	—
15¢	—	—	15¢	1

CSE370, Lecture 21

10

 2. State minimization

- ◆ Reuse states where possible
 - Notice we can use the deposited coin values for states
 - State is the same if we input 2 nickels or 1 dime



CSE370, Lecture 21

11

3. State encoding

- ◆ Encode states uniquely
 - 4 states:
 - ↳ 2 bits minimum
 - ↳ 4 bits maximum
 - Look for optimal encoding
 - Assume D flip-flops

present state	inputs		next state	present output
Q0 Q1	D	N	P1 P0	output
0 0	0	0	0 0	0
	0	1	0 1	0
	1	0	1 0	0
	1	1	—	—
0 1	0	0	0 1	0
	0	1	1 0	0
	1	0	1 1	0
	1	1	—	—
1 0	0	0	1 0	0
	0	1	1 1	0
	1	0	1 1	0
	1	1	—	—
1 1	—	—	1 1	1

CSE370, Lecture 21

12

Verilog FSM - Reduce 1s example

◆ Moore machine


```

`define zero 0
`define one1 1 ← state assignment
`define twos 2

module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
reg [2:1] state; // state variables
reg [2:1] next_state;

always @(posedge clk)
  if (reset) state = `zero;
  else state = next_state;

```

 

CSE370, Lecture 21

19

Moore Verilog FSM (cont'd)

```

always @(in or state) ← crucial to include
  case (state)
  `zero:
  // last input was a zero
  begin
    if (in) next_state = `one1;
    else next_state = `zero;
  end
  `one1:
  // we've seen one 1
  begin
    if (in) next_state = `twos;
    else next_state = `zero;
  end
  `twos:
  // we've seen at least 2 ones
  begin
    if (in) next_state = `twos;
    else next_state = `zero;
  end
endcase

always @(state)
  case (state)
  `zero: out = 0;
  `one1: out = 0;
  `twos: out = 1;
  endcase
endmodule

```

note that output depends only on state

CSE370, Lecture 21

20

Mealy Verilog FSM


```

module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
reg state; // state variables
reg next_state;

always @(posedge clk)
  if (reset) state = `zero;
  else state = next_state;

always @(in or state)
  case (state)
  `zero: // last input was a zero
  begin
    out = 0;
    if (in) next_state = `one;
    else next_state = `zero;
  end
  `one: // we've seen one 1
  if (in) begin
    next_state = `one; out = 1;
  end else begin
    next_state = `zero; out = 0;
  end
  endcase
endmodule

```

 

CSE370, Lecture 21

21

Synchronous Mealy Machine

```

module reduce (clk, reset, in, out);
input clk, reset, in;
output out;
reg out;
reg state; // state variables

always @(posedge clk)
  if (reset) state = `zero;
  else
  case (state) // last input was a zero
  begin
    out = 0;
    if (in) state = `one;
    else state = `zero;
  end
  `one: // we've seen one 1
  if (in) begin
    state = `one; out = 1;
  end else begin
    state = `zero; out = 0;
  end
  endcase
endmodule

```

CSE370, Lecture 21

22