 


Advanced Digital Design with the Verilog HDL



M. D. Ciletti

**Department
of
Electrical and Computer Engineering
University of Colorado
Colorado Springs, Colorado**

ciletti@vlsic.uccs.edu

Draft: Chap 6c: Synthesis of Combinational and Sequential Logic (Rev 9/17/2003)

Copyright 2000, 2002, 2003. These notes are solely for classroom use by the instructor. No part of these notes may be copied, reproduced, or distributed to a third party, including students, in any form without the written permission of the author.

Note to the instructor: These slides are provided solely for classroom use in academic institutions by the instructor using the text, *Advance Digital Design with the Verilog HDL* by Michael Ciletti, published by Prentice Hall. This material may not be used in off-campus instruction, resold, reproduced or generally distributed in the original or modified format for any purpose without the permission of the Author. This material may not be placed on any server or network, and is protected under all copyright laws, as they currently exist. I am providing these slides to you subject to your agreeing that you will not provide them to your students in hardcopy or electronic format or use them for off-campus instruction of any kind. Please email to me your agreement to these conditions.

I will greatly appreciate your assisting me by calling to my attention any errors or any other revisions that would enhance the utility of these slides for classroom use.



Synthesis of Implicit State Machines, Registers and Counters

- Implicit state machines are described by one or more edge-sensitive event-control expressions in the same behavior
- Clock edges define the boundaries of the states
- Machine remains in a fixed state between clock edges
- All transitions must be synchronized to the same edge of the clock
- Do not declare a state register – it is implicit
- Limitation: Each state of an implicit state machine may be entered from only one other state

Example: Implicit State Machines

- Synthesis tools infer the existence of an implicit FSM when a cyclic (***always***) behavior has more than one embedded, clock-synchronized, event control expression
- The multiple event control expressions within an implicit finite state machine separate the activity of the behavior into distinct clock cycles of the machine

```

always @ (posedge clk) // Synch event before first assignment
begin
    reg_a <= reg_b;           // Executes in first clock cycle
    reg_c <= reg_d;           // Executes in first clock cycle.
@ (posedge clk)           // Begins second clock cycle.
begin
    reg_g <= reg_f;           // Executes in second clock cycle.
    reg_m <= reg_r;           // Executes in second clock cycle.
end
end

```

Synthesis of Implicit State Machines

- Synthesis tool infers the size of the state
- Registers are allocated to hold "multiple wait states"
- Synthesis tool infers the logic governing state transitions

Example: Ripple Counter

```
module ripple_counter (count, toggle, clock, reset,);  
  output      [3: 0]    count;  
  input       toggle, clock, reset;  
  reg         [3: 0]    count;  
  wire        c0, c1, c2;  
  
  assign c0 = count[0];  
  assign c1 = count[1];  
  assign c2 = count[2];  
  
  always @ (posedge reset or posedge clock)  
    if (reset == 1'b1) count[0] <= 1'b0; else  
      if (toggle == 1'b1) count[0] <= ~count[0];  
  
  always @ (posedge reset or negedge c0)  
    if (reset == 1'b1) count[1] <= 1'b0; else  
      if (toggle == 1'b1) count[1] <= ~count[1];
```

```


always @ (posedge reset or negedge c1)
  if (reset == 1'b1) count[2] <= 1'b0; else
    if (toggle == 1'b1) count[2] <= ~count[2];

```


```

always @ (posedge reset or negedge c2)
  if (reset == 1'b1) count[3] <= 1'b0; else
    if (toggle == 1'b1) count[3] <= ~count[3];
endmodule

```

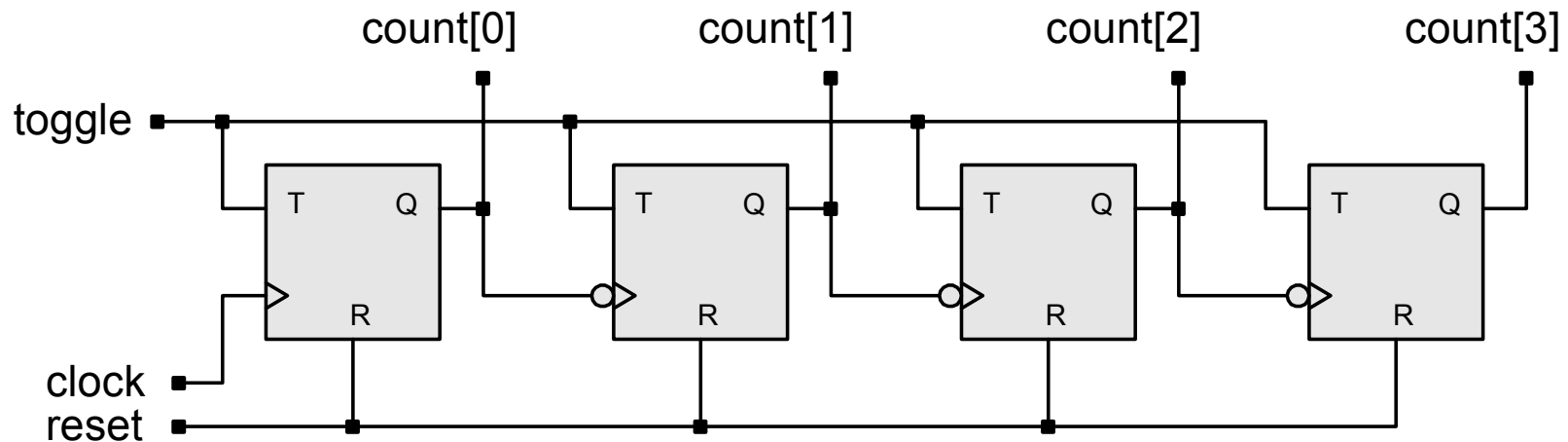


Synthesized circuit:

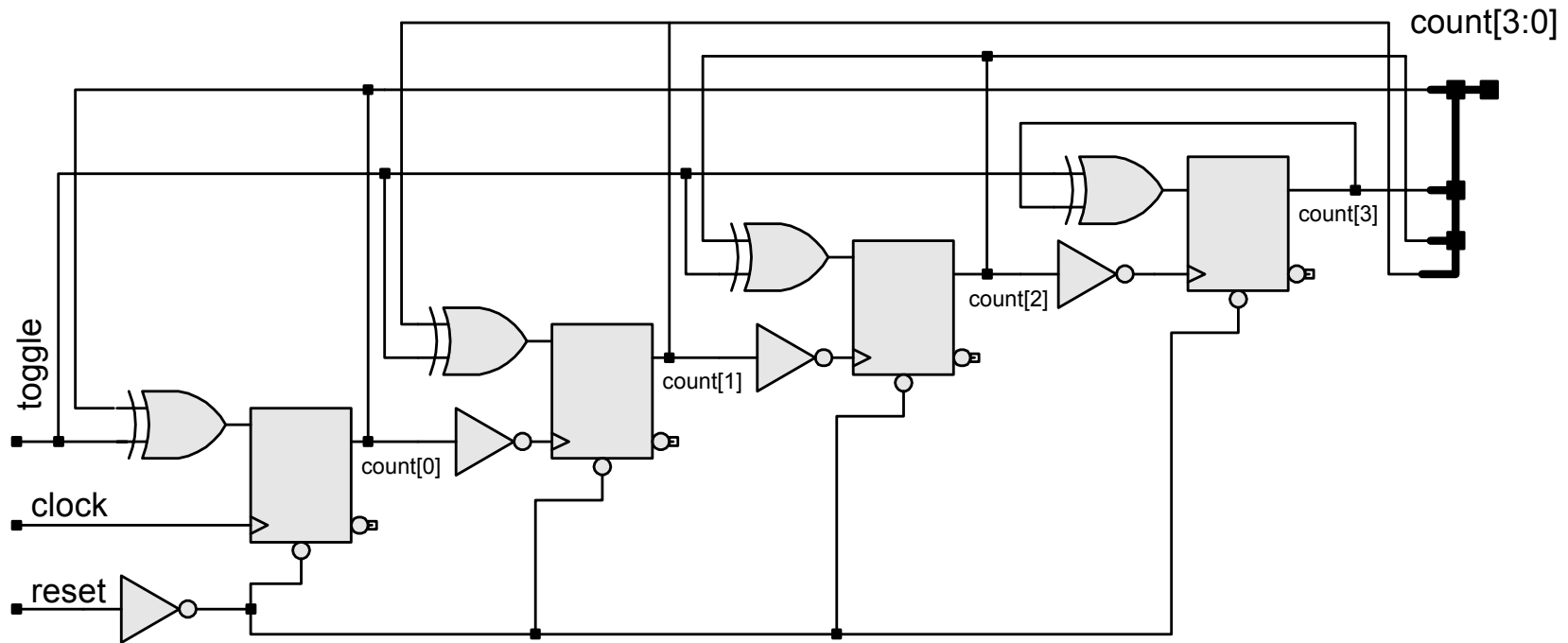


Example: Ring Counter



- A sequential machine having an identical activity flow in every cycle is a one-cycle implicit state machine
- One state: "running"

Revisit Example 5.40

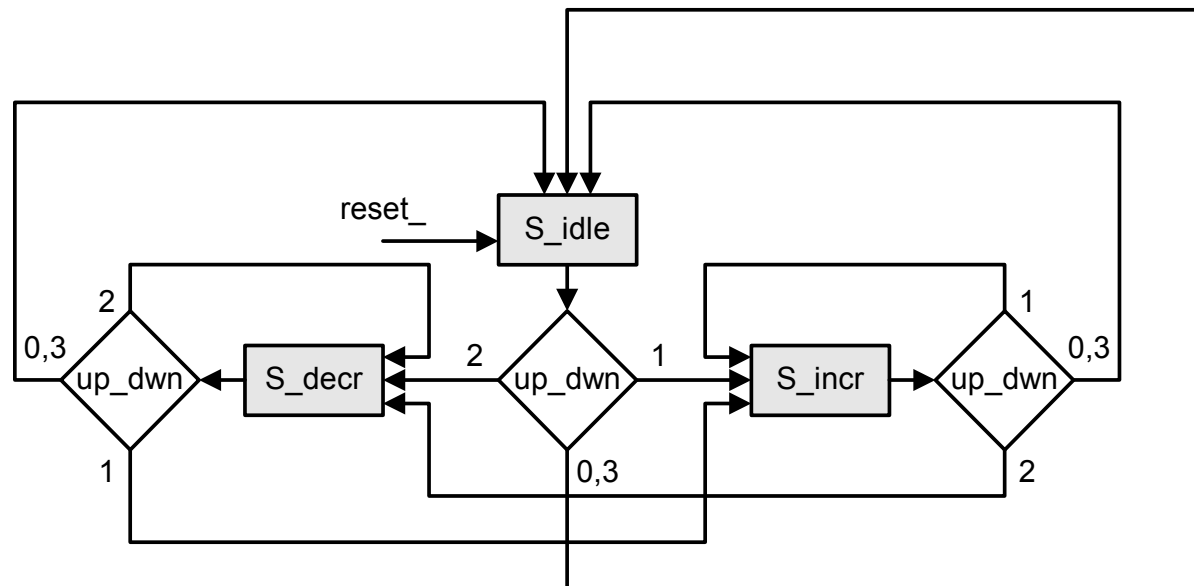

 


2
0,3
up.
1

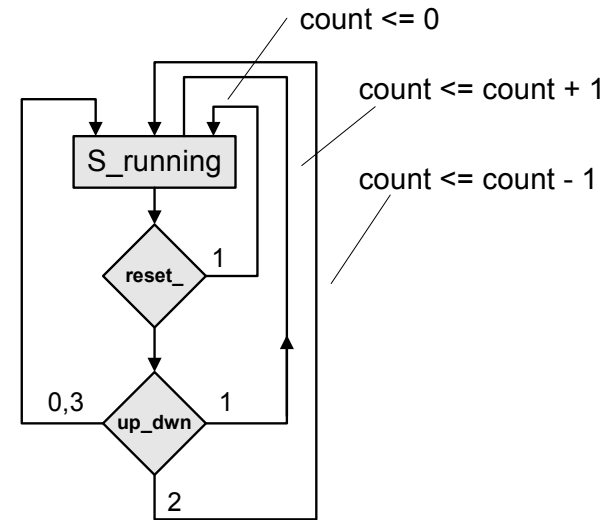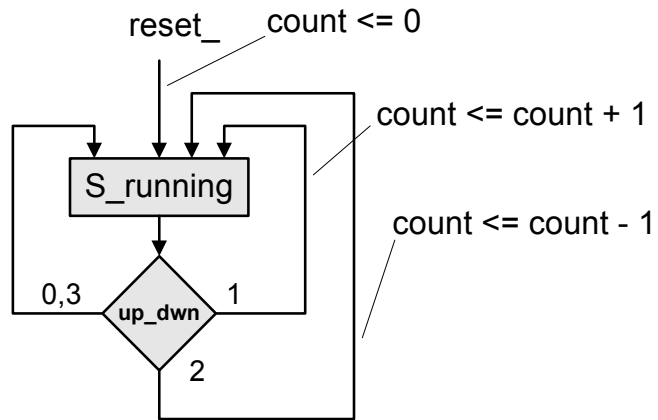

Note: modeling the machine with a single implicit state is simpler than modeling a machine whose state is the count.

We'll see later that this problem can be partitioned into a datapath and a controller.

```
module Up_Down_Implicit1 (count, up_dwn, clock, reset_);  
  
  output [2: 0]    count;  
  input   [1: 0]    up_dwn;  
  input          clock, reset_;  
  
  reg [2: 0] count;  
  
  always @ (negedge clock or negedge reset_)  
    if (reset_ == 0) count <= 3'b0; else  
      if (up_dwn == 2'b00 || up_dwn == 2'b11) count <= count; else  
        if (up_dwn == 2'b01) count <= count + 1; else  
          if (up_dwn == 2'b10) count <= count - 1;  
  
endmodule
```

 

Synthesis of Registers


Register: Array of D-type flip-flops with a common clock

Example 6.31

```
module shifter_1 (sig_d, new_signal, Data_in, clock, reset);  
  output      sig_d, new_signal;  
  input       Data_in, clock, reset;  
  
  reg         sig_a, sig_b, sig_c, sig_d, new_signal;
```

```
always @ (posedge reset or posedge clock)  
begin if (reset == 1'b1)  
  begin  
    sig_a <= 0;  
    sig_b <= 0;  
    sig_c <= 0;  
    sig_d <= 0;  
    new_signal <= 0;  
  end  
else  
  begin  
    sig_a <= Data_in;  
    sig_b <= sig_a;  
    sig_c <= sig_b;  
    sig_d <= sig_c;  
    new_signal <= (~ sig_a) & sig_b;  
  end  
end  
endmodule
```

Note: *new_signal* receives value within a synchronous behavior and appears as an output port. It will be synthesized as the output of a flip-flop.

 


Example 6.32

- *new_signal* is formed outside of the behavior in a continuous assignment
- *new_signal* appears as an output port
- *new_signal* is synthesized as the output of combinational logic.

```
module shifter_2 (sig_d, new_signal, Data_in, clock, reset);  
  output      sig_d, new_signal;  
  input       Data_in, clock, reset;  
  
  reg         sig_a, sig_b, sig_c, sig_d, new_signal;
```



```
always @ (posedge reset or posedge clock)  
begin  
  if (reset == 1'b1)  
    begin  
      sig_a <= 0;  
      sig_b <= 0;  
      sig_c <= 0;  
      sig_d <= 0;  
    end  
  else  
    begin  
      sig_a <= shift_input;  
      sig_b <= sig_a;  
      sig_c <= sig_b;  
      sig_d <= sig_c;  
    end  
  end  
  assign new_signal = (~ sig_a) & sig_b;  
endmodule
```

 

Example 6.33 Two versions of an accumulator forming the running sum of two samples of an input.

```
module Add_Accum_1 (accum, overflow, data, enable, clk, reset_b);  
  output [3: 0]    accum;  
  output          overflow;  
  input [3: 0]    data;  
  input          enable, clk, reset_b;  
  reg           accum, overflow;  
  
  always @ (posedge clk or negedge reset_b)  
    if (reset_b == 0) begin accum <= 0; overflow <= 0; end  
    else if (enable) {overflow, accum} <= accum + data;  
endmodule
```


```
module Add_Accum_2 (accum, overflow, data, enable, clk, reset_b);  
    output [3: 0]    accum;  
    output         overflow;  
    input [3: 0]    data;  
    input         enable, clk, reset_b;  
    reg          accum;  
    wire [3:0]    sum;  
    assign      {overflow, sum} = accum + data;  
  
    always @ (posedge clk or negedge reset_b)  
        if (reset_b == 0) accum <= 0;  
        else if (enable) accum <= sum;  
endmodule
```


Simulation Results:

- *Add_Accum_1* forms *overflow_1* one cycle after storing the results of an overflow condition
- *Add_Accum_2* forms *overflow_2* as an unregistered Mealy output

Synthesis Results:

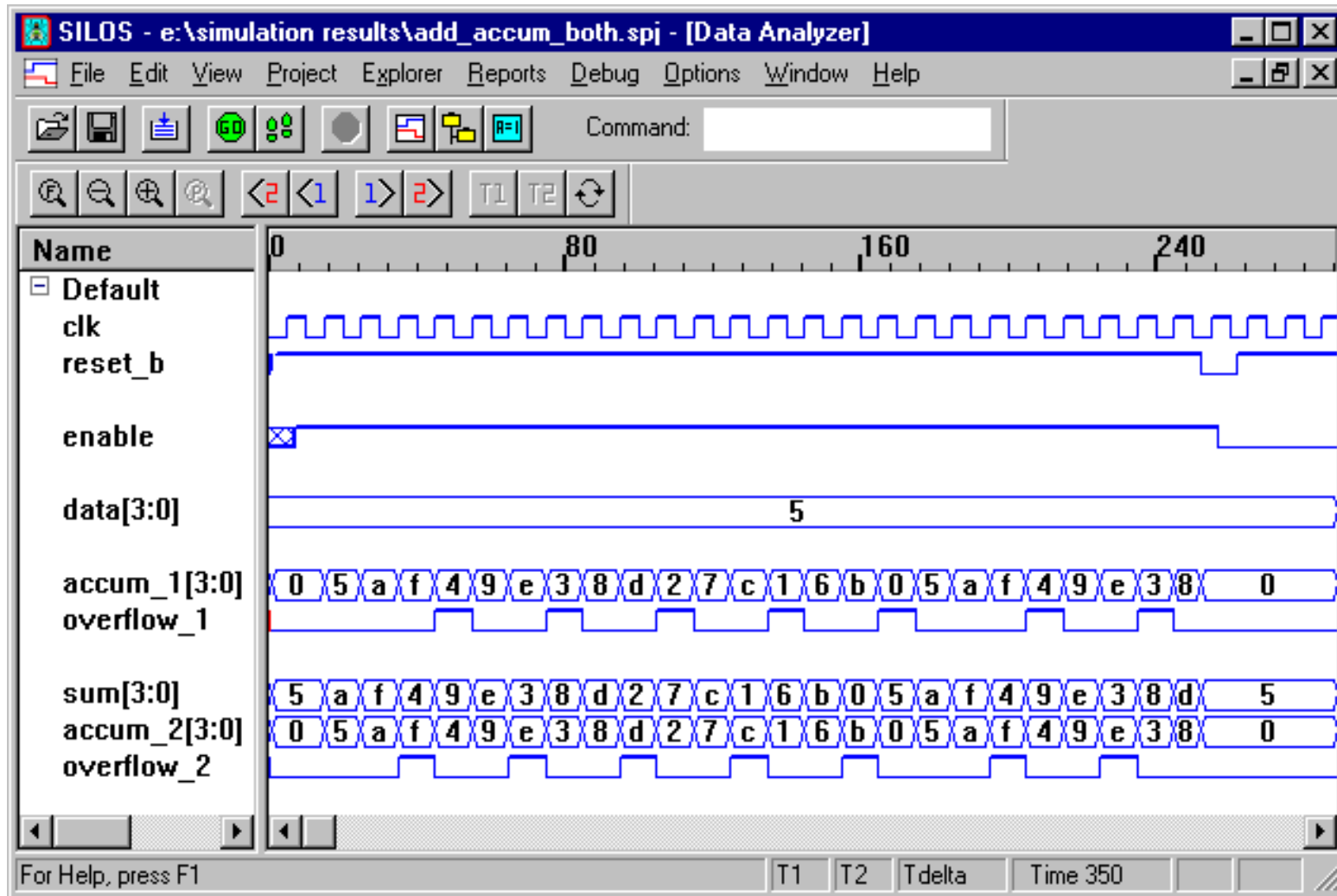- *overflow_1* is formed in *Add_Accum_1* as a registered version of *overflow_2*, which is formed in *Add_Accum_2*.



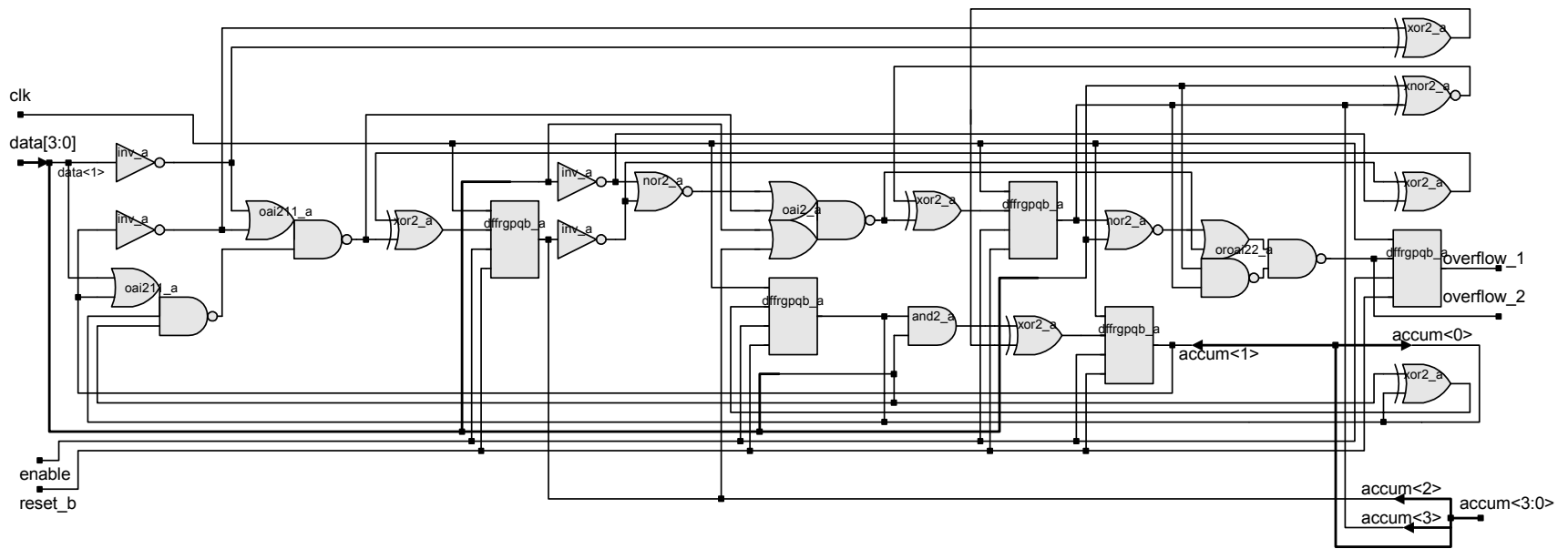

Resets

- Provide a reset signal to every sequential module that is to be synthesized
 - Initialize the state
 - Support testing
- Provide an external signal to reset an implicit state machine
- Provide reset logic to every cycle of the behavioral model
 - Return to the top of the multi-cycle behavior from any cycle
 - Return to the same state independently of when reset is asserted
 - Synthesis will produce extra logic to accommodate incomplete resets
- May have to synchronize the reset signal


Partial Resets

- Implicit state machine to asserts D_out after two successive samples of D_in are both either 1 or 0
- Hold samples in a two-stage shift register
- Prevent premature assertion by having a state machine set *flag* after two samples have been received
- Examine consequences of partially resetting the data register

```
module Seq_Rec_Moore_imp (D_out, D_in, clock, reset);  
  output      D_out;  
  input       D_in;  
  input       clock, reset;  
  reg         last_bit, this_bit, flag;  
  wire       D_out;  
  always begin: wrapper_for_synthesis  
    @ (posedge clock /* or posedge reset*/)  
    begin: machine  
      if (reset == 1) begin  
        last_bit <= 0;  
        // this_bit <= 0;  
        // flag <= 0;  
        disable machine; end  
      else begin  
        // last_bit <= this_bit;  
        this_bit <= D_in;
```


```
forever  
  @ (posedge clock /* or posedge reset */) begin  
    if (reset == 1) begin  
      // last_bit <= 0;  
      // this_bit <= 0;  
      flag <= 0;  
      disable machine; end  
    else begin  
      last_bit <= this_bit;  
      this_bit <= D_in;  
      flag <= 1; end          // second edge  
    end  
  end  
end // machine  
end // wrapper_for_synthesis  
  
  assign D_out = (flag && (this_bit == last_bit));  
endmodule
```

Simulation Results:

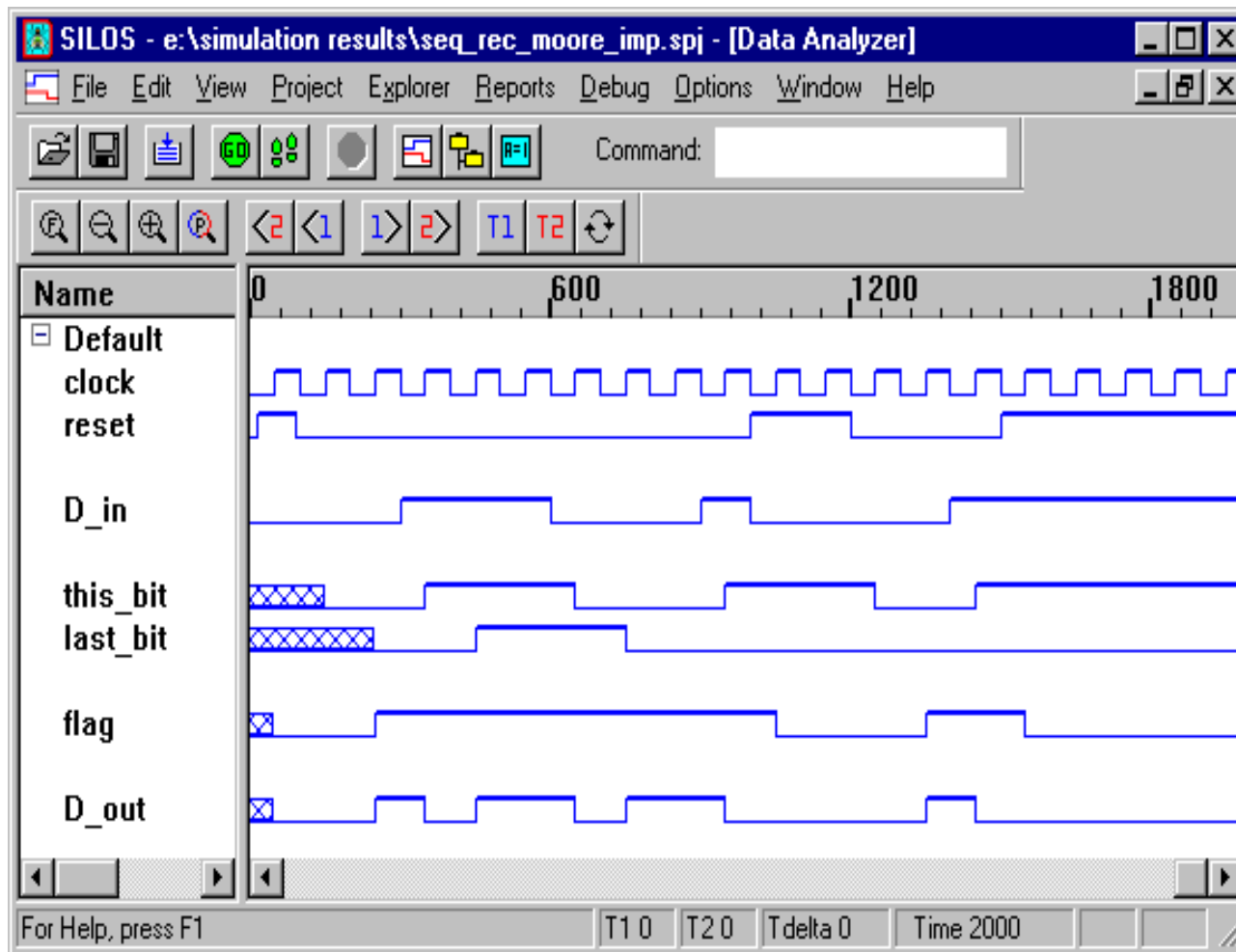

Note: synthesis depends on how the reset is implemented

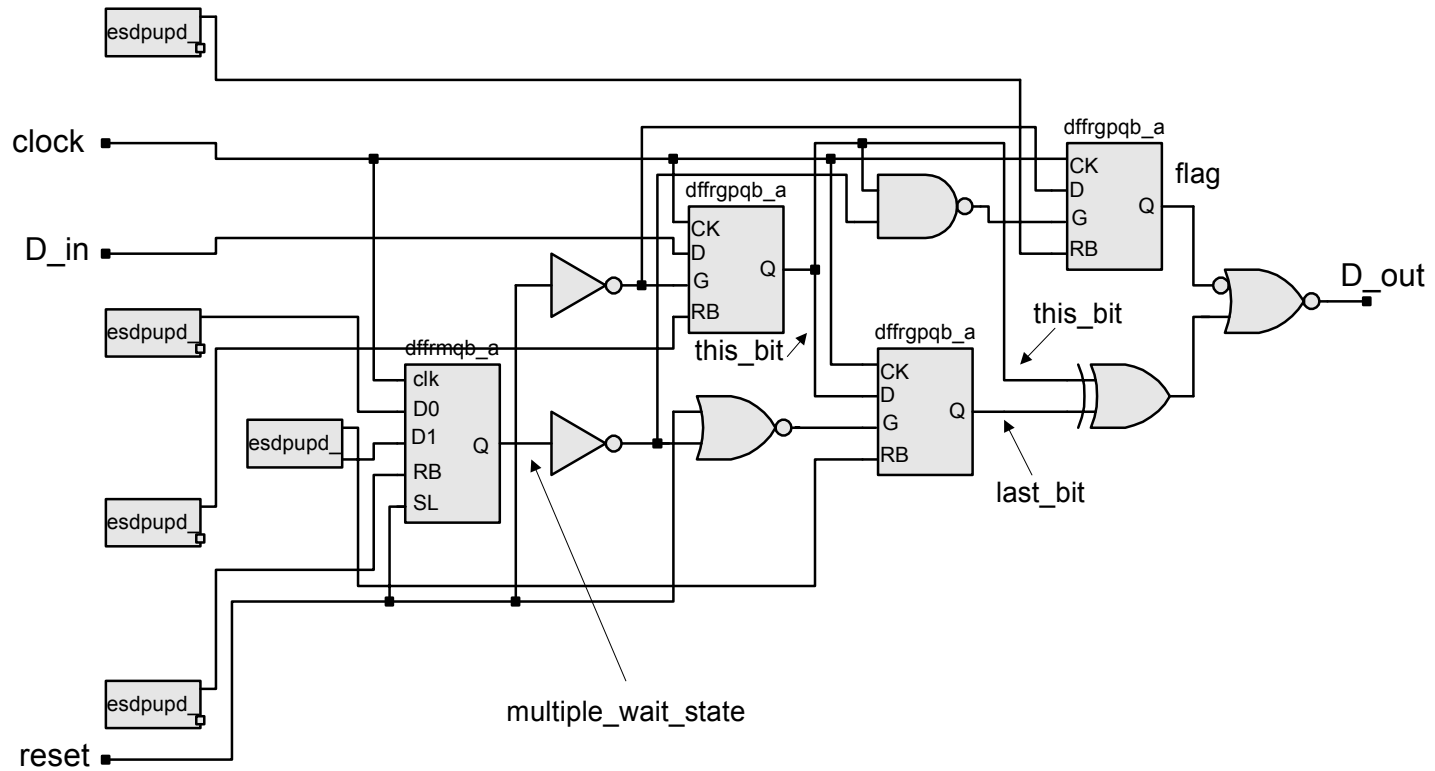
Case 1: Flush only last_bit (earliest bit received)



Features to note:

- dffrgpqb_a is a gate-input flip-flop with an internal datapath from Q to D
 - Q is connected to D when G is low
 - Q is connected to external datapath (D) when Q is high
- dffmpqb_a is a dual multiplexed input flip-flop
 - Holds `multiple_wait_state` indicating two samples received
 - RB (reset) input is disabled by `espupd`
 - SL (set) is active low and wire to reset
 - $D0$ and $D1$ are wired to power and ground respectively
 - SL low selects $D0$; SL high selects $D1$
- Assertion of reset:
 - Causes *this_bit* and *last_bit* to hold their values
 - Steers the external input (0) to the *flag* register
- De-assertion of reset:
 - `multiple_wait_state` is 1 after first clock
 - Steers *this_bit* to *last_bit*
 - this_bit* gets *in_bit* after reset is de-asserted
- Only *flag* is flushed in the loop

Case 2: Flush the pipeline

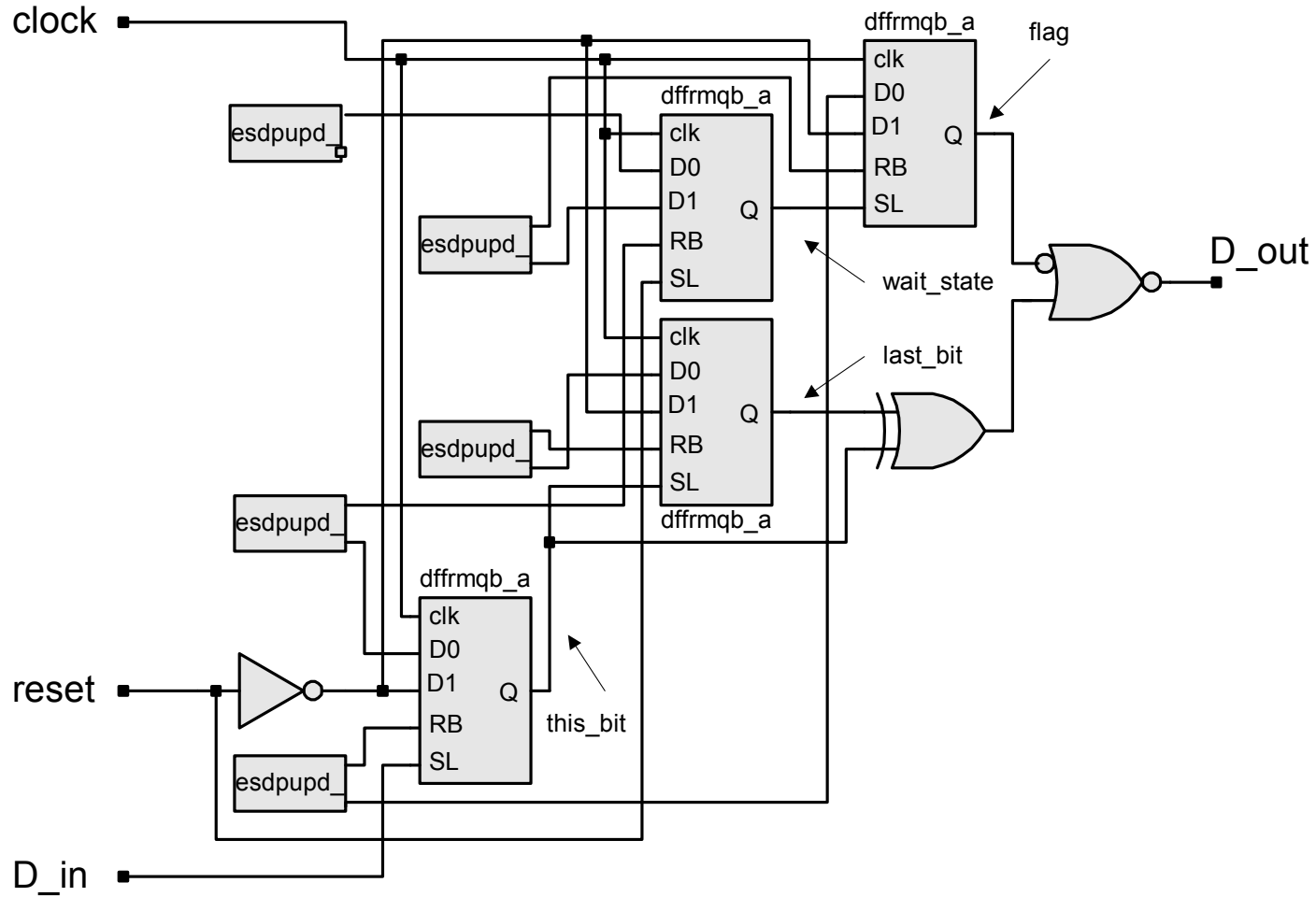

When registers are not flushed on reset, additional logic is required to feed their outputs back to their inputs to retain their state under the action of the clock.

Option: for simpler hardware, drive the register to a known value on reset.



Synthesis of Gated Clocks and Clock Enables


Caution: Gated clocks can add skew to the clock path, and cause the clock signal to violate a flip-flop's constraint on the minimum width of the clock pulse.

Recommended style:

```
module best_gated_clock (clock, reset_, data_gate, data, Q);  
  input      clock, reset_, data, data_gate;  
  output     Q;  
  reg        Q;  
  
  always @ (posedge clock or negedge reset_)  
    if (reset_ == 0) Q <= 0; else if (data_gate) Q <= data;  
endmodule
```


Features:

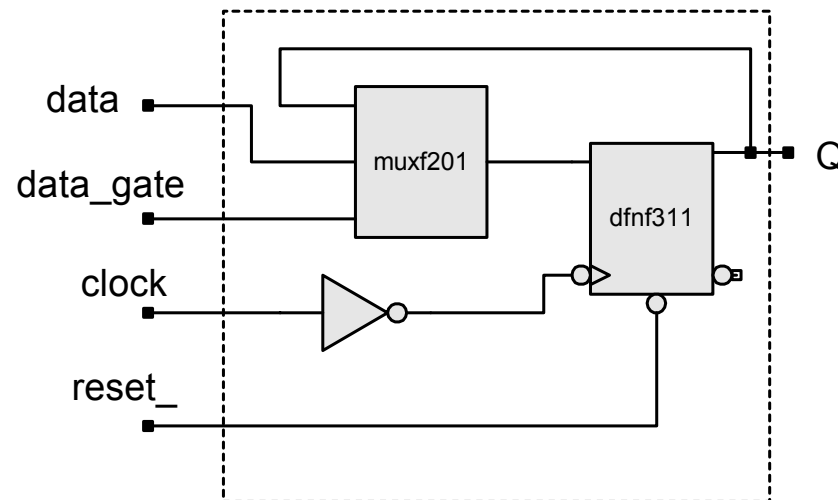- Input data and flip-flop output are multiplexed at D input
- Clock synchronizes the circuit
- *data_gate* gates the action of the clock
- Clock slivers are not a problem



Typical model for clock enable logic:

```
always @ (posedge clk)  
if (enable == 1) q_out <= Data_in;
```



Anticipating the Results of Synthesis

- Data types
- Operator grouping
- Expression Substitution
- Loops

Additional details in "Modeling, Synthesis, and Rapid Prototyping with the Verilog HDL"

Synthesis of Data Types

- The identity of nets that are primary inputs or outputs are retained in synthesis
- Internal nets may be eliminated by synthesis
- Integers are stored as 32-bit words (minimum per IEEE 1364)
- Used sized parameters rather than integer parameters
- Explicit use of x or z in logical tests will not synthesize

Synthesis of Operators

Some operators may map directly into library cells (e.g. +, 1, <, >, =)
Synthesis might impose restrictions on an operator

- Shift operators is allowed only if the shift index is a constant
- Reduction, bitwise, and logical operators synthesize to equivalent gates
- Conditional operator synthesizes to a mux structure
- If both operands of * are constant the tool produces the constant result
- If one operand of * is a power of 2 the synthesis tool forms the result by left-shifting the other operand
- If one operand of / is a power of 2 the result will be formed by right-shifting the other operand
- If the divisor is a power of 2 the % operator will be formed as a part-select

See "Modeling, Synthesis and Rapid Prototyping with the Verilog HDL for more details


Operator Grouping

Use parentheses within expressions to influence the outcome of synthesis

Example 6.35

```
module operator_group (sum1, sum2, a, b, c, d);  
  output [4: 0]    sum1, sum2;  
  input  [3: 0]    a, b, c, d;  
  
  assign sum1 = a + b + c + d;      // 3 levels of logic  
  assign sum2 = (a + b) + (c + d); // 2 levels of logic  
  
endmodule
```


Synthesis results:

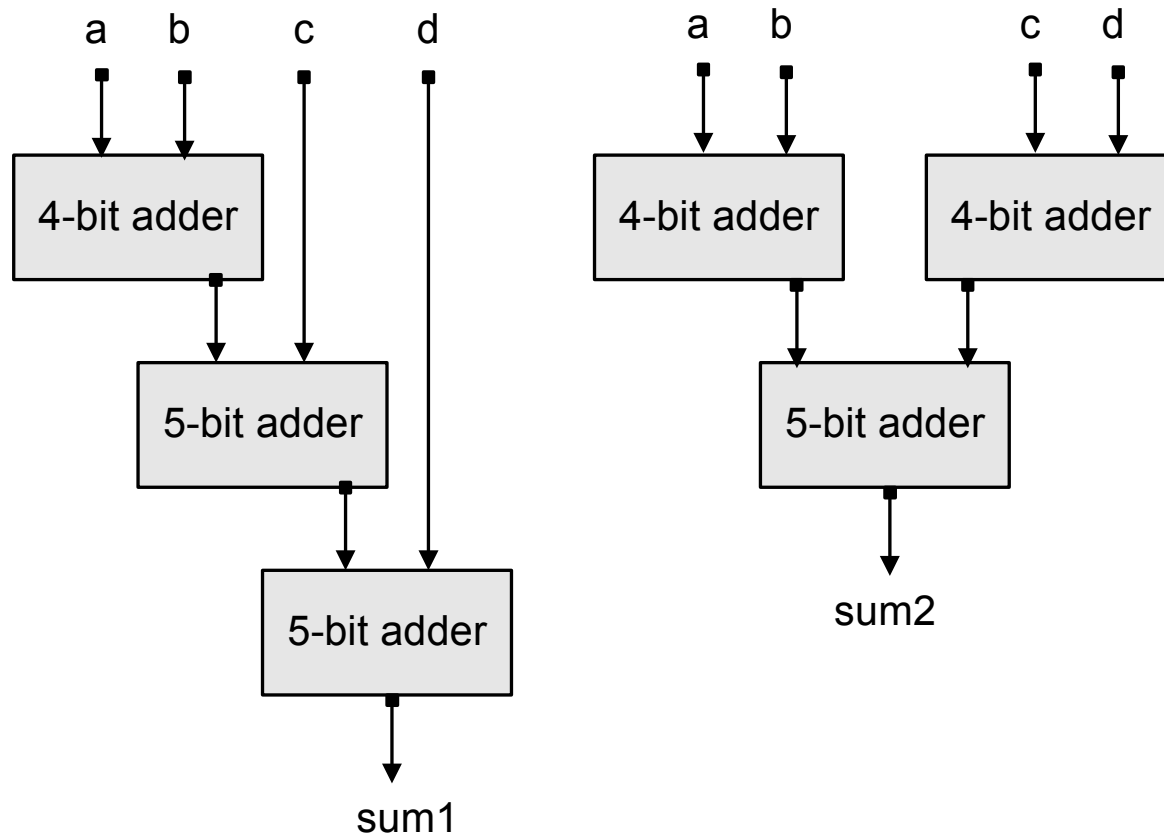

Note: Use sum1 with input d to accommodate a late signal

Expression Substitution

- Synthesis tools perform expression substitution to determine the effective logic of a sequence of procedural assignments
- Remember: procedural assignments have immediate effect on the value of the target variable

Example 6.36

```
module multiple_reg_assign
  (data_out1, data_out2, data_a, data_b, data_c, data_d, sel, clk);

  output      [4: 0]    data_out1, data_out2;
  input       [3: 0]    data_a, data_b, data_c, data_d;
  input              clk;

  reg         [4: 0]    data_out1, data_out2;

  always @ (posedge clk)
  begin
    data_out1 = data_a + data_b ;
    data_out2 = data_out1 + data_c;
    if (sel == 1'b0)
      data_out1 = data_out2 + data_d;
  end
endmodule
```

More readable alternative:

```
module expression_sub
  (data_out1, data_out2, data_a, data_b, data_c, data_d, sel, clk);

  output    [4: 0]    data_out1, data_out2;
  input     [3: 0]    data_a, data_b, data_c, data_d;
  input          sel, clk;
  reg       [4: 0]    data_out1, data_out2;


  always @ (posedge clk)
  begin
    data_out2 = data_a + data_b + data_c;
    if (sel == 1'b0)
      data_out1 = data_a + data_b + data_c + data_d;
    else
      data_out1 = data_a + data_b;
  end
endmodule
```


Equivalent logic with nonblocking assignments

```
module expression_sub_nb
  (data_out1nb, data_out2nb, data_a, data_b, data_c, data_d, sel, clk);

  output      [4: 0]    data_out1nb, data_out2nb;
  input       [3: 0]    data_a, data_b, data_c, data_d;
  input              sel, clk;
  reg         [4: 0]    data_out1nb, data_out2nb;

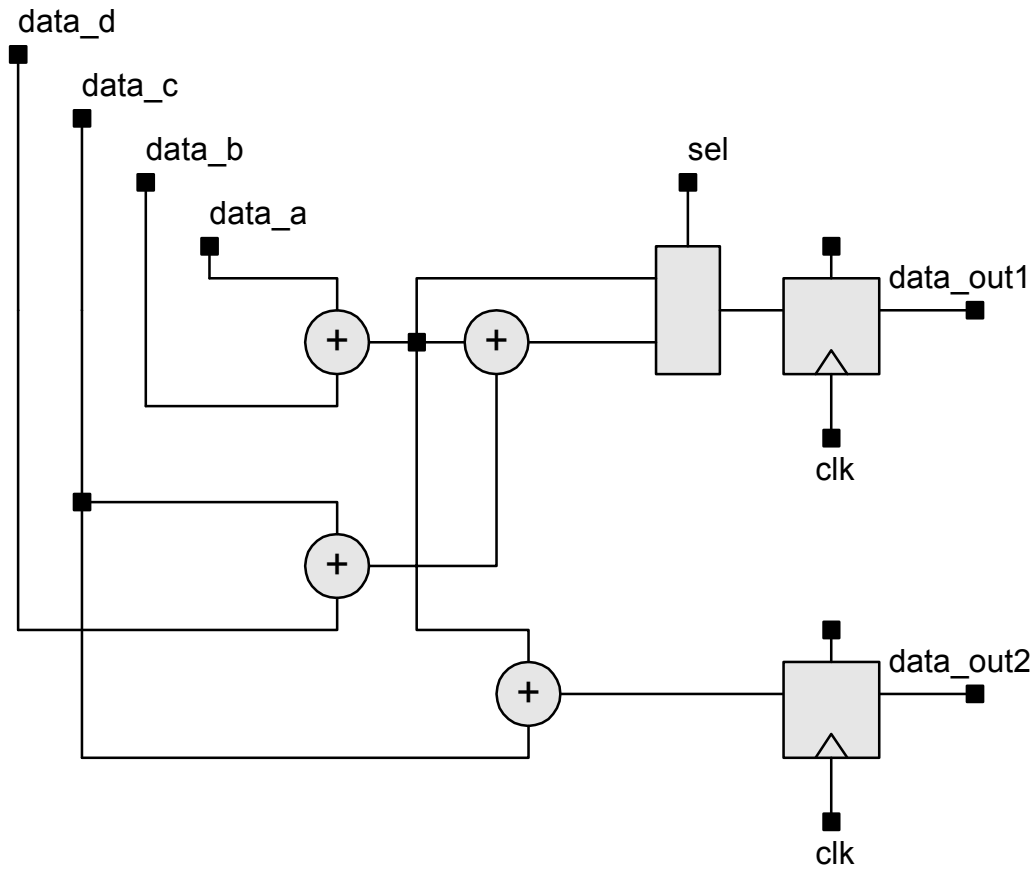  always @ (posedge clk)
  begin
    data_out2nb <= data_a + data_b + data_c;
    if (sel == 1'b0)
      data_out1nb <= data_a + data_b + data_c + data_d;
    else
      data_out1nb <= data_a + data_b;
    end
  endmodule
```



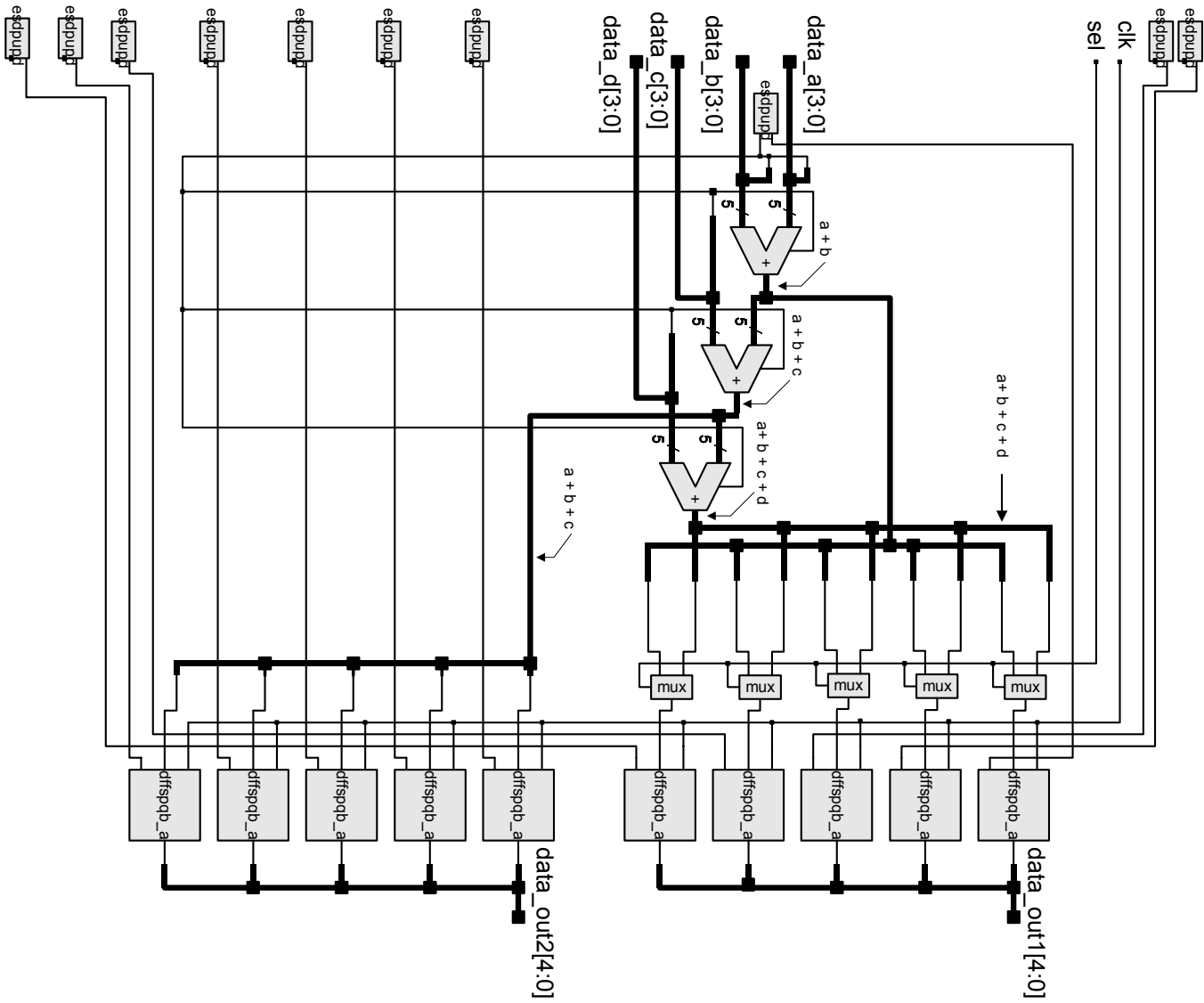



Synthesis of Loops

Classifications of loops according to data dependency and timing controls

Static (data-independent) loop: the number of its iterations can be determined by the compiler *before* simulation

Non-static (data-dependent) loop: the number of iterations depends on some variable during operation.

 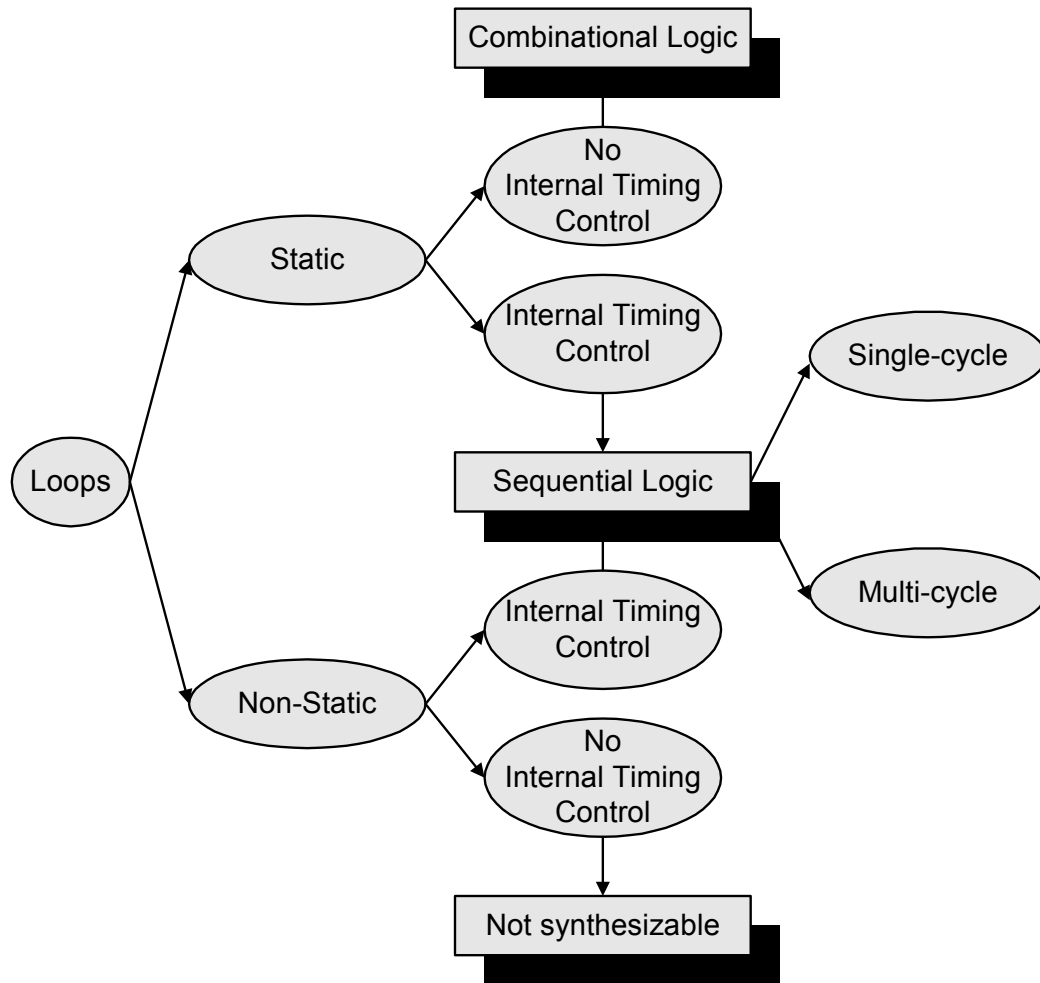Note: Non-static loops that do not have internal timing controls cannot be synthesized directly.



Static Loops – No Internal Timing Control

If a loop has no internal timing controls and no data dependencies, its computational activity is implicitly combinational.

Example 6.37

```
module for_and_loop_comb (out, a, b);  
  output    [3: 0]  out;  
  input     [3: 0]  a, b;  
  
  reg       [2: 0]  i;  
  reg       [3: 0]  out;  
  wire      [3: 0]  a, b;  
  
  always @ (a or b)  
  begin  
    for (i = 0; i <= 3; i = i+1)  
      out[i] = a[i] & b[i];  
  end  
endmodule
```


Equivalent unrolled loop:

$out[0] = a[0] \& b[0];$

$out[1] = a[1] \& b[1];$

$out[2] = a[2] \& b[2];$

$out[3] = a[3] \& b[3];$

 

There are no dependencies in the datapath, and the order in which the statements are evaluated does not affect the outcome of the evaluation.

Example 6.38 Count the 1s in a word received in parallel format


```
module count_ones_a (bit_count, data, clk, reset);  
parameter          data_width = 4;  
parameter          count_width = 3;  
output    [count_width-1: 0]    bit_count;  
input     [data_width-1: 0]     data;  
input     clk, reset;  
reg       [count_width-1: 0]     count, bit_count, index;  
reg       [data_width-1: 0]     temp;
```

```
always @ (posedge clk)  
  if (reset) begin count = 0; bit_count = 0; end  
  else begin  
    count = 0;  
    bit_count = 0;  
    temp = data;  
    for (index = 0; index < data_width; index = index + 1) begin  
      count = count + temp[0];  
      temp = temp >> 1;  
    end  
    bit_count = count;  
  end  
endmodule
```

Note:


- The loop in the Verilog model *count_ones_a* below has no internal timing controls and is static
- The order in which the statements in the cyclic behavior execute is important
- The model uses the blocked assignment operator (=)
- *bit_count* asserts after the loop has executed, within the same clock cycle that the loop executes

Simulation results:

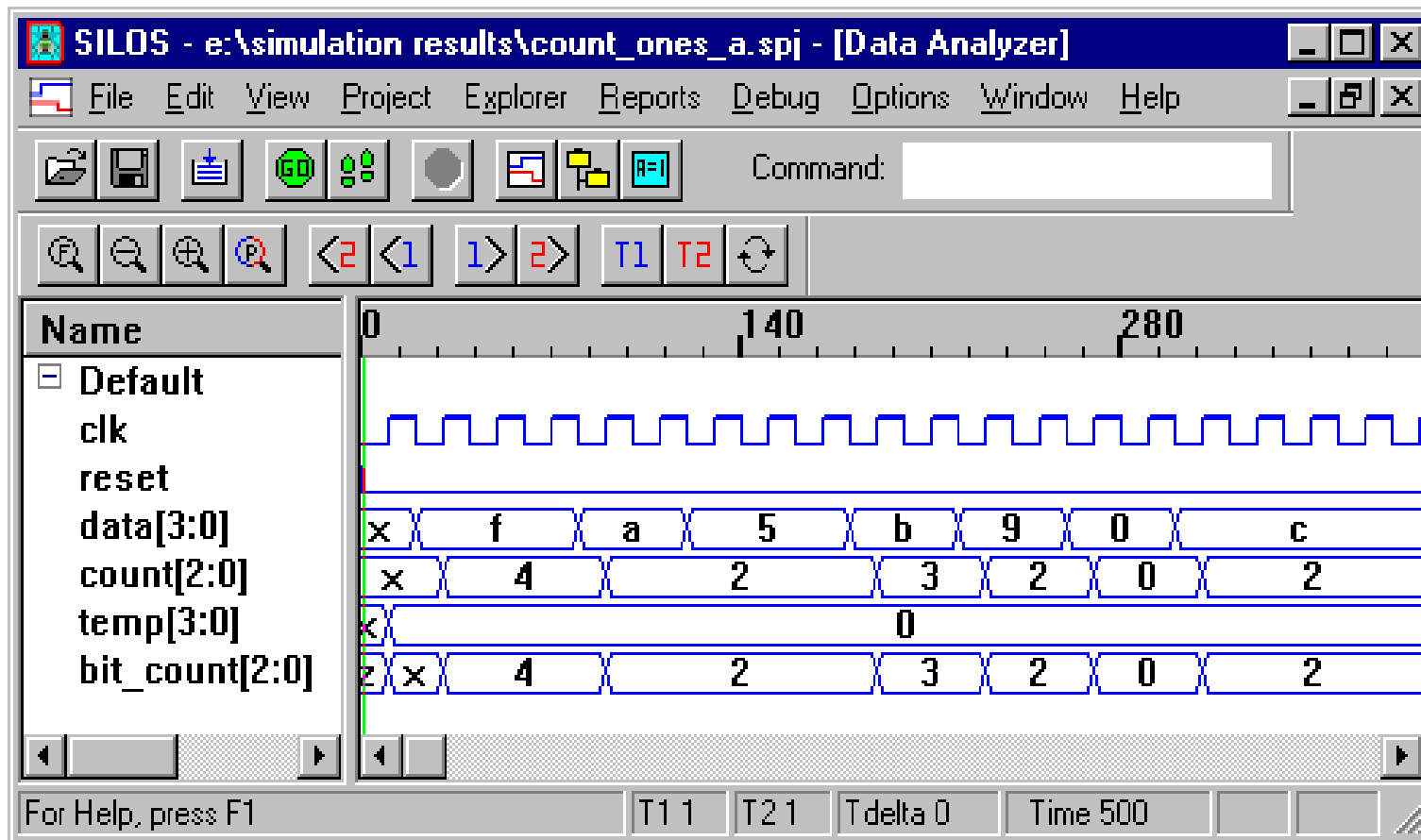

Note: the displayed values of *temp*, *count* and *bit_count* are final values that result after any intermediate values have been overwritten.

Synthesis results:

 

Static Loops with Embedded Timing Control

Embedded event control expressions synchronize and distribute the computational activity of a loop over one or more cycles of the clock (implicit state machine with a cycle for each iteration)

Example 6.39

```

module count_ones_b0 (bit_count, data, clk, reset);
  parameter                data_width = 4;
  parameter                count_width = 3;
  output    [count_width-1: 0] bit_count;
  input    [data_width-1: 0] data;
  input    clk, reset;
  reg    [count_width-1: 0] count, bit_count;
  reg    [data_width-1: 0] temp;
  integer index;

```

```
always begin: wrapper_for_synthesis
  @ (posedge clk) begin: machine
    if (reset) begin bit_count = 0; disable machine; end
    else
      count = 0; bit_count = 0; index = 0; temp = data;
      forever @ (posedge clk)
        if (reset) begin bit_count = 0; disable machine; end
        else if (index < data_width-1) begin
          count = count + temp[0];
          temp = temp >> 1;
          index = index + 1;
          end
          else begin
            bit_count = count + temp[0];
            disable machine;
          end
        end
      end // machine
    end // wrapper_for_synthesis
endmodule
```


```
module count_ones_b1 (bit_count, data, clk, reset);  
  parameter data_width = 4;  
  parameter count_width = 3;  
  output [count_width-1: 0] bit_count;  
  input [data_width-1: 0] data;  
  input clk, reset;  
  reg [count_width-1: 0] count, bit_count;  
  reg [data_width-1: 0] temp;  
  integer index;
```


```
always begin: wrapper_for_synthesis
  @ (posedge clk) begin: machine
    if (reset) begin bit_count = 0; disable machine; end
    else begin
      count = 0; bit_count = 0; index = 0; temp = data;
      while (index < data_width) begin
        if (reset) begin bit_count = 0; disable machine; end
        else if ((index < data_width) && (temp[0] ))
          count = count + 1;
          temp = temp >> 1;
          index = index + 1;
          @ (posedge clk);
        end
        if (reset) begin bit_count = 0; disable machine; end
          else bit_count = count;
        disable machine;
      end
    end // machine
  end // wrapper_for_synthesis
endmodule
```

```

module count_ones_b2 (bit_count, data, clk, reset);
  parameter data_width = 4;
  parameter count_width = 3;
  output [count_width-1: 0] bit_count;
  input [data_width-1: 0] data;
  input clk, reset;
  reg [count_width-1: 0] count, bit_count;
  reg [data_width-1: 0] temp;
  integer index;
  always begin: machine
    for (index = 0; index <= data_width; index = index +1) begin
      @ (posedge clk)
        if (reset) begin bit_count = 0; disable machine; end
        else if (index == 0) begin count = 0; bit_count = 0; temp = data; end
        else if (index < data_width) begin count = count + temp[0]; temp = temp >>
1; end
        else bit_count = count + temp[0];
      end
    end // machine
endmodule

```

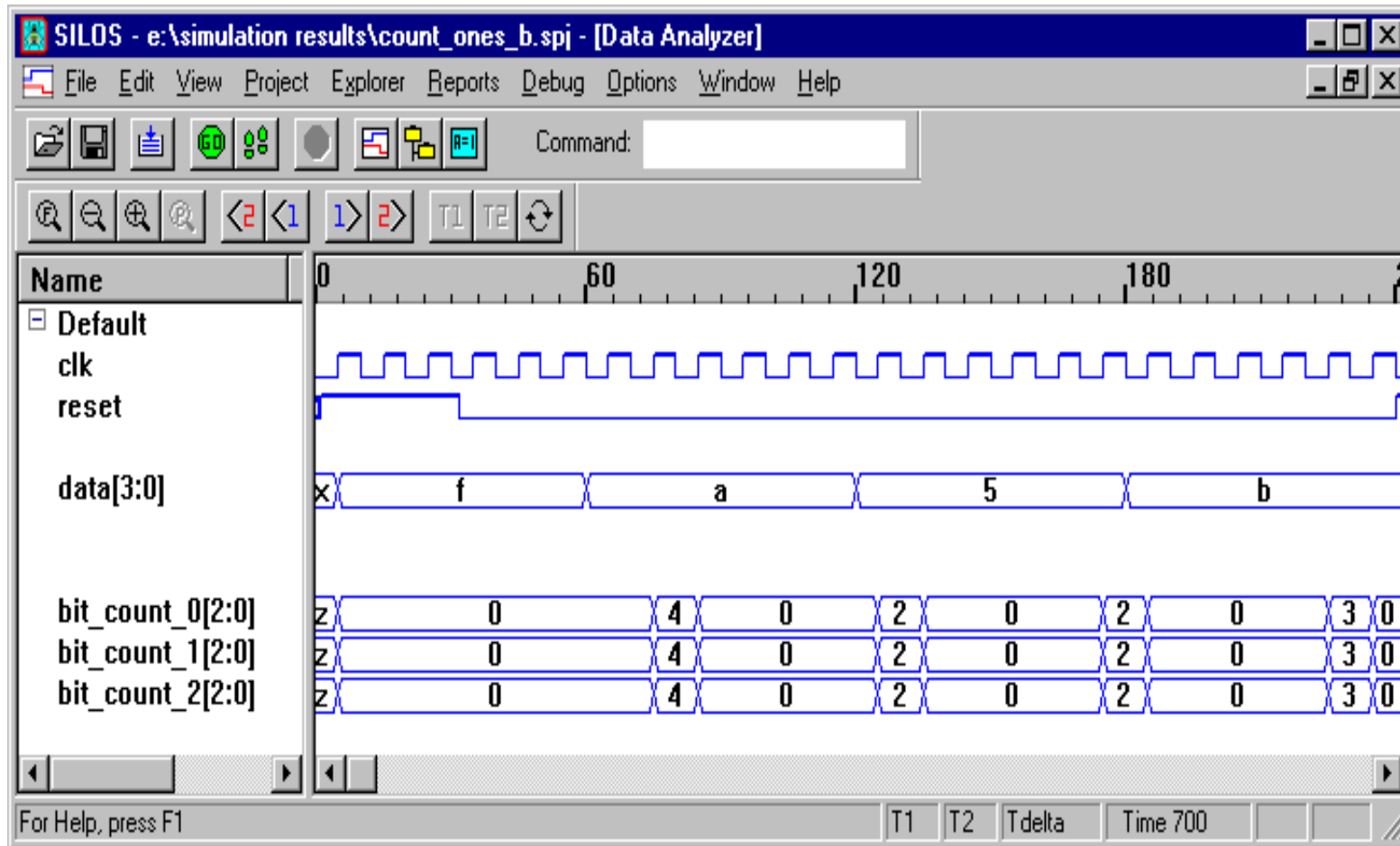

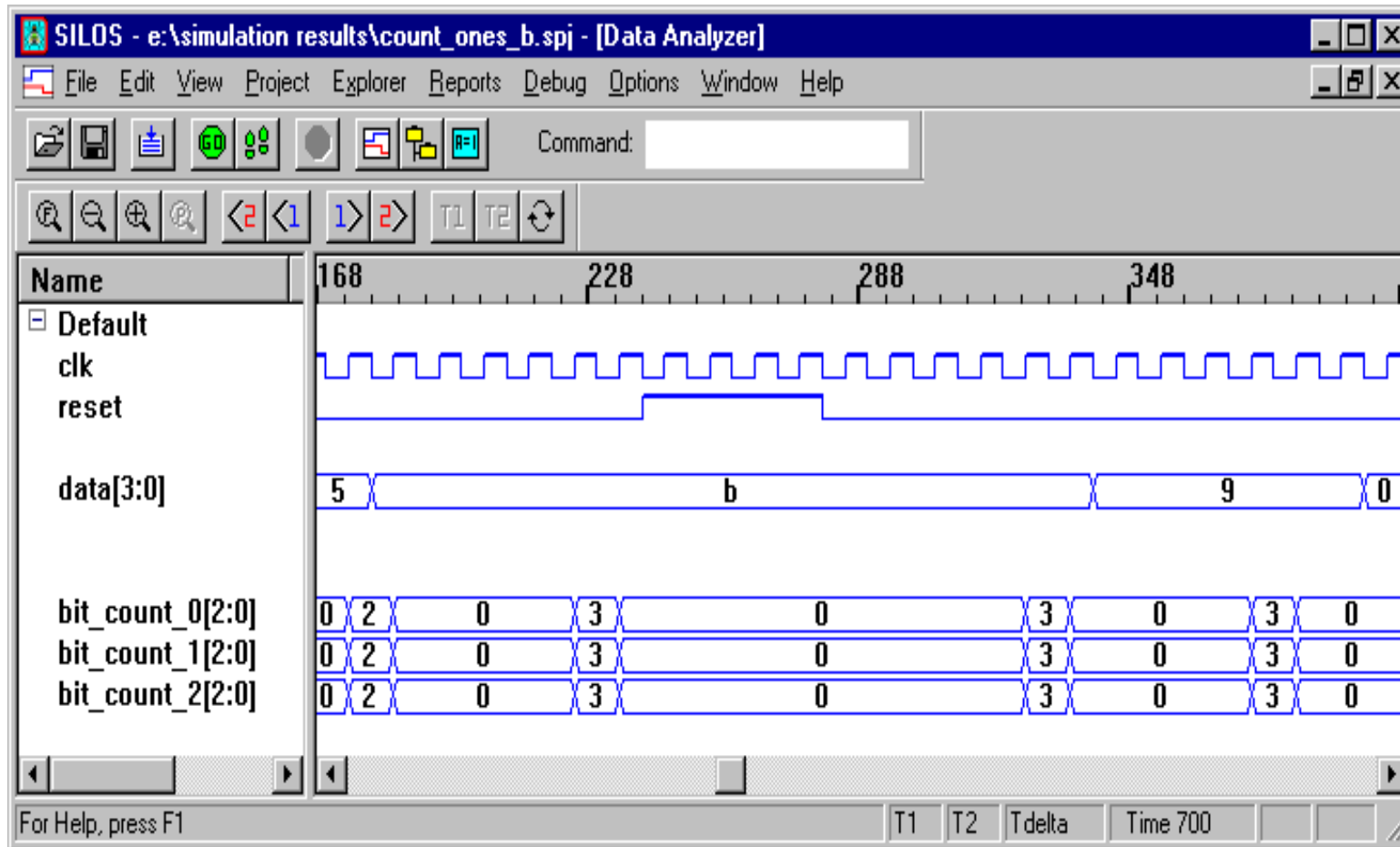


Nonstatic Loops without Embedded Timing Control

The number of iterations to be executed by a loop having a data dependency cannot be determined before simulation.

Example 6.40

```
module count_ones_c (bit_count, data, clk, reset);  
  parameter          data_width = 4;  
  parameter          count_width = 3;  
  output      [count_width-1: 0]    bit_count;  
  input       [data_width-1: 0]     data;  
  input       clk, reset;  
  reg         [count_width-1: 0]     count, bit_count, index;  
  reg         [data_width-1: 0]     temp;
```

```
always @ (posedge clk)  
  if (reset) begin count = 0; bit_count = 0; end  
  else begin  
    count = 0;  
    temp = data;  
    for (index = 0; | temp; index = index + 1) begin  
      if (temp[0] ) count = count + 1;  
      temp = temp >> 1;  
    end  
    bit_count = count;  
  end  
endmodule
```

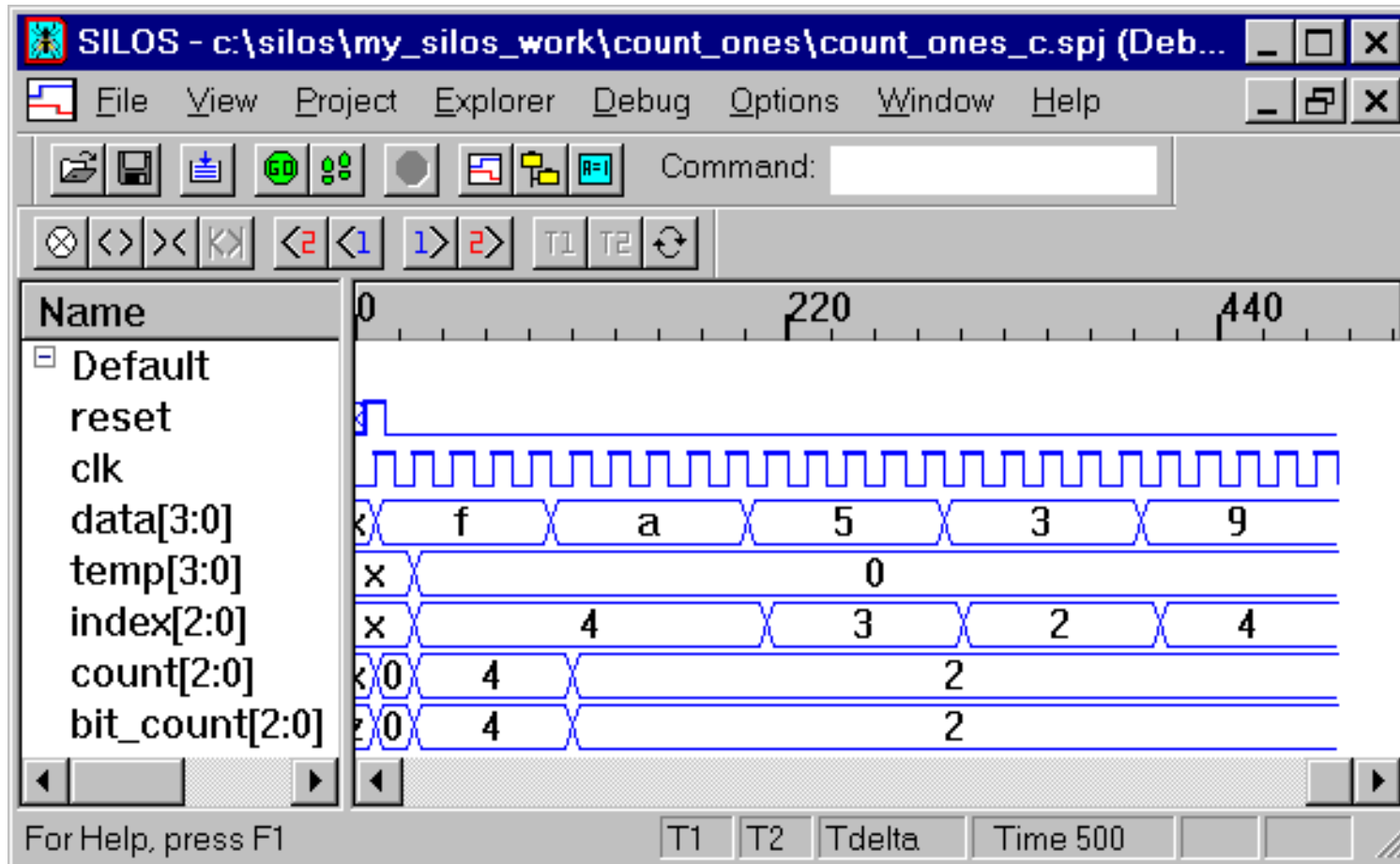

Nonstatic Loops without Embedded Timing Control


For synthesis , the iterations of a non-static loop must be separated by a synchronizing edge-sensitive control expression.

Example 6.41

```
module count_ones_d (bit_count, data, clk, reset);  
  parameter          data_width = 4;  
  parameter          count_width = 3;  
  output      [count_width-1: 0]    bit_count;  
  input       [data_width-1: 0]     data;  
  input       clk, reset;  
  reg         [count_width-1: 0]     count, bit_count;  
  reg         [data_width-1: 0]     temp;
```

```
always begin: wrapper_for_synthesis
  @ (posedge clk)
    if (reset) begin count = 0; bit_count = 0; end
    else begin: bit_counter
      count = 0;
      temp = data;
      while (temp)
        @ (posedge clk)
          if (reset) begin
            count = 2'b0;
            disable bit_counter; end
          else begin
            count = count + temp[0];
            temp = temp >> 1;
          end
        end
      end
    end
```
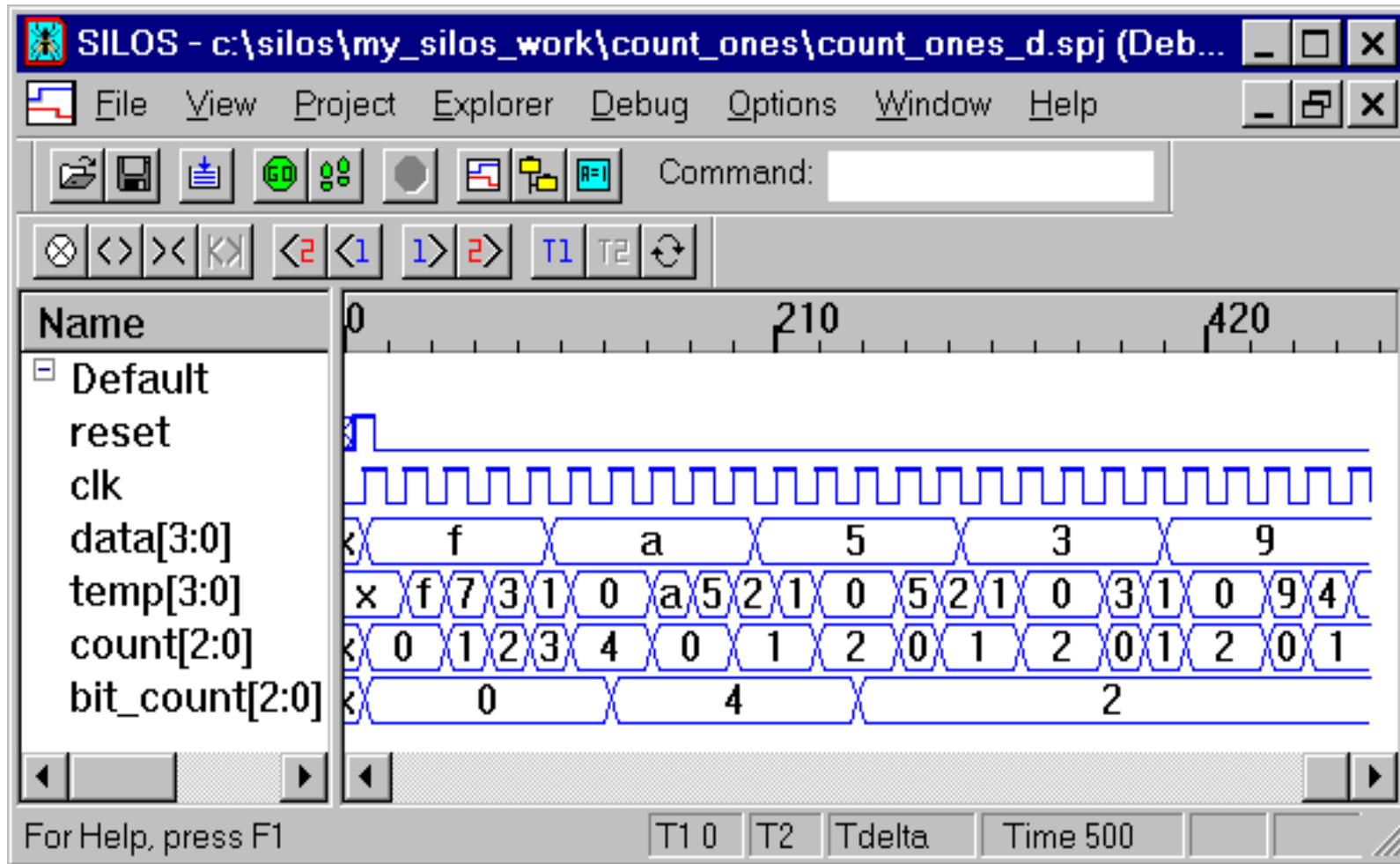
```
@ (posedge clk);  
  if (reset) begin  
    count = 0;  
    disable bit_counter; end  
  else bit_count = count;  
end // bit_counter  
end  
endmodule
```




```
module count_ones_SD (bit_count, done, data, start, clk, reset);  
  parameter data_width = 4;  
  parameter count_width = 3;  
  output      [count_width-1: 0]    bit_count;  
  output      done;  
  input       [data_width-1: 0]    data;  
  input       clk, reset;  
  reg         [count_width-1: 0]    count, bit_count, index;  
  reg         [data_width-1: 0]    temp;  
  reg         done, start;
```

```
always @ (posedge clk) begin: bit_counter  
  if (reset) begin count = 0; bit_count = 0; done = 0; end  
  else if (start) begin  
    done = 0;  
    count = 0;  
    bit_count = 0;  
    temp = data;
```



```
for (index = 0; index < data_width; index = index + 1)
  @ (posedge clk)
  if (reset) begin count = 0; bit_count = 0; done = 0;
    disable bit_counter; end
  else begin
    count = count + temp[0];
    temp = temp >> 1;
  end

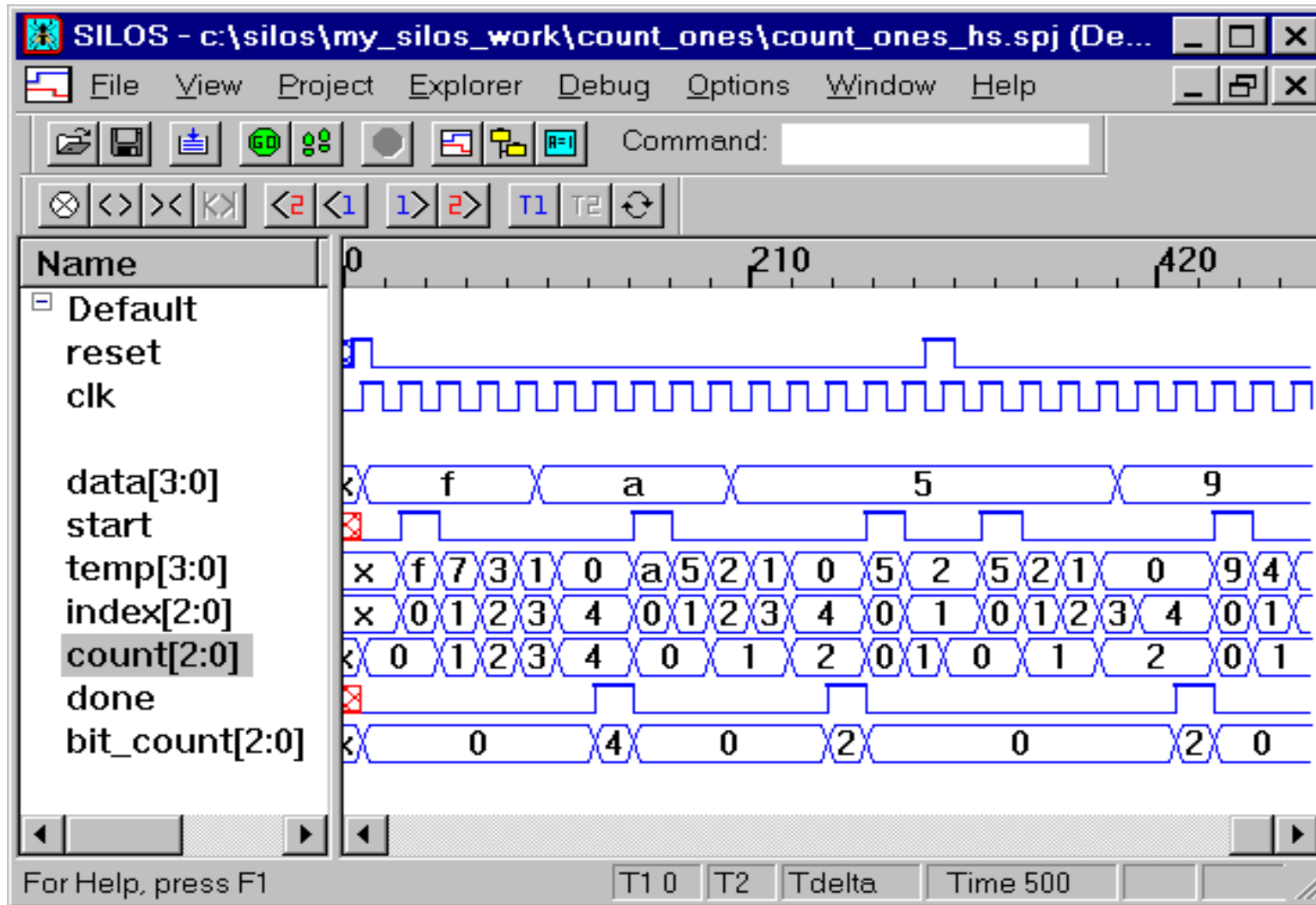
  @ (posedge clk) // Required for final register transfer
  if (reset) begin count = 0; bit_count = 0; done = 0;\
    disable bit_counter; end
  else begin
    bit_count = count;
    done = 1; end
end
end
endmodule
```



State Machine Replacements for Unsynthesizable Loops

Replace loop structures of non-static loops that don't have embedded timing controls by equivalent synthesizable sequential behavior.

Example 6.42

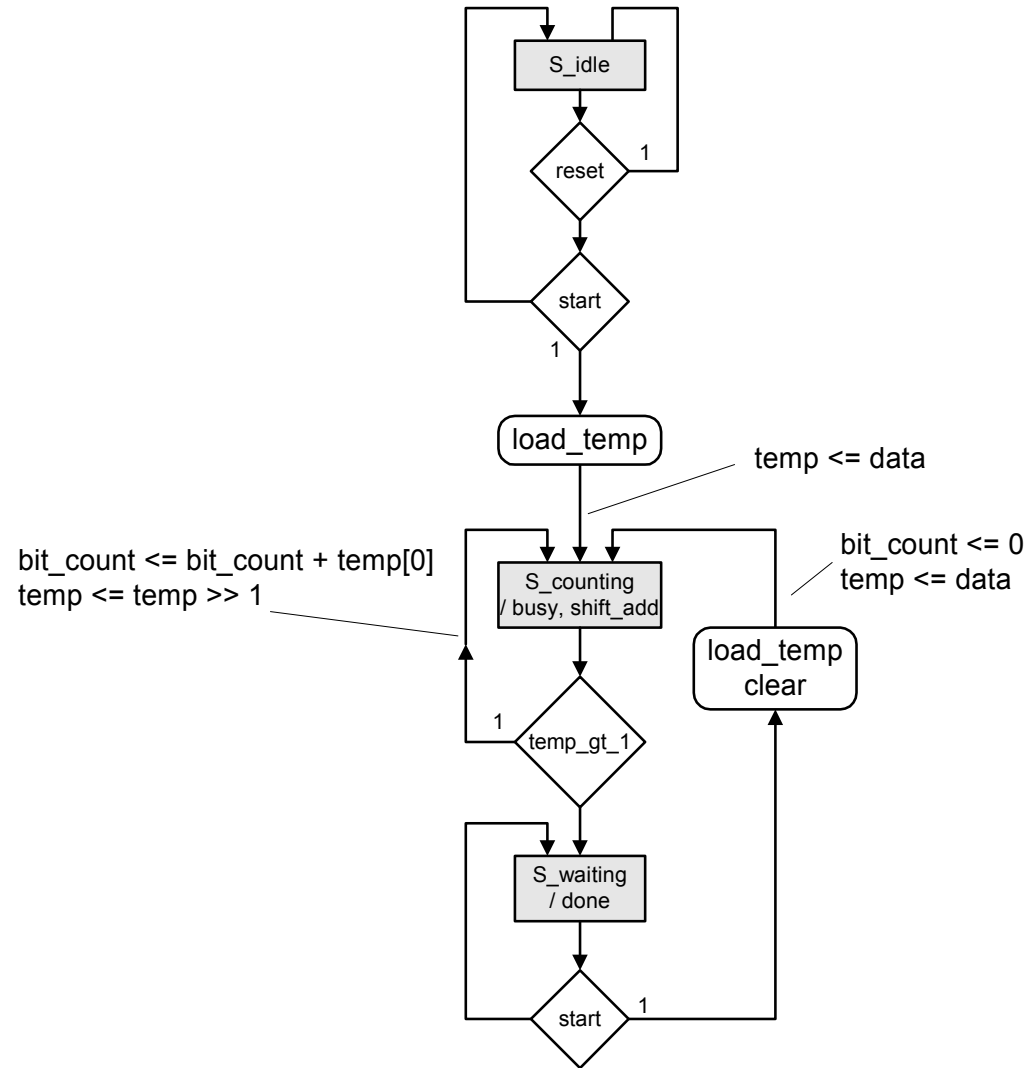

```

module count_ones_SM (bit_count, busy, done, data, start, clk, reset);

  parameter          counter_size = 3;
  parameter          word_size = 4;

  output      [counter_size -1 : 0] bit_count;
  output      busy, done;
  input      [word_size-1: 0] data;
  input      start, clk, reset;
  wire      load_temp, shift_add, clear;
  wire      temp_0, temp_gt_1;

  controller M0 (load_temp, shift_add, clear, busy, done, start, temp_gt_1, clk,
reset);
  datapath M1 (temp_gt_1, temp_0, data, load_temp, shift_add, clk, reset);
  bit_counter_unit M2 (bit_count, temp_0, clear, clk, reset);

endmodule

```

```
module controller (load_temp, shift_add, clear, busy, done, start, temp_gt_1, clk,  
reset);  
  parameter          state_size = 2;  
  parameter          S_idle = 0;  
  parameter          S_counting = 1;  
  parameter          S_waiting = 2;  
  
  output             load_temp, shift_add, clear, busy, done;  
  input              start, temp_gt_1, clk, reset;  
  
  reg                bit_count;  
  reg                [state_size-1 : 0] state, next_state;  
  reg                load_temp, shift_add, busy, done, clear;
```

```
always @ (state or start or temp_gt_1) begin
```

```
load_temp = 0; shift_add = 0; done = 0;
```

```
busy = 0; clear = 0; next_state = S_idle;
```

```
case (state)
```

```
  S_idle: if (start) begin next_state = S_counting; load_temp = 1; end
```

```
  S_counting: begin busy = 1; if (temp_gt_1) begin next_state = S_counting;  
              shift_add = 1; end
```

```
              else begin next_state = S_waiting; shift_add = 1; end
```

```
              end
```

```
  S_waiting: begin
```

```
    done = 1;
```

```
    if (start) begin next_state = S_counting; load_temp = 1; clear = 1; end
```

```
    else next_state = S_waiting;
```

```
  end
```

```
  default: begin clear = 1; next_state = S_idle; end
```

```
endcase
```

```
end
```

```
always @ (posedge clk) // state transitions  
if (reset)  
    state <= S_idle;  
else state <= next_state;  
endmodule
```



```


module datapath (temp_gt_1, temp_0, data, load_temp, shift_add, clk, reset);
  parameter word_size = 4;
  output temp_gt_1, temp_0;
  input [word_size-1: 0] data;
  input load_temp, shift_add, clk, reset;


  reg [word_size-1: 0] temp;
  wire temp_gt_1 = (temp > 1);
  wire temp_0 = temp[0];


  always @ (posedge clk) // state and register transfers
    if (reset) begin
      temp <= 0; end
    else begin
      if (load_temp) temp <= data;
      if (shift_add) begin temp <= temp >> 1; end
    end
endmodule


```

```
module bit_counter_unit (bit_count, temp_0, clear, clk, reset);  
  parameter          counter_size = 3;  
  output      [counter_size -1 : 0] bit_count;  
  input          temp_0;  
  input          clear, clk, reset;  
  reg            bit_count;  
  
  always @ (posedge clk)    // state and register transfers  
    if (reset || clear)  
      bit_count <= 0;  
    else bit_count <= bit_count + temp_0;  
endmodule
```

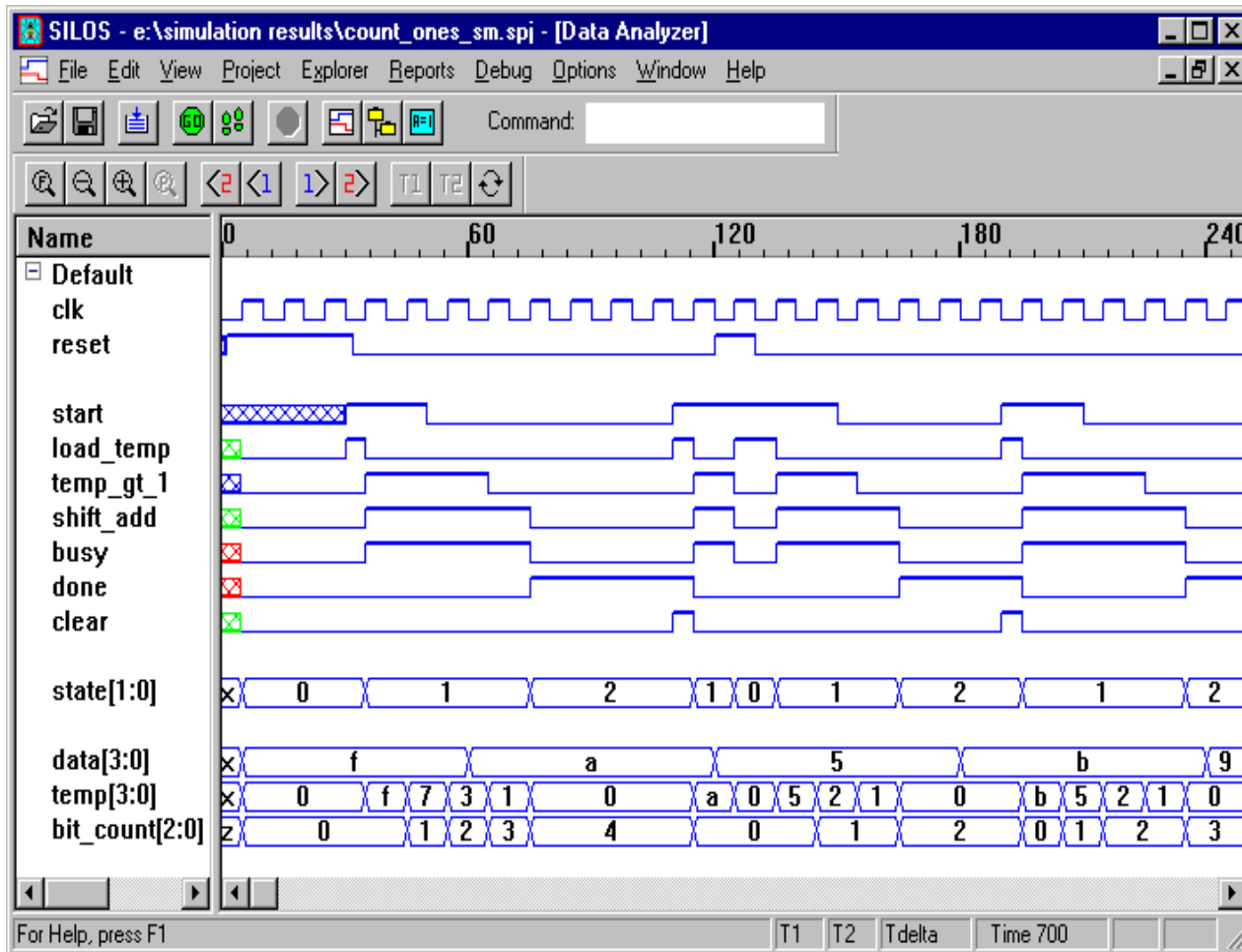

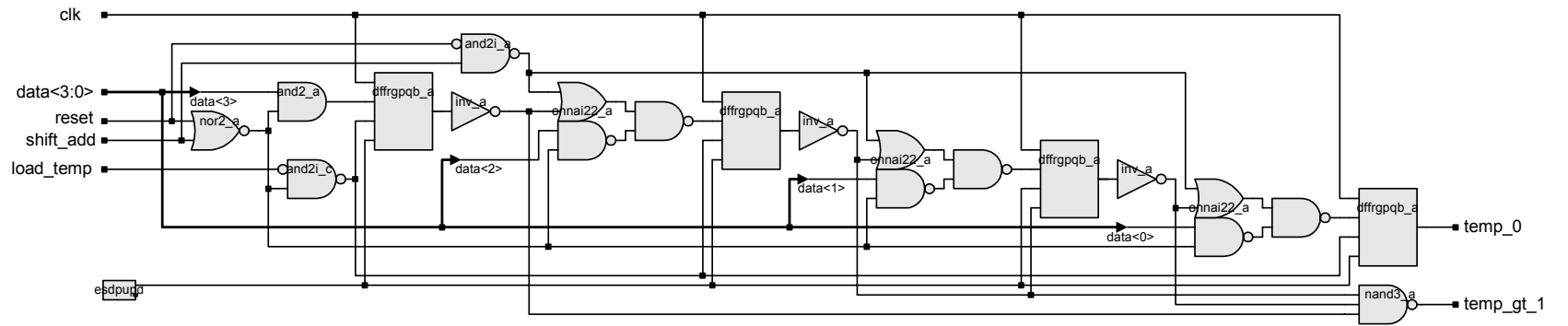

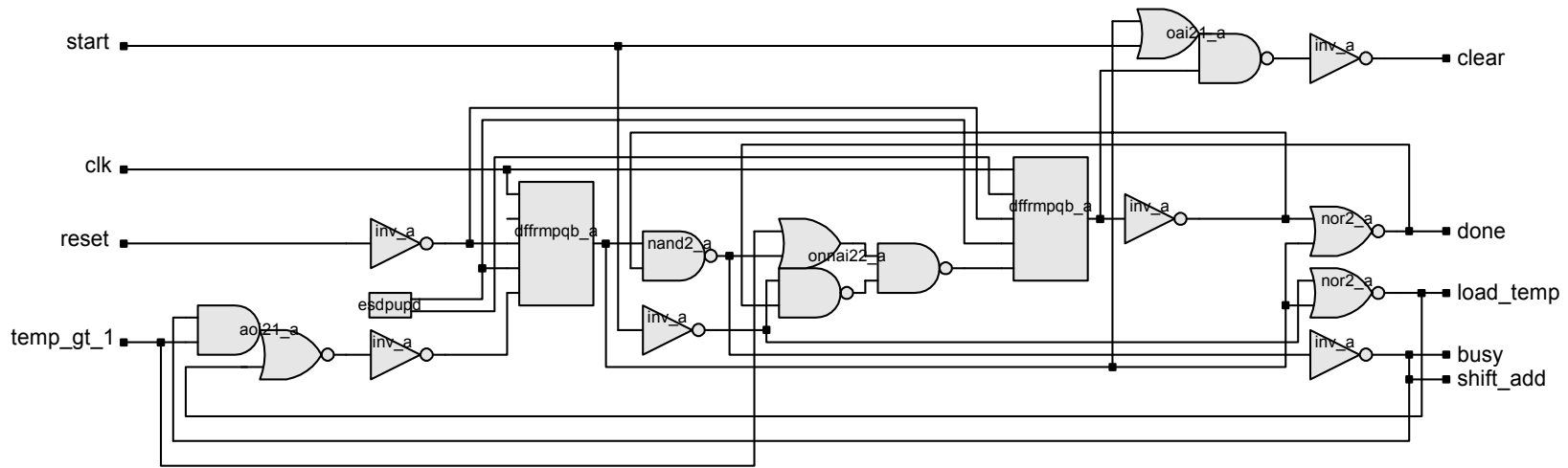

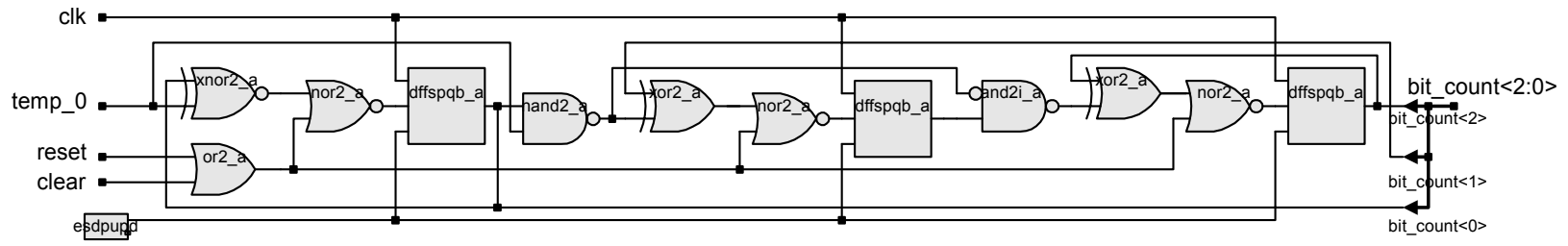

Example 6.43 Implicit State Machine

```

module count_ones_IMP (bit_count, start, done, data, data_ready, clk,
reset);
  parameter                word_size = 4;
  parameter                counter_size = 3;
  parameter                state_size = 2;
  output    [counter_size - 1 : 0] bit_count;
  output    start, done;
  input    [word_size-1: 0] data;
  input    data_ready, clk, reset;

  reg                bit_count;
  reg    [state_size-1 : 0] state, next_state;
  reg    start, done, clear;
  reg    [word_size-1: 0] temp;

```

```
always @ (posedge clk) if (reset)  
  begin temp<= 0; bit_count <= 0; done <= 0; start <= 0; end  
  else if (data_ready && data && !temp)  
    begin temp <= data; bit_count <= 0; done <= 0; start <= 1; end  
  else if (data_ready && (!data) && done)  
    begin bit_count <= 0; done <= 1; end  
  else if (temp == 1)  
    begin bit_count <= bit_count + temp[0]; temp <= temp >> 1; done <=  
1; end  
    else if (temp && !done)  
      begin start <= 0; temp <= temp >> 1; bit_count <= bit_count +  
temp[0]; end  
endmodule
```