 


Advanced Digital Design with the Verilog HDL



M. D. Ciletti

Department
of

Electrical and Computer Engineering
University of Colorado
Colorado Springs, Colorado


ciletti@vlsic.uccs.edu

Draft: Chap 5: Logic Design with Behavioral Models of Combinational and Sequential Logic (Rev 9/23/2003)

Copyright 2000, 2002, 2003. These notes are solely for classroom use by the instructor. No part of these notes may be copied, reproduced, or distributed to a third party, including students, in any form without the written permission of the author.

Note to the instructor: These slides are provided solely for classroom use in academic institutions by the instructor using the text, *Advance Digital Design with the Verilog HDL* by Michael Ciletti, published by Prentice Hall. This material may not be used in off-campus instruction, resold, reproduced or generally distributed in the original or modified format for any purpose without the permission of the Author. This material may not be placed on any server or network, and is protected under all copyright laws, as they currently exist. I am providing these slides to you subject to your agreeing that you will not provide them to your students in hardcopy or electronic format or use them for off-campus instruction of any kind. Please email to me your agreement to these conditions.

 I will greatly appreciate your assisting me by calling to my attention any errors or any other revisions that would enhance the utility of these slides for classroom use.



COURSE OVERVIEW

- Review of combinational and sequential logic design
- Modeling and verification with hardware description languages
- Introduction to synthesis with HDLs
- Programmable logic devices
- State machines, datapath controllers, RISC CPU
- Architectures and algorithms for computation and signal processing
- Synchronization across clock domains
- Timing analysis
- Fault simulation and testing, JTAG, BIST

Data Types

- Two families of data types for variables:

Nets: wire, tri, wand, triand, wor, trior, supply0, supply1

Registers: reg, integer, real, time, realtime

- Nets establish structural connectivity
- Register variables act as storage containers for the waveform of a signal
- Default size of a net or reg variable is a signal bit
- An **integer** is stored at a minimum of 32 bits
- **time** is stored as 64 bit integer
- **real** is stored as a real number
- **realtime** stores the value of time as a real number

Behavioral Models

- Behavioral models are abstract descriptions of functionality.
- Widely used for quick development of model
- Follow by synthesis
- We'll consider two types:
 - Continuous assignment (Boolean equations)
 - Cyclic behavior (more general, e.g. algorithms)

Example: Abstract Models of Boolean Equations

- Continuous assignments (Keyword: **assign**) are the Verilog counterpart of Boolean equations
- Hardware is implicit (i.e. combinational logic)

Example 5.1 (p 145): Revisit the AOI circuit in Figure 4.7

```
module AOI_5_CA0 (y_out, x_in1, x_in2, x_in3, x_in4, x_in5);  
  input      x_in1, x_in2, x_in3, x_in4, x_in5;  
  output     y_out;  
  
  assign y_out = ~((x_in1 & x_in2) | (x_in3 & x_in4 & x_in5));  
  
endmodule
```


- The LHS variable is monitored automatically and updates when the RHS expression changes value

Example 5.2 (p 146)

```
module AOI_5_CA1 (y_out, x_in1, x_in2, x_in3, x_in4, x_in5, enable);  
  input      x_in1, x_in2, x_in3, x_in4, x_in5, enable;  
  output     y_out;  
  
  assign y_out = enable ? ~((x_in1 & x_in2) | (x_in3 & x_in4 & x_in5)) : 1'bz;  
  
endmodule
```

- The *conditional operator* (`? :`) acts like a software if-then-else switch that selects between two expressions.
- Must provide both expressions

Equivalent circuit:

 


Implicit Continuous Assignment

Example 5.3

```
module AOI_5_CA2 (y_out, x_in1, x_in2, x_in3, x_in4, x_in5, enable);  
  input      x_in1, x_in2, x_in3, x_in4, x_in5, enable;  
  output    y_out;  
  
  wire y_out = enable ? ~((x_in1 & x_in2) | (x_in3 & x_in4 & x_in5)) : 1'bz;  
  
endmodule
```

Example 5.4 (p 148)

 

```
module Mux_2_32_CA ( mux_out, data_1, data_0, select);  
  parameter word_size = 32;  
  output [word_size -1: 0] mux_out;  
  input [word_size-1: 0] data_1, data_0;  
  input select;  
  
  assign mux_out = select ? data_1 : data_0;  
endmodule
```

Propagation Delay for Continuous Assignments

Example 5.3 (Note: Three-state behavior)

```
module AOI_5_CA2 (y_out, x_in1, x_in2, x_in3, x_in4);  
  input      x_in1, x_in2, x_in3, x_in4;  
  output    y_out;  
  
  wire #1 y1 = x_in1 & x_in2; // Bitwise and operation  
  wire #1 y2 = x_in3 & x_in4;  
  wire #1 y_out = ~ (y1 | y2); // Complement the result of bitwise OR operation  
endmodule
```


Multiple Continuous Assignments

- Multiple continuous assignments are active concurrently

```
module compare_2_CA0 (A_lt_B, A_gt_B, A_eq_B, A1, A0, B1, B0);  
  input   A1, A0, B1, B0;  
  output  A_lt_B, A_gt_B, A_eq_B;  
  
  assign A_lt_B = (~A1) & B1 | (~A1) & (~A0) & B0 | (~A0) & B1 & B0;  
  assign A_gt_B = A1 & (~B1) | A0 & (~B1) & (~B0) | A1 & A0 & (~B0);  
  assign A_eq_B = (~A1) & (~A0) & (~B1) & (~B0) | (~A1) & A0 & (~B1) & B0  
                | A1 & A0 & B1 & B0 | A1 & (~A0) & B1 & (~B0);  
  
endmodule
```

- Note: this style can become unwieldy and error-prone

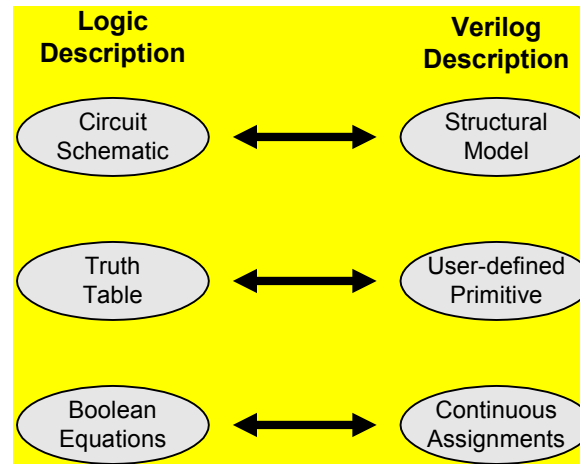Review of Modeling Styles for Combinational Logic



Latched and Level-Sensitive Behavior

- Avoid explicit or implicit structural feedback
- It simulates but won't synthesize
- Timing analyzers won't work either

Example

```
assign q = set ~& qbar;  
assign qbar = rst ~& q;
```


Recommended Style for Transparent Latch

- Use a continuous assignment with feedback to model a latch
- Synthesis tools understand this model

Example 5.7

```
module Latch_CA (q_out, data_in, enable);  
  output      q_out;  
  input       data_in, enable;  
  
  assign q_out = enable ? data_in : q_out;  
endmodule
```

Simulation results:

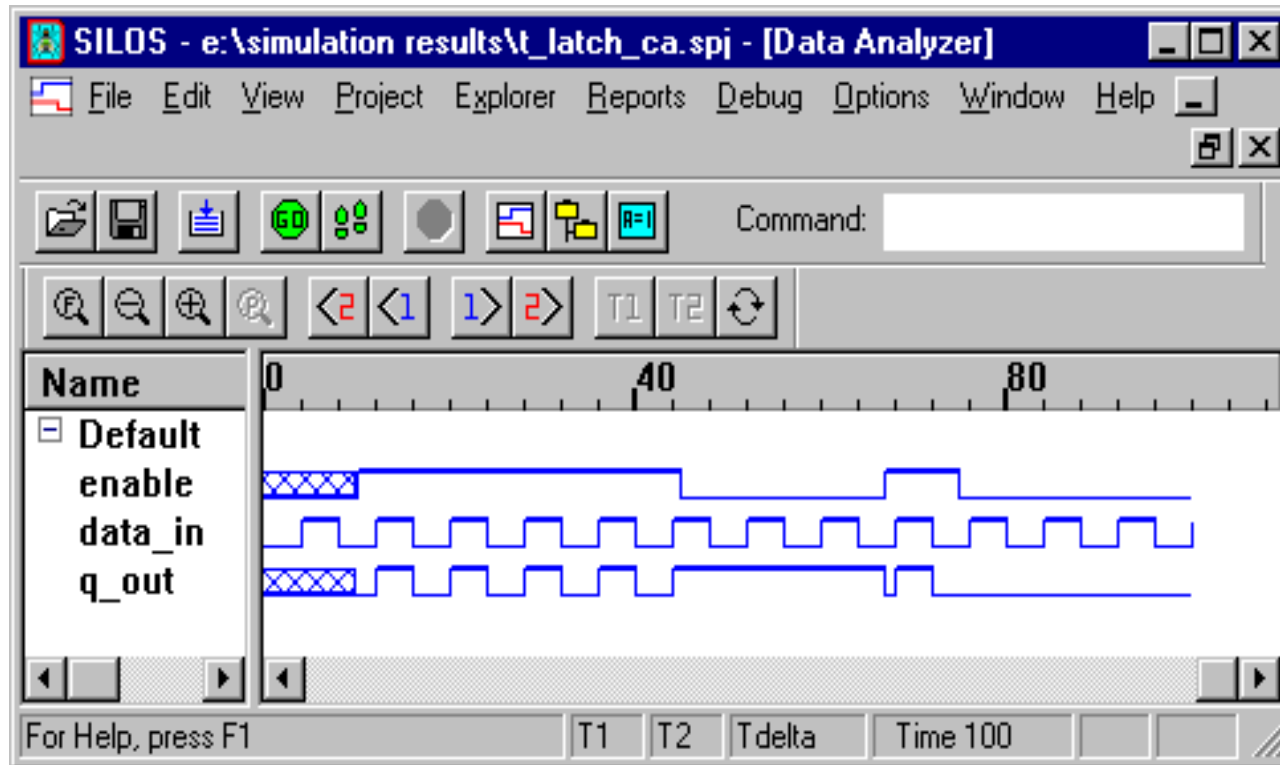


Example: T-Latch with Active-Low Reset

Example 5.8: T-latch with active-low reset (nested conditional operators)

```
module Latch_Rbar_CA (q_out, data_in, enable, reset_bar);  
  output      q_out;  
  input       data_in, enable, reset_bar;  
  
  assign q_out = !reset_bar ? 0 : enable ? data_in : q_out;  
endmodule
```

Simulation results:

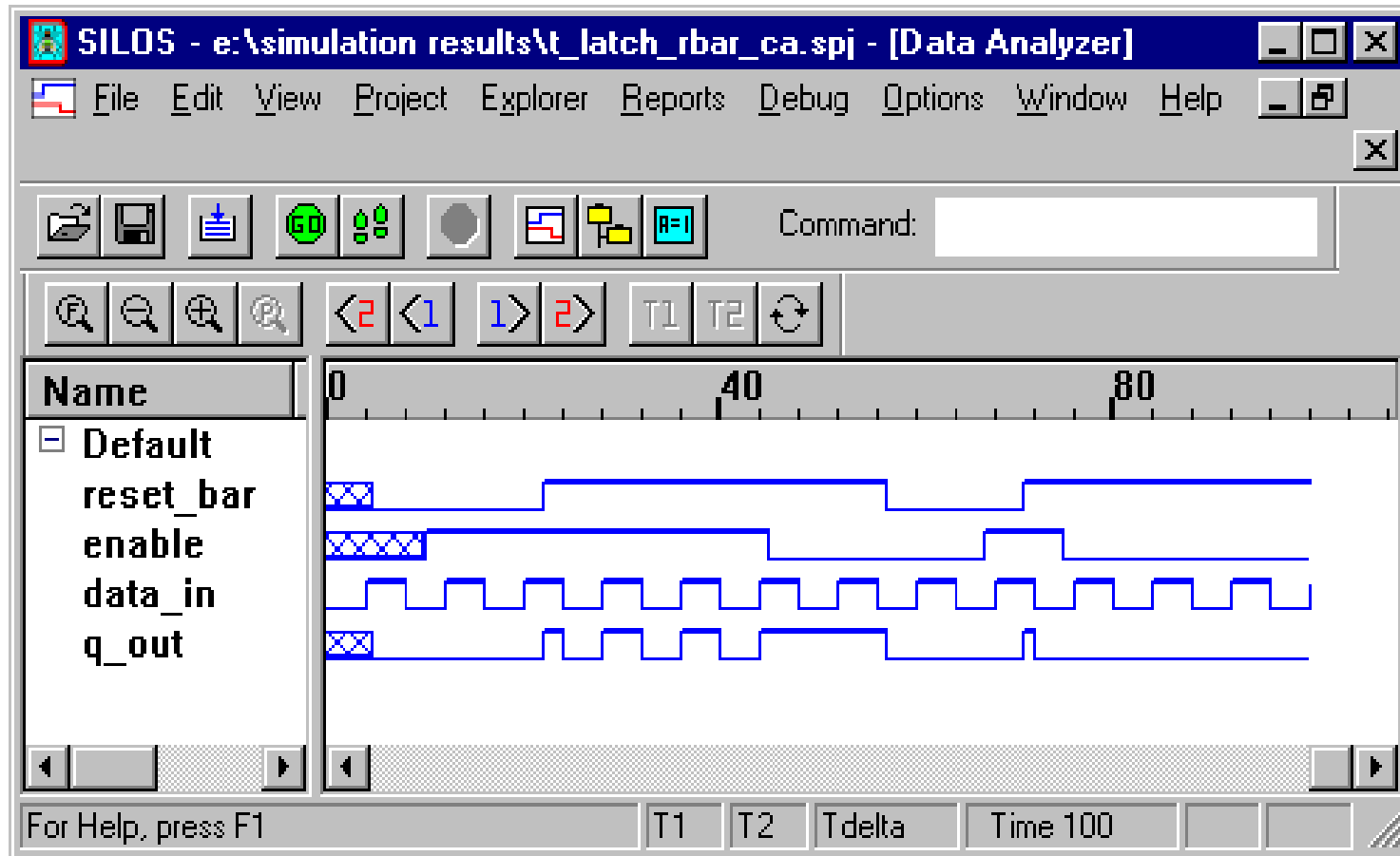

Abstract Modeling with Cyclic Behaviors

- Cyclic behaviors assign values to register variables to describe the behavior of hardware
- Model level-sensitive and edge-sensitive behavior
- Synthesis tool selects the hardware
- Note: Cyclic behaviors re-execute after executing the last procedural statement executes (subject to timing controls – more on this later)

Example 5.9: D-type Flip-Flop

```
module df_behav (q, q_bar, data, set, reset, clk);
input          data, set, clk, reset;
output        q, q_bar;
reg           q;

assign q_bar = ~ q;

always @ (posedge clk) // Flip-flop with synchronous set/reset
begin
  if (reset == 0) q <= 0;      // <= is the nonblocking assignment operator
  else if (set == 0) q <= 1;
  else q <= data;
end
endmodule
```

Example 5.10 (Asynchronous reset)

```
module asynch_df_behav (q, q_bar, data, set, clk, reset );  
  input      data, set, reset, clk;  
  output    q, q_bar;  
  reg       q;  
  
  assign q_bar = ~q;  
  
  always @ (negedge set or negedge reset or posedge clk)  
  begin  
    if (reset == 0) q <= 0;  
    else if (set == 0) q <= 1;  
    else q <= data;           // synchronized activity  
  end  
endmodule
```

Note: See discussion in text

Note: Consider simultaneous assertion of set and reset).

Example: Transparent Latch (Cyclic Behavior)

```
module tr_latch (q_out, enable, data);  
  output q_out;  
  input enable, data;  
  reg q_out;  
  
  always @ (enable or data)  
  begin  
    if (enable) q_out = data;  
  end  
endmodule
```

Alternative Behavioral Models

Example 5. 12 (Two-bit comparator)

```
module compare_2_CA1 (A_lt_B, A_gt_B, A_eq_B, A1, A0, B1, B0);  
  input      A1, A0, B1, B0;  
  output    A_lt_B, A_gt_B, A_eq_B;  
  
  assign A_lt_B = ({A1,A0} < {B1,B0});  
  assign A_gt_B = ({A1,A0} > {B1,B0});  
  assign A_eq_B = ({A1,A0} == {B1,B0});  
endmodule
```

Example 5.13 (Clarity!)

```
module compare_2_CA1 (A_lt_B, A_gt_B, A_eq_B, A, B);  
  input   [1: 0]    A, B;  
  output          A_lt_B, A_gt_B, A_eq_B;  
  
  assign A_lt_B = (A < B);    // The RHS expression is true (1) or false (0)  
  assign A_gt_B = (A > B);  
  assign A_eq_B = (A == B);  
endmodule
```


Example 5.14 (Parameterized and reusable model)

```
module compare_32_CA (A_gt_B, A_lt_B, A_eq_B, A, B);  
  parameter word_size = 32;  
  input      [word_size-1: 0] A, B;  
  output    A_gt_B, A_lt_B, A_eq_B;  
  
  assign A_gt_B = (A > B),           // Note: list of multiple assignments  
          A_lt_B = (A < B),  
          A_eq_B = (A == B);  
endmodule
```

Dataflow – RTL Models

- Dataflow (register transfer level) models of combinational logic describe concurrent operations on datapath signals, usually in a synchronous machine

Example 5.15

```
module compare_2_RTL (A_lt_B, A_gt_B, A_eq_B, A1, A0, B1, B0);  
input      A1, A0, B1, B0;  
output    A_lt_B, A_gt_B, A_eq_B;  
reg      A_lt_B, A_gt_B, A_eq_B;  
  
  always @ (A0 or A1 or B0 or B1) begin  
    A_lt_B =  ({A1,A0} < {B1,B0});  
    A_gt_B =  ({A1,A0} > {B1,B0});  
    A_eq_B =  ({A1,A0} == {B1,B0});  
  end  
endmodule
```

Modeling Trap

- The order of execution of procedural statements in a cyclic behavior may depend on the order in which the statements are listed
- A procedural assignment cannot execute until the previous statement executes
- Expression substitution is recognized by synthesis tools


Example 5.16

```

module shiftreg_PA (E, A, clk, rst);
  output A;
  input E;
  input clk, rst;
  reg A, B, C, D;

  always @ (posedge clk or posedge rst) begin
    if (reset) begin A = 0; B = 0; C = 0; D = 0; end
    else begin
      A = B;
      B = C;
      C = D;
      D = E;
    end
  end
endmodule

```

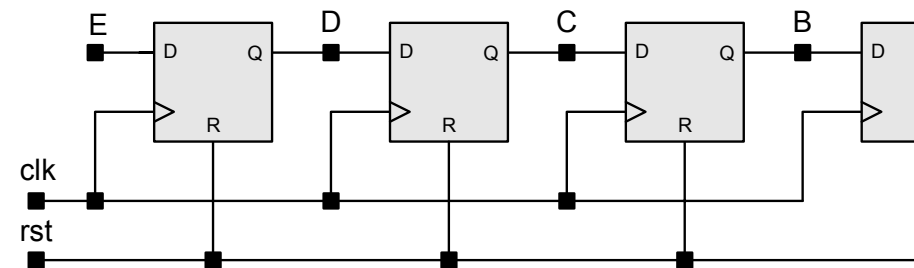Result of synthesis:

Reverse the order of the statements:

```

module shiftreg_PA_rev (A, E, clk, rst);
  output A;
  input E;
  input clk, rst;
  reg A, B, C, D;

  always @ (posedge clk or posedge rst) begin
    if (rst) begin A = 0; B = 0; C = 0; D = 0; end
    else begin
      D = E;
      C = D;
      B = C;
      A = B;
    end
  end
endmodule

```

Result of synthesis:

 


Figure 5.8 Circuit synthesized as a result of expression substitution in an incorrect model of a 4-bit serial shift register.

Nonblocking Assignment Operator and Concurrent Assignments

- Nonblocking assignment statements execute *concurrently* (in parallel) rather than sequentially
- The order in which nonblocking assignments are listed has no effect.
- Mechanism: the RHS of the assignments are sampled, then assignments are updated
- Assignments are based on values held by RHS before the statements execute
- Result: No dependency between statements

Example: Shift Register

Example 5.17

```
module shiftreg_nb (A, E, clk, rst);
  output A;
  input E;
  input clk, rst;
  reg A, B, C, D;


  always @ (posedge clk or posedge rst) begin
    if (rst) begin A <= 0; B <= 0; C <= 0; D <= 0; end
    else begin
      A <= B;          // D <= E;
      B <= C;          // C <= D;
      C <= D;          // B <= D;
      D <= E;          // A <= B;
    end
  end
endmodule
```


Algorithm-Based Models

Example 5.18

```
module compare_2_algo (A_lt_B, A_gt_B, A_eq_B, A, B);  
  output      A_lt_B, A_gt_B, A_eq_B;  
  input   [1: 0]  A, B;  
  
  reg      A_lt_B, A_gt_B, A_eq_B;  
  
  always @ (A or B)    // Level-sensitive behavior  
  begin  
    A_lt_B = 0;  
    A_gt_B = 0;  
    A_eq_B = 0;  
    if (A == B)      A_eq_B = 1;    // Note: parentheses are required  
    else if (A > B)  A_gt_B = 1;  
    else             A_lt_B = 1;  
  end  
endmodule
```


Result of synthesis:

 

Simulation with Behavioral Models

See discussion in text – p 165

 Example 5.19: Four-Channel Mux with Three-State Output



```
module Mux_4_32_case (mux_out, data_3, data_2, data_1, data_0, select, enable);  
  output [31: 0] mux_out;  
  input [31: 0] data_3, data_2, data_1, data_0;  
  input [1: 0] select;  
  input enable;  
  reg [31: 0] mux_int;  
  
  assign mux_out = enable ? mux_int : 32'bz;  
  
  always @ ( data_3 or data_2 or data_1 or data_0 or select)  
  case (select)  
    0: mux_int = data_0;  
    1: mux_int = data_1;  
    2: mux_int = data_2;  
    3: mux_int = data_3;  
    default: mux_int = 32'bx; // May execute in simulation  
  endcase  
endmodule
```

Example 5.20: Alternative Model

```
module Mux_4_32_if
  (mux_out, data_3, data_2, data_1, data_0, select, enable);
output [31: 0] mux_out;
input [31: 0] data_3, data_2, data_1, data_0;
input [1: 0] select;
input enable;
reg [31: 0] mux_int;

assign mux_out = enable ? mux_int : 32'bz;

always @ (data_3 or data_2 or data_1 or data_0 or select)
  if (select == 0) mux_int = data_0; else
    if (select == 1) mux_int = data_1; else
      if (select == 2) mux_int = data_2; else
        if (select == 3) mux_int = data_3; else mux_int = 32'bx;
endmodule
```


Example 5.21: Alternative Model

```
module Mux_4_32_CA (mux_out, data_3, data_2, data_1, data_0, select, enable);
    output      [31: 0]  mux_out;
    input       [31: 0]  data_3, data_2, data_1, data_0;
    input       [1: 0]   select;
    input                               enable;
    wire        [31: 0]  mux_int;

    assign mux_out = enable ? mux_int : 32'bz;
    assign mux_int = (select == 0) ? data_0 :
                    (select == 1) ? data_1 :
                    (select == 2) ? data_2 :
                    (select == 3) ? data_3: 32'bx;

endmodule
```

Example 5.22: Encoder

 

```

module encoder (Code, Data);
  output      [2: 0] Code;
  input       [7: 0] Data;
  reg         [2: 0] Code;


  always @ (Data)
  begin
    if (Data == 8'b00000001) Code = 0; else
    if (Data == 8'b00000010) Code = 1; else
    if (Data == 8'b00000100) Code = 2; else
    if (Data == 8'b00001000) Code = 3; else
    if (Data == 8'b00010000) Code = 4; else
    if (Data == 8'b00100000) Code = 5; else
    if (Data == 8'b01000000) Code = 6; else
    if (Data == 8'b10000000) Code = 7; else Code = 3'bx;
  end

```


/* Alternative description is given below

```
always @ (Data)
  case (Data)
    8'b00000001 : Code = 0;
    8'b00000010 : Code = 1;
    8'b00000100 : Code = 2;
    8'b00001000 : Code = 3;
    8'b00010000 : Code = 4;
    8'b00100000 : Code = 5;
    8'b01000000 : Code = 6;
    8'b10000000 : Code = 7;
    default : Code = 3'bx;
  endcase
*/
endmodule
```

Synthesis result (standard cells):

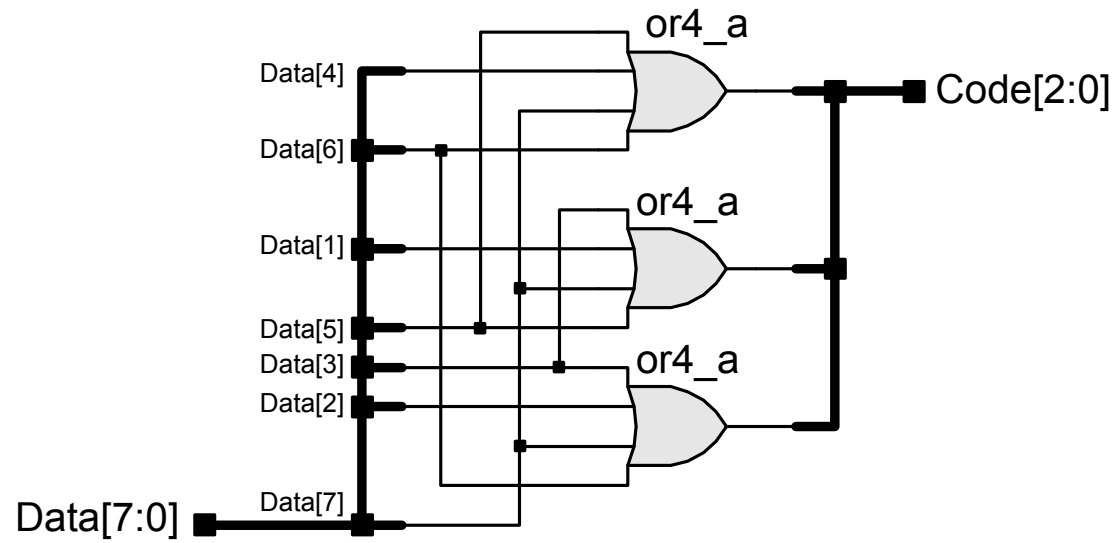

Example 5.23: Priority Encoder


```

module priority (Code, valid_data, Data);
  output      [2: 0] Code;
  output      valid_data;
  input       [7: 0] Data;
  reg        [2: 0] Code;

  assign      valid_data = |Data; // "reduction or" operator

  always @ (Data)
  begin
    if (Data[7]) Code = 7; else
    if (Data[6]) Code = 6; else
    if (Data[5]) Code = 5; else
    if (Data[4]) Code = 4; else
    if (Data[3]) Code = 3; else
    if (Data[2]) Code = 2; else
    if (Data[1]) Code = 1; else
    if (Data[0]) Code = 0; else
      Code = 3'bx;
  end


```

 

/*// Alternative description is given below

```
always @ (Data)
  case (Data)
    8'b1xxxxxxx : Code = 7;
    8'b01xxxxxx : Code = 6;
    8'b001xxxxx : Code = 5;
    8'b0001xxxx : Code = 4;
    8'b00001xxx : Code = 3;
    8'b000001xx : Code = 2;
    8'b0000001x : Code = 1;
    8'b00000001 : Code = 0;
    default : Code = 3'bx;
  endcase
*/
endmodule
```

Synthesis Result:

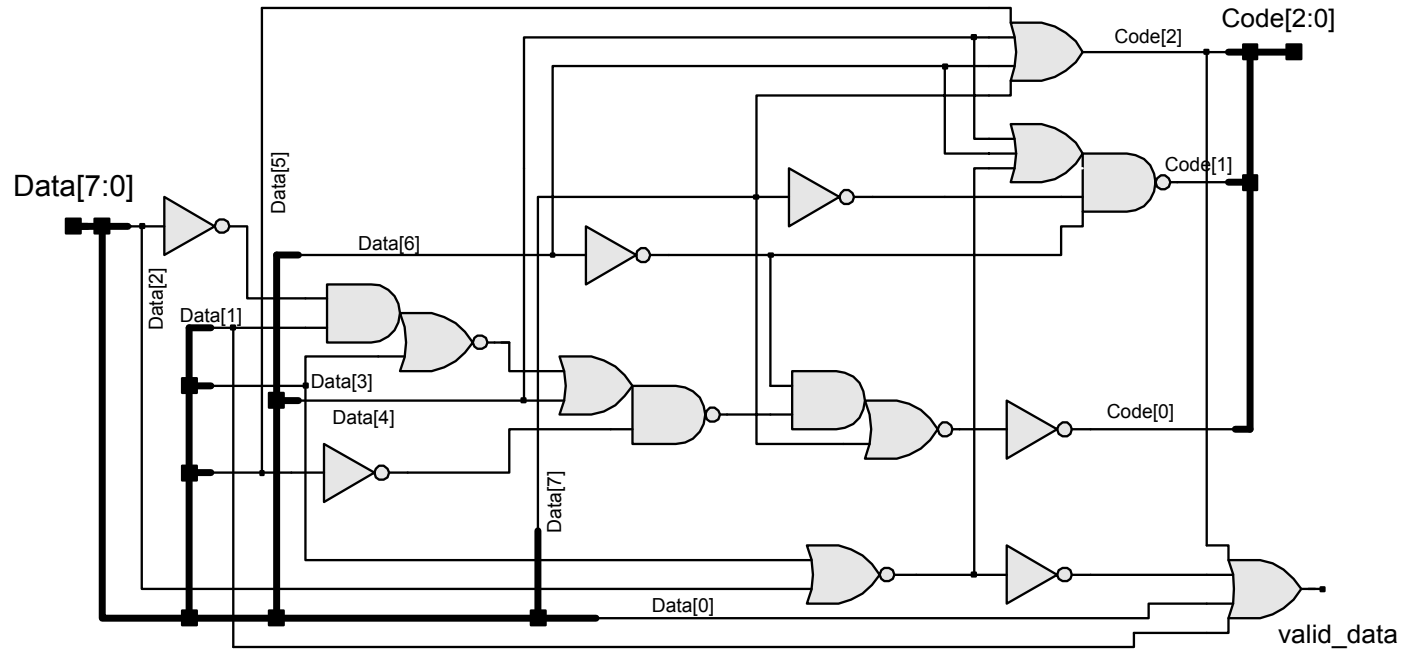

Example 5.24: Decoder




```
module decoder (Data, Code);
  output      [7: 0] Data;
  input       [2: 0] Code;
  reg        [7: 0] Data;


  always @ (Code)
  begin
    if (Code == 0) Data = 8'b00000001; else
    if (Code == 1) Data = 8'b00000010; else
    if (Code == 2) Data = 8'b00000100; else
    if (Code == 3) Data = 8'b00001000; else
    if (Code == 4) Data = 8'b00010000; else
    if (Code == 5) Data = 8'b00100000; else
    if (Code == 6) Data = 8'b01000000; else
    if (Code == 7) Data = 8'b10000000; else
      Data = 8'bx;
  end
end
```

```
/* Alternative description is given below
always @ (Code)
  case (Code)
    0      : Data = 8'b00000001;
    1      : Data = 8'b00000010;
    2      : Data = 8'b00000100;
    3      : Data = 8'b00001000;
    4      : Data = 8'b00010000;
    5      : Data = 8'b00100000;
    6      : Data = 8'b01000000;
    7      : Data = 8'b10000000;
    default: Data = 8'bx;
  endcase
*/
endmodule
```

Synthesis Result:

 

Example 5.25: Seven Segment Display

 

```

module Seven_Seg_Display (Display, BCD);
  output [6: 0]Display;
  input   [3: 0]BCD;
  reg    [6: 0]Display;
  //
  //          abc_defg
  parameter BLANK   = 7'b111_1111;
  parameter ZERO    = 7'b000_0001;           // h01
  parameter ONE     = 7'b100_1111;           // h4f
  parameter TWO     = 7'b001_0010;           // h12
  parameter THREE   = 7'b000_0110;           // h06

```

```
parameter FOUR    = 7'b100_1100;           // h4c
parameter FIVE    = 7'b010_0100;           // h24
parameter SIX      = 7'b010_0000;           // h20
parameter SEVEN    = 7'b000_1111;           // h0f
parameter EIGHT    = 7'b000_0000;           // h00
parameter NINE     = 7'b000_0100;           // h04
```

```
always @ (BCD or)
```


```
  case (BCD)
```

```
    0:      Display = ZERO;
    1:      Display = ONE;
    2:      Display = TWO;
    3:      Display = THREE;
    4:      Display = FOUR;
    5:      Display = FIVE;
    6:      Display = SIX;
    7:      Display = SEVEN;
    8:      Display = EIGHT;
    9:      Display = NINE;
  default: Display = BLANK;
```

```
  endcase
```

```
endmodule
```

Example 5.26: LFSR (RTL – Dataflow)

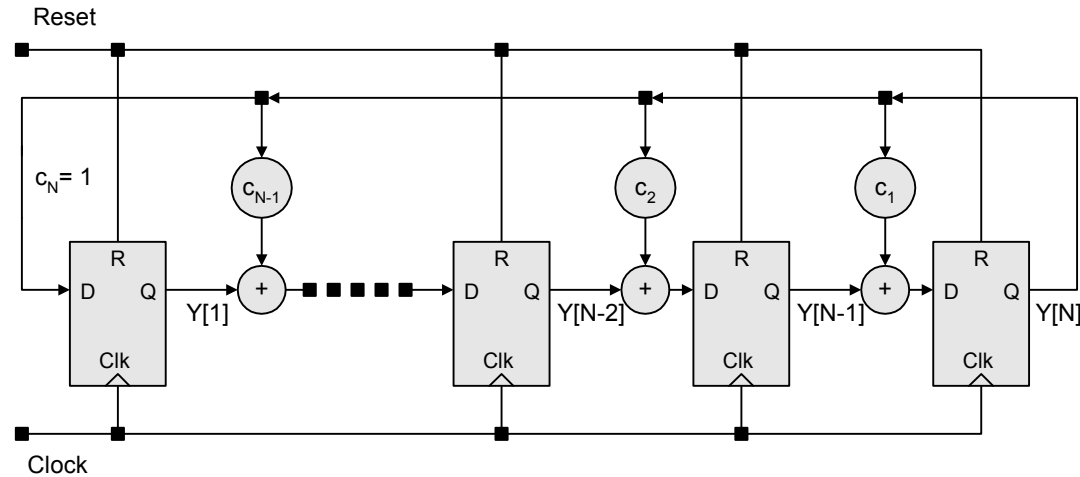


```

module Auto_LFSR_RTL (Y, Clock, Reset);
  parameter          Length = 8;
  parameter          initial_state = 8'b1001_0001; // 91h
  parameter [1: Length] Tap_Coefficient = 8'b_1111_1100;

  input              Clock, Reset;
  output [1: Length] Y;
  reg [1: Length] Y;

```

```
always @ (posedge Clock)  
if (!Reset) Y <= initial_state; // Active-low reset to initial state  
else begin  
    Y[1] <= Y[8];  
    Y[2] <= Tap_Coefficient[7] ? Y[1] ^ Y[8] : Y[1];  
    Y[3] <= Tap_Coefficient[6] ? Y[2] ^ Y[8] : Y[2];  
    Y[4] <= Tap_Coefficient[5] ? Y[3] ^ Y[8] : Y[3];  
    Y[5] <= Tap_Coefficient[4] ? Y[4] ^ Y[8] : Y[4];  
    Y[6] <= Tap_Coefficient[3] ? Y[5] ^ Y[8] : Y[5];  
    Y[7] <= Tap_Coefficient[2] ? Y[6] ^ Y[8] : Y[6];  
    Y[8] <= Tap_Coefficient[1] ? Y[7] ^ Y[8] : Y[7];  
  
end  
endmodule
```

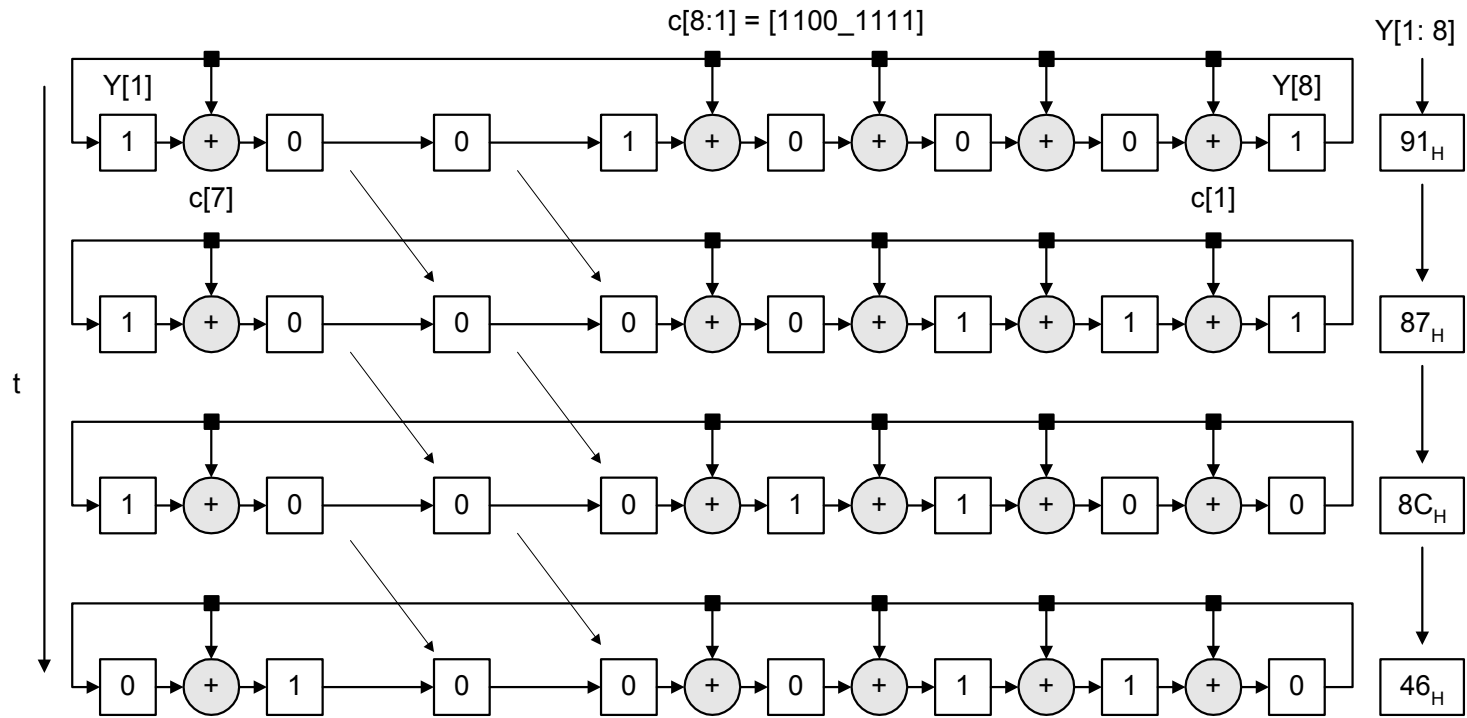

Example 5.27: LFSR (RTL – Algorithm)

```

module Auto_LFSR_ALGO (Y, Clock, Reset);
  parameter Length = 8;
  parameter initial_state = 8'b1001_0001;
  parameter [1: Length] Tap_Coefficient = 8'b1111_1100;
  input Clock, Reset;
  output [1: Length] Y;
  integer Cell_ptr;
  reg [1: Length] Y; // Redundant declaration for some compilers

  always @ (posedge Clock)
  begin
    if (Reset == 0) Y <= initial_state; // Arbitrary initial state, 91h
    else begin for (Cell_ptr = 2; Cell_ptr <= Length; Cell_ptr = Cell_ptr + 1)
      if (Tap_Coefficient [Length - Cell_ptr + 1] == 1)
        Y[Cell_ptr] <= Y[Cell_ptr - 1]^ Y [Length];
      else
        Y[Cell_ptr] <= Y[Cell_ptr - 1];
        Y[1] <= Y[Length];
      end
    end
  end
endmodule

```

Example 5.28: repeat Loop

```
...  
word_address = 0;  
repeat (memory_size)  
  begin  
    memory [ word_address ] = 0;  
    word_address = word_address + 1;  
  end  
...
```

Example 5.29: for Loop

```
reg [15: 0] demo_register;
integer K;
```

...

```
for (K = 4; K; K = K - 1)
begin
  demo_register [K + 10] = 0;
  demo_register [K + 2] = 1;
end
```

...


15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0
x	0	0	0	0	x	x	x	x	1	1	1	1	x	x	x

Example 5.30: Majority Circuit

```
module Majority_4b (Y, A, B, C, D);  
  input  A, B, C, D;  
  output Y;  
  reg    Y;  
  always @ (A or B or C or D) begin  
    case ({A, B, C, D})  
      7, 11, 13, 14, 15: Y = 1;  
      default           Y = 0;  
    endcase  
  end  
endmodule
```

```
module Majority (Y, Data);  
  parameter size = 8;  
  parameter max = 3;  
  parameter majority = 5;  
  input      [size-1: 0] Data;  
  output     Y;  
  reg        Y;  
  reg        [max-1: 0] count;  
  integer    k;
```

```
always @ (Data) begin  
  count = 0;  
  for (k = 0; k < size; k = k + 1) begin  
    if (Data[k] == 1) count = count + 1;  
  end  
  Y = (count >= majority);  
end  
endmodule
```

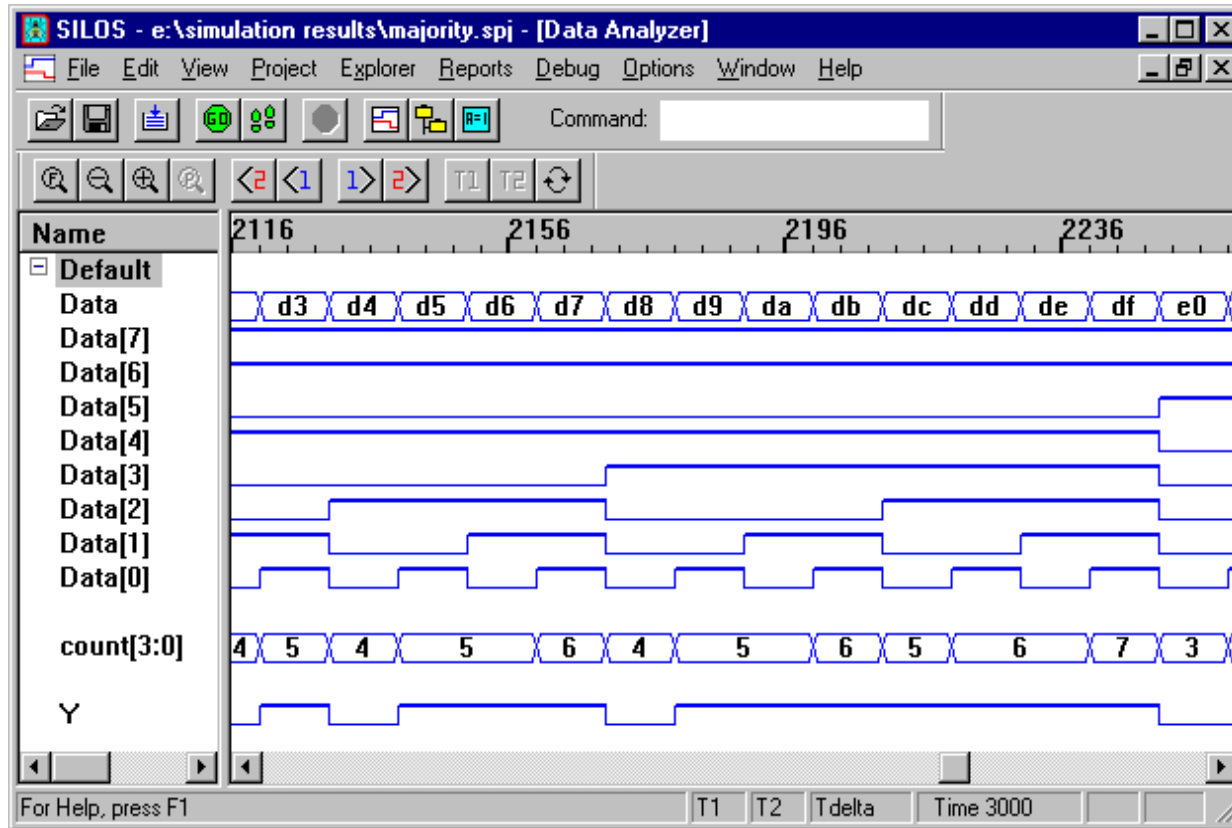

Example 5.31 Parameterized Model of LFSR

```
module Auto_LFSR_Param (Y, Clock, Reset);
  parameter          Length = 8;
  parameter          initial_state = 8'b1001_0001; // Arbitrary initial state
  parameter [1: Length] Tap_Coefficient = 8'b1111_1100;

  input              Clock, Reset;
  output [1: Length] Y;
  reg   [1: Length] Y;
  integer          k;

  always @ (posedge Clock)
    if (!Reset) Y <= initial_state;
    else begin
      for (k = 2; k <= Length; k = k + 1)
        Y[k] <= Tap_Coefficient[Length-k+1] ? Y[k-1] ^ Y[Length] : Y[k-1];
      Y[1] <= Y[Length];
    end
endmodule
```

Example 5.32: Ones Counter

```
begin: count_of_1s      // count_of_1s declares a named block of statements
  reg [7: 0] temp_reg;

  count = 0;
  temp_reg = reg_a; // load a data word
  while (temp_reg)
    begin
      if (temp_reg[0]) count = count + 1;
      temp_reg = temp_reg >> 1;
    end
  end
```

Alternative Description:

```
begin: count_of_1s  
  reg [7: 0] temp_reg;  
  
  count = 0;  
  temp_reg = reg_a; // load a data word  
  while (temp_reg)  
    begin  
      count = count + temp_reg[0];  
      temp_reg = temp_reg >> 1;  
    end  
  end
```

Note: Verilog 2001 includes arithmetic shift operators (See Appendix I)



Example 5.32: Clock Generator

```
parameter half_cycle = 50;
```

```
initial
```

```
begin: clock_loop // Note: clock_loop is a named block of statements
```

```
  clock = 0;
```

```
  forever
```

```
    begin
```

```
      #half_cycle clock = 1;
```



```
      #half_cycle clock = 0;
```

```
    end
```

```
  end
```

```
initial
```

```
  #350 disable clock_loop;
```

  

Example 5.34

```
module find_first_one (index_value, A_word, trigger);  
  output [3: 0]    index_value;  
  input  [15: 0]   A_word;  
  input          trigger;  
  reg    [3: 0]    index_value;  
  
  always @ (trigger)  
  begin: search_for_1  
    index_value = 0;  
    for (index_value = 0; index_value < 15; index_value = index_value + 1)  
      if (A_word[index_value] == 1) disable search_for_1;  
  end  
endmodule
```


Example 5.35: Multi-Cycle Operations (4-Cycle Adder)

```

module add_4cycle (sum, data, clk, reset);
  output      [5: 0]    sum;
  input       [3: 0]    data;
  input       clk, reset;
  reg         [5: 0]    sum;    // Redundant for some compilers

  always @ (posedge clk) begin: add_loop
    if (reset) disable add_loop;           else sum <= data;
    @ (posedge clk) if (reset) disable add_loop; else sum <= sum + data;
    @ (posedge clk) if (reset) disable add_loop; else sum <= sum + data;
    @ (posedge clk) if (reset) disable add_loop; else sum <= sum + data;
  end
endmodule

```

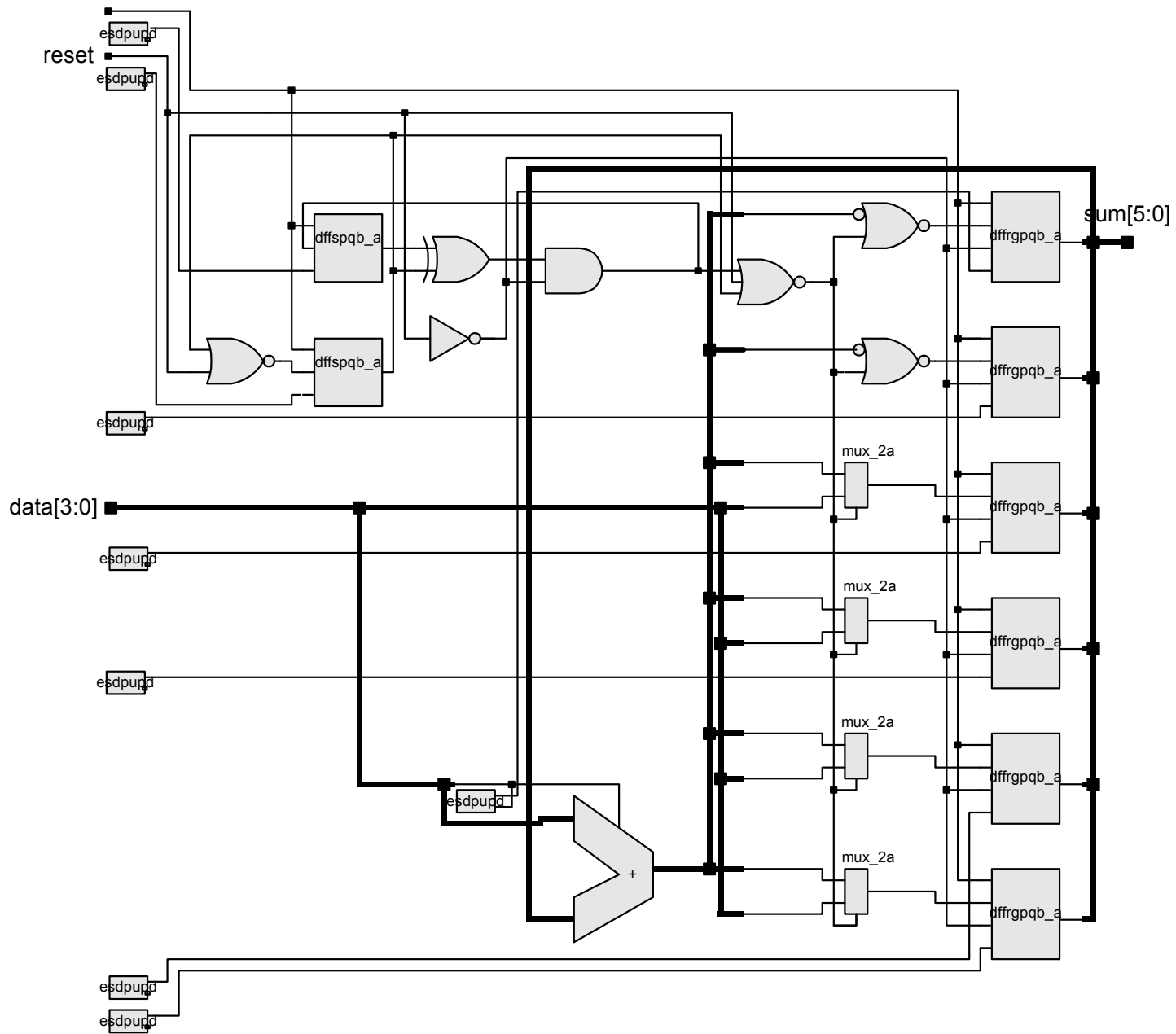


Example 5.36: Task (Adder)

```
module adder_task (c_out, sum, clk, reset, c_in, data_a, data_b, clk);
  output      [3: 0]    sum;
  output      c_out;
  input       [3: 0]    data_a, data_b;
  input       clk, reset;
  input       c_in;

  reg         [3: 0]    sum; // Redundant for some compilers
  reg         c_out;
  reg         [3: 0]    acc;

  always @ (posedge clk or posedge reset)
    if (reset) {c_out, sum} <= 0; else
      add_values (c_out, sum, data_a, data_b, c_in);
```

```
task add_values;  
  output          c_out;  
  output    [3: 0] sum;  
  input      [3: 0] data_a, data_b;  
  input      c_in;  
  
  reg          sum;  
  reg          c_out;  
  
  begin  
    {c_out, sum} <= data_a + (data_b + c_in);  
  end  
endtask  
endmodule
```

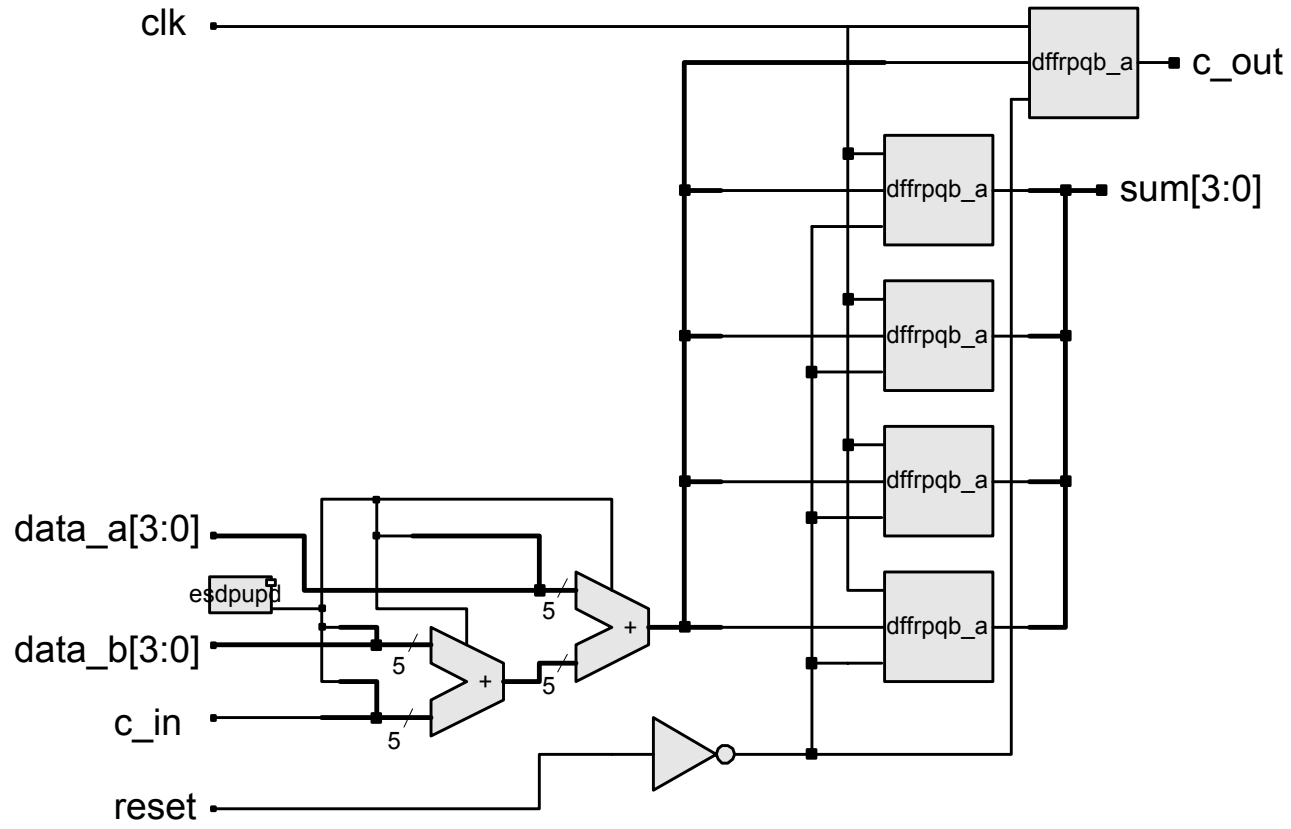

Example 5.37: Function (Word Aligner)



```
module word_aligner (word_out, word_in);
  output      [7: 0]    word_out;
  input       [7: 0]    word_in;

  assign word_out = aligned_word(word_in);

  function    [7: 0]    aligned_word;
  input      [7: 0]    word_in;
  begin
    aligned_word = word_in;
    if (aligned_word != 0)
      while (aligned_word[7] == 0) aligned_word = aligned_word << 1;
    end
  endfunction
endmodule
```

Example 5.38: Arithmetic Unit

```
module arithmetic_unit (result_1, result_2, operand_1, operand_2);  
  
  output      [4: 0] result_1;  
  output      [3: 0] result_2;  
  input       [3: 0] operand_1, operand_2;  
  
  assign result_1 = sum_of_operands (operand_1, operand_2);  
  assign result_2 = largest_operand (operand_1, operand_2);  
  
  function [4: 0] sum_of_operands;  
    input [3: 0] operand_1, operand_2;  
  
    sum_of_operands = operand_1 + operand_2;  
  endfunction  
  
  function [3: 0] largest_operand;  
    input [3: 0] operand_1, operand_2;  
  
    largest_operand = (operand_1 >= operand_2) ? operand_1 : operand_2;  
  endfunction  
endmodule
```

  
[1]

operand_2[3:0]


Algorithmic State Machine (ASM) Chart

- STGs do not directly display the evolution of states resulting from an input
- ASM charts reveal the sequential steps of a machine's activity
- Focus on machine's activity, rather than contents of registers
- ASM chart elements
 1. state box
 2. decision box
 3. conditional box
- Clock governs transitions between states
- Linked ASM charts describe complex machines
- ASM charts represent Mealy and Moore machines


ASM Charts (Cont.)

 


State Box

 

 
Conditional Output or Register Operation Box



Decision Box

 


Example 5.39 Tail Light Controller

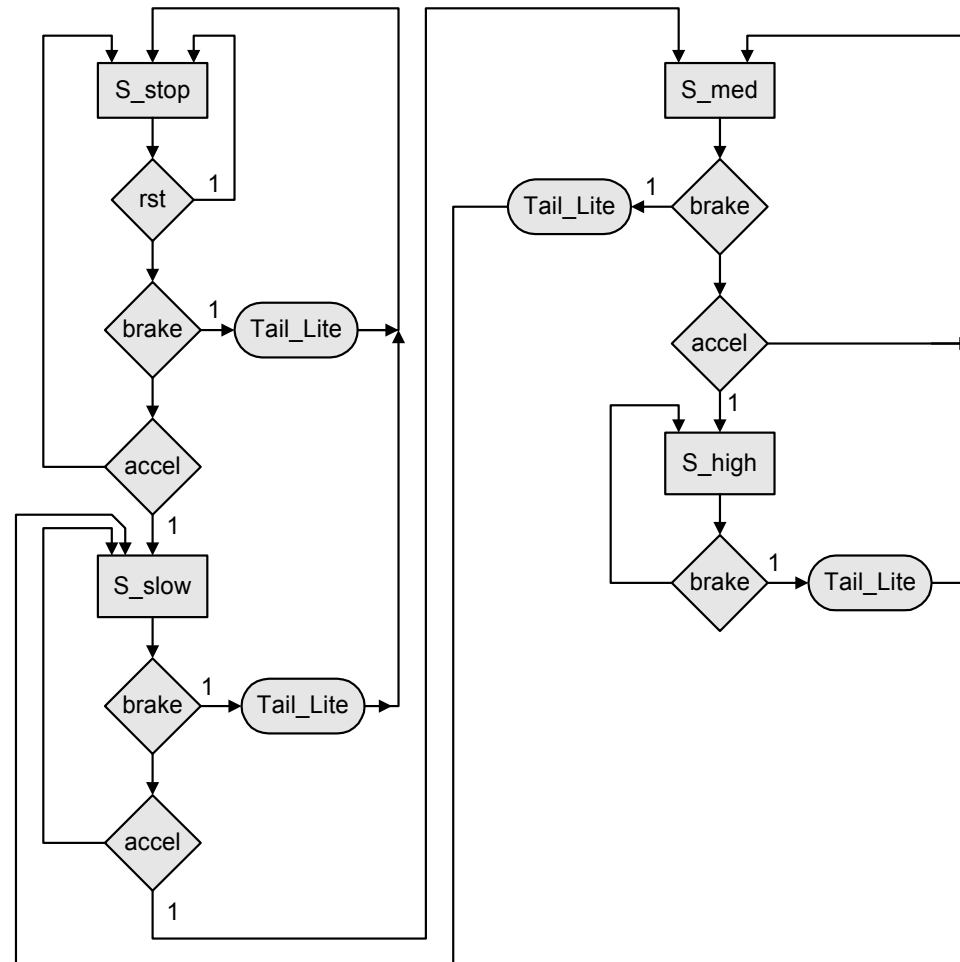


ASMD Chart

- Form an ASMD (Algorithmic State Machine and datapath) chart by annotating each of its paths to indicate the concurrent register operations that occur in the associated datapath unit when the state of the controller makes a transition along the path
- Clarify a design of a sequential machine by separating the design of its datapath from the design of the controller
- ASMD chart maintains a clear relationship between a datapath and its controller
- Annotate path with concurrent register operations
- Outputs of the controller control the datapath

Example 5.39 Two-Stage Pipeline

 

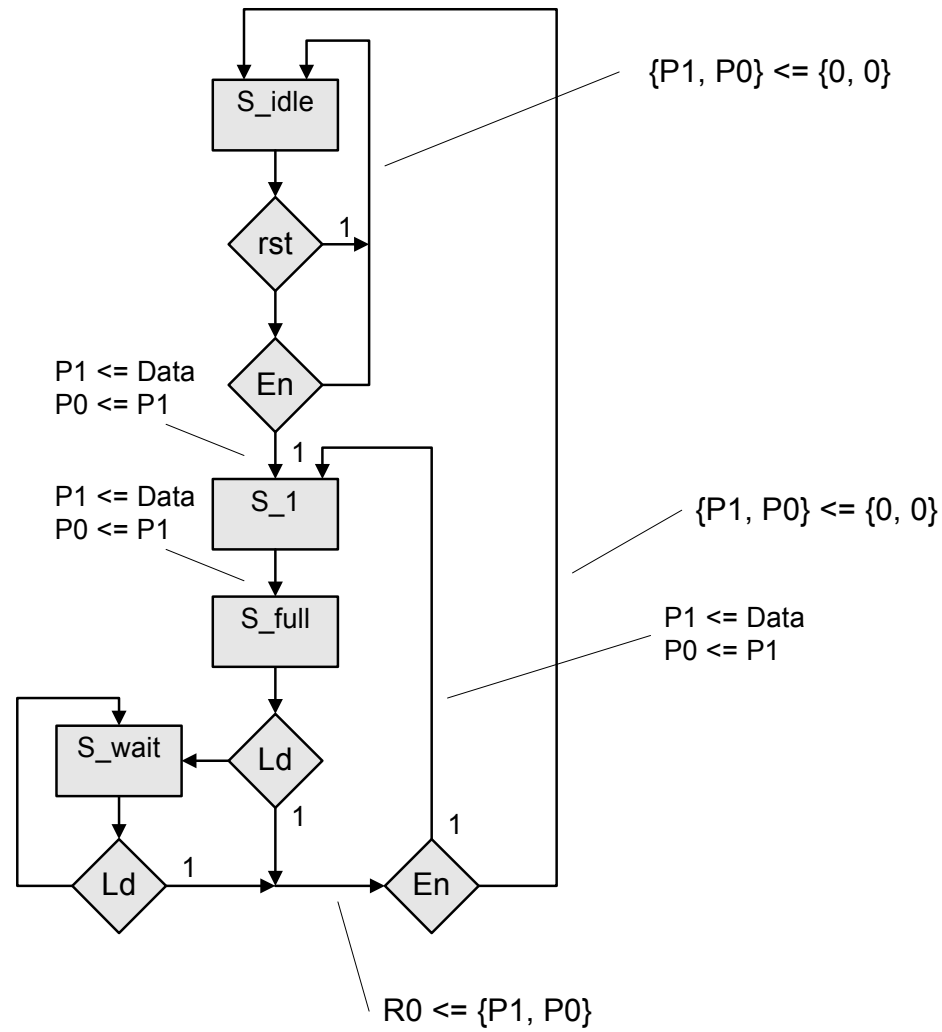



See Problem 24

Datapath Controller Design



- Specify register operations for the datapath
- Define the ASM chart of the controller (PI and feedback from datapath)
- Annotate the arcs of the ASM chart with the datapath operations associated with the state transitions of the controller
- Annotate the state of the controller with unconditional output signals
- Include conditional boxes for the signals generated by the controller to control the datapath.
- Verify the controller
- Verify the datapath
- Verify the integrated units

Example 5.40 Counters

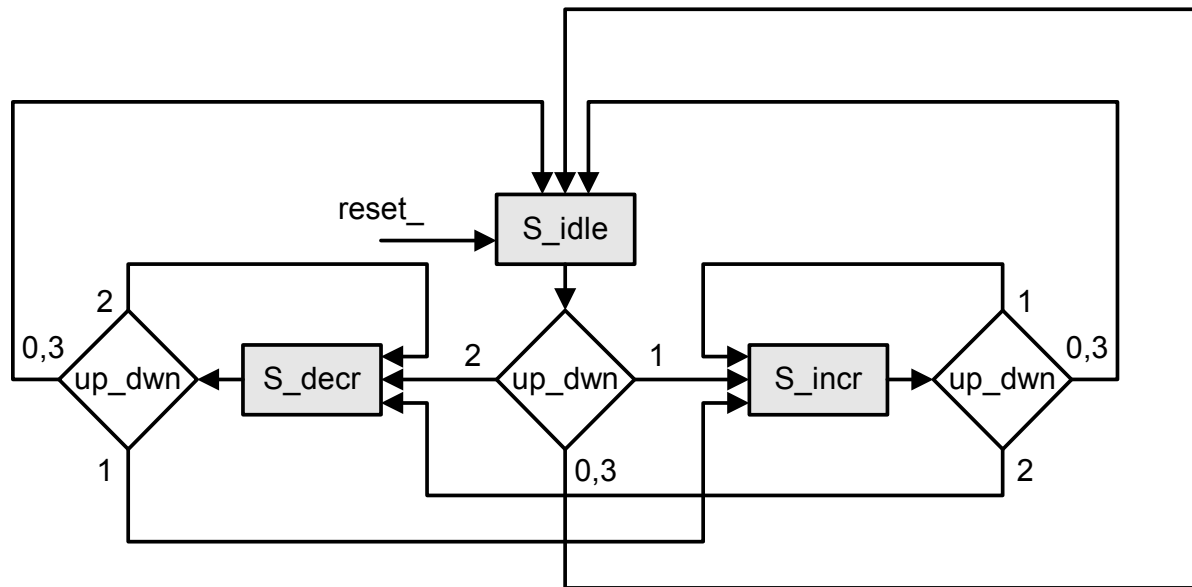


 


2
0,3
up.
1

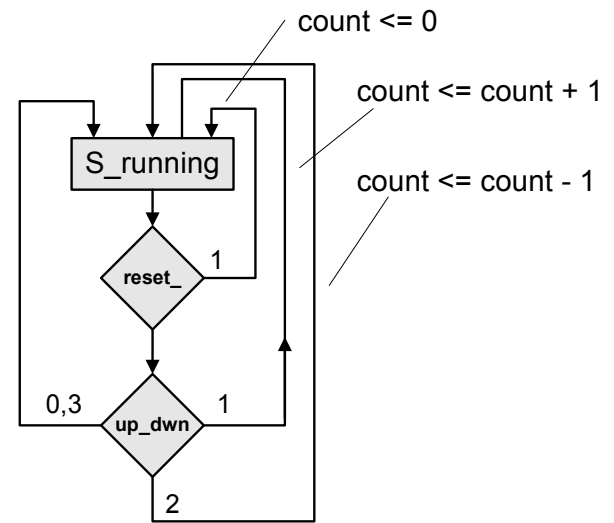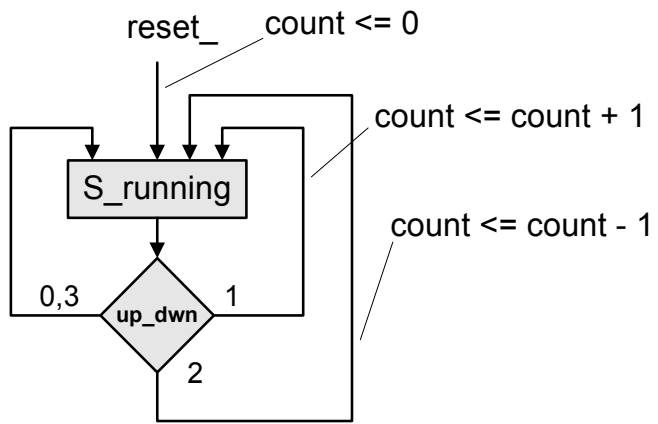

```
module Up_Down_Implicit1 (count, up_dwn, clock, reset_);  
  output [2: 0]    count;  
  input   [1: 0]    up_dwn;  
  input    clock, reset_;  
  
  reg [2: 0] count;  
  
  always @ (negedge clock or negedge reset_)  
    if (reset_ == 1)          count <= 3'b0; else  
      if (up_dwn == 2'b00 || up_dwn == 2'b11) count <= count; else  
        if (up_dwn == 2'b01)          count <= count + 1; else  
          if (up_dwn == 2'b10)          count <= count -1;  
  
endmodule
```

 

Example 5.41 Ring Counter

 


```

module ring_counter (count, enable, clock, reset);
  output      [7: 0]    count;
  input      enable, reset, clock;
  reg        [7: 0]    count;


  always @ (posedge reset or posedge clock)
    if (reset == 1'b1) count <= 8'b0000_0001; else
      if (enable == 1'b1) count <= {count[6: 0], count[7]};
      // Concatenation operator
endmodule


```

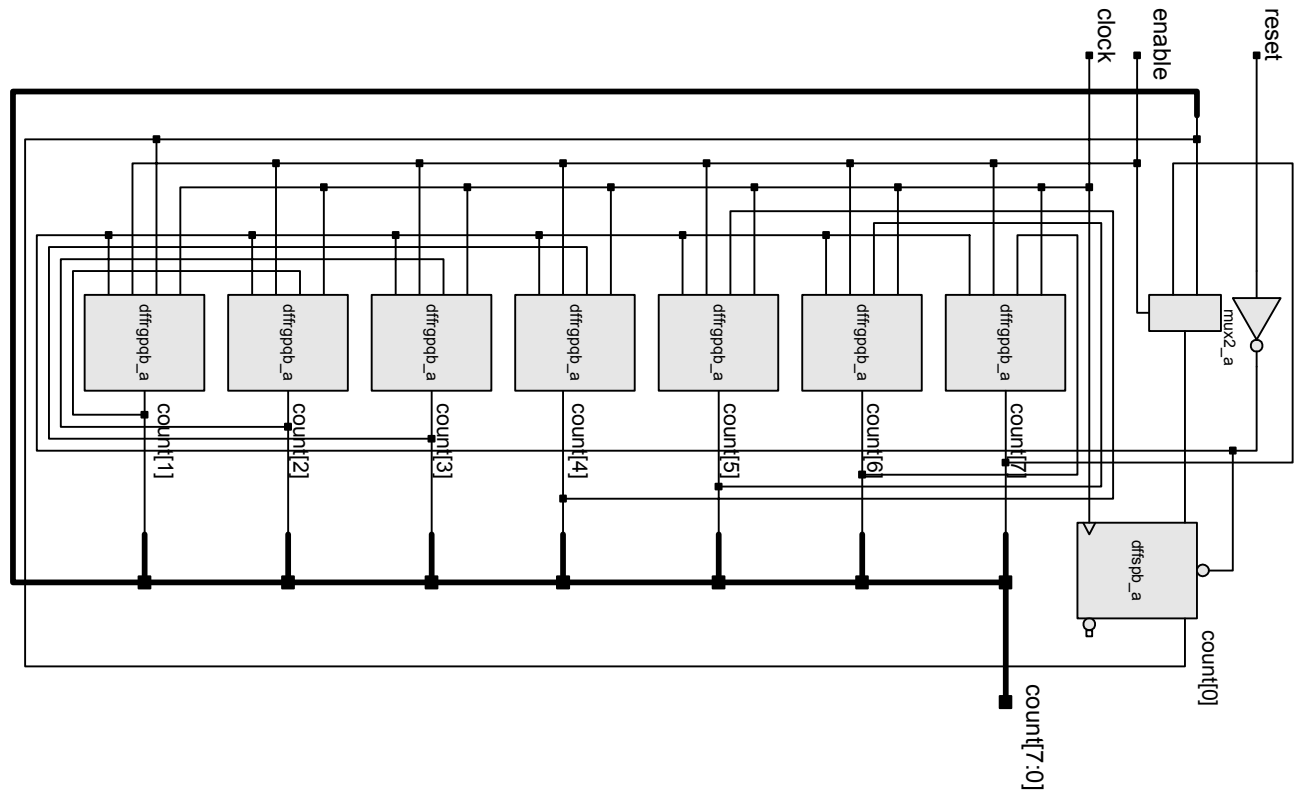

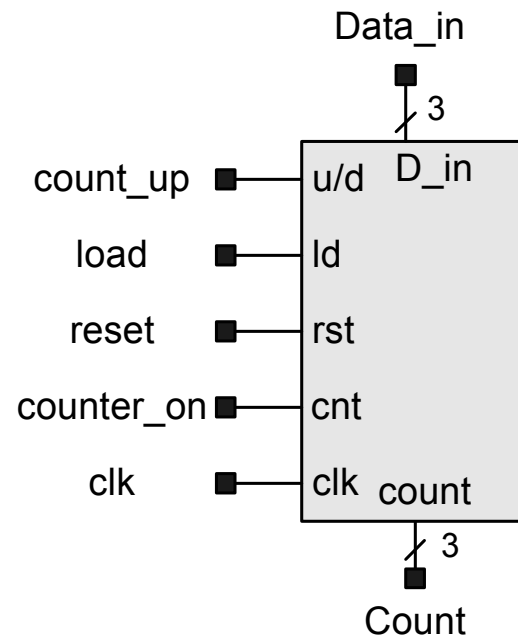Example 5.423-Bit Up_Down Counter

```
module up_down_counter (Count, Data_in, load, count_up, counter_on, clk, reset);  
  output      [2: 0]    Count;  
  input       load, count_up, counter_on, clk, reset,;  
  input       [2: 0]    Data_in;  
  reg         [2: 0]    Count;  
  
  always @ (posedge reset or posedge clk)  
    if (reset == 1'b1) Count = 3'b0; else  
      if (load == 1'b1) Count = Data_in; else  
        if (counter_on == 1'b1) begin  
          if (count_up == 1'b1) Count = Count +1;  
          else Count = Count -1;  
        end  
endmodule
```



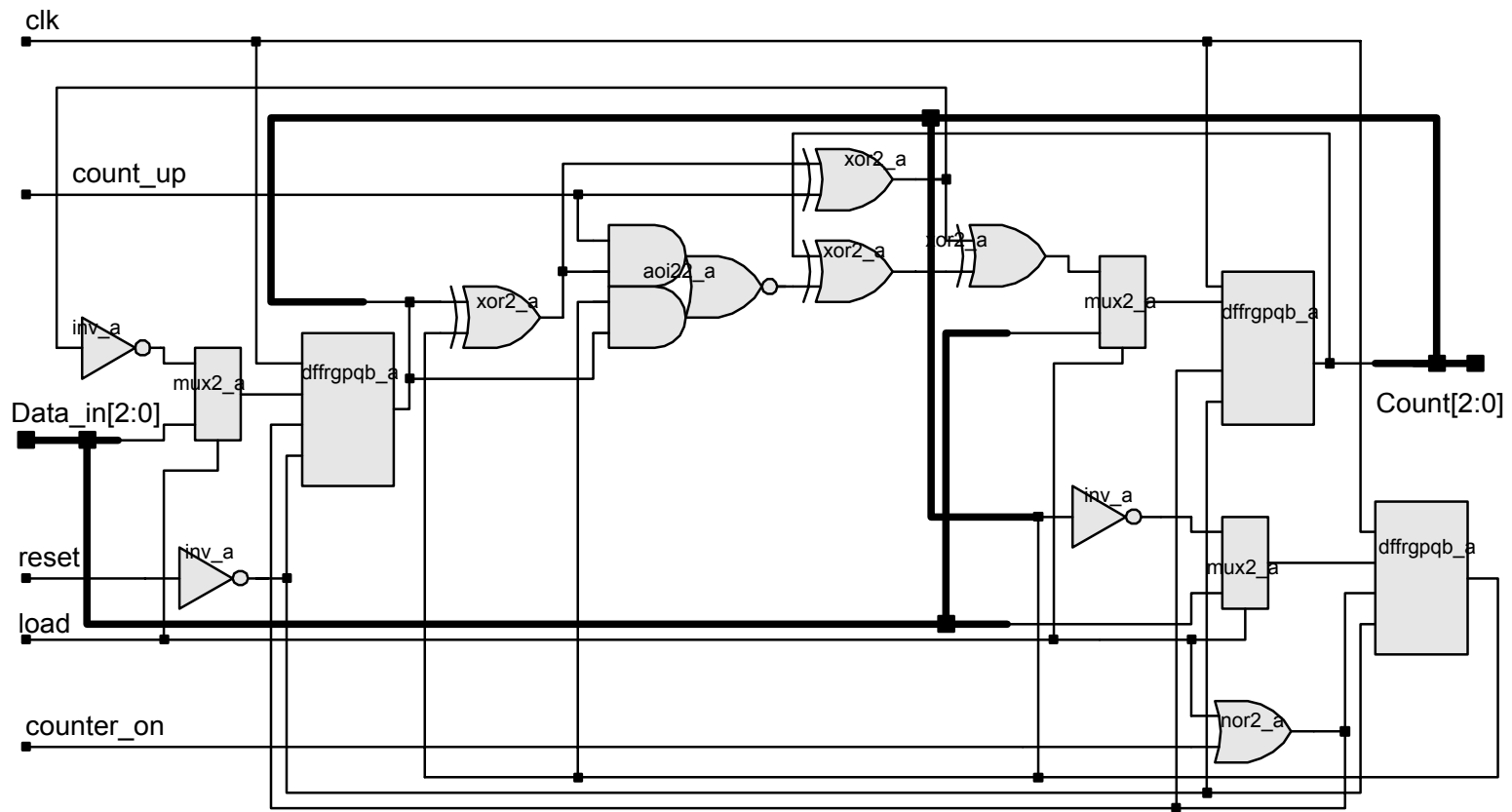

See Appendix H for Flip-Flop types



Example 5.43: Shift Register

```
module Shift_reg4 (Data_out, Data_in, clock, reset);
  output          Data_out;
  input           Data_in, clock, reset;
  reg [3: 0]      Data_reg;

  assign Data_out = Data_reg[0];

  always @ (negedge reset or posedge clock)
  begin
    if (reset == 1'b0)      Data_reg <= 4'b0;
    else                    Data_reg <= {Data_in, Data_reg[3:1]};
  end
endmodule
```

Synthesis Result:

 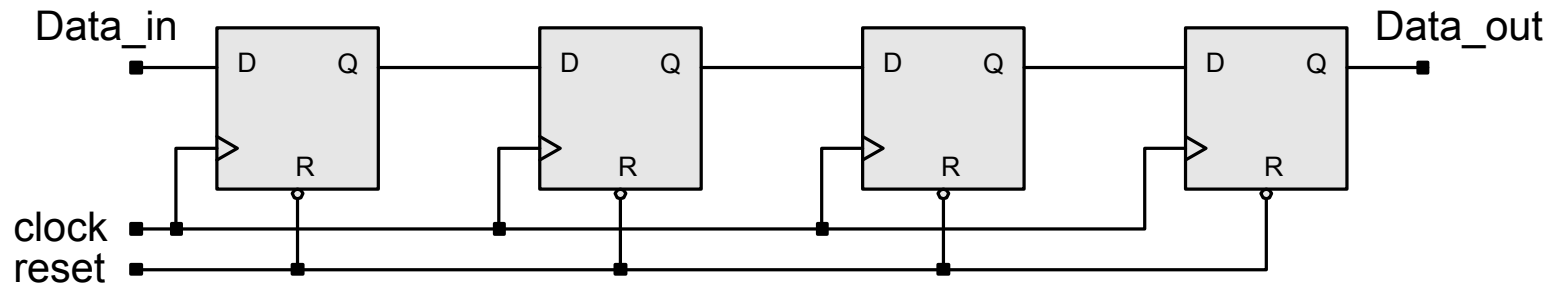


Example 5.44 Parallel Load Shift Register


```
module Par_load_reg4 (Data_out, Data_in, load, clock, reset);
  input  [3: 0]    Data_in;
  input          load, clock, reset;
  output [3: 0]    Data_out;    // Port size
  reg        Data_out;        // Data type


  always @ (posedge reset or posedge clock)
  begin
    if (reset == 1'b1)        Data_out <= 4'b0;
    else if (load == 1'b1) Data_out <= Data_in;
  end
endmodule
```

Synthesis Result

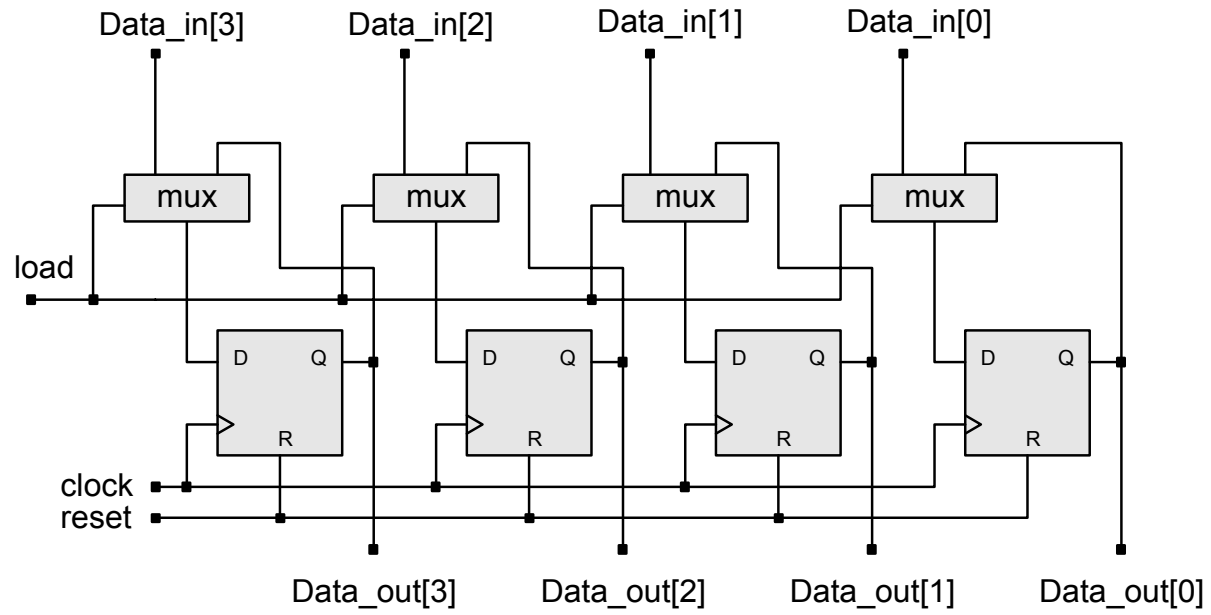


Example 5.45: Barrel Shifter

 


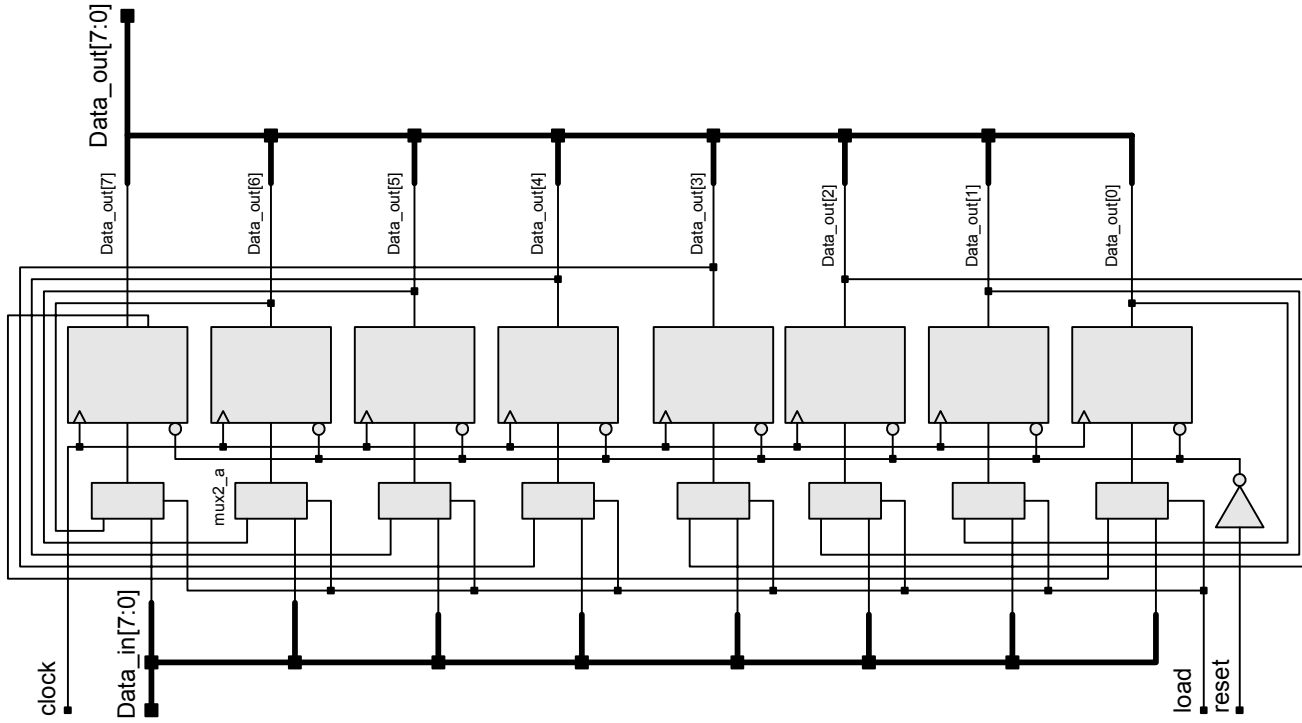

```
module barrel_shifter (Data_out, Data_in, load, clock, reset);  
  output [7: 0] Data_out;  
  input [7: 0] Data_in;  
  input load, clock, reset;  
  reg [7: 0] Data_out;  
  
  always @ (posedge reset or posedge clock)  
  begin  
    if (reset == 1'b1) Data_out <= 8'b0;  
    else if (load == 1'b1) Data_out <= Data_in;  
    else Data_out <= {Data_out[6: 0], Data_out[7]};  
  end  
endmodule
```

 

Example 5.46: Universal Shift Register

 


```
module Universal_Shift_Reg
  (Data_Out, MSB_Out, LSB_Out, Data_In, MSB_In, LSB_In, s1, s0, clk, rst);
output [3: 0] Data_Out;
output MSB_Out, LSB_Out;
input [3: 0] Data_In;
input MSB_In, LSB_In;
input s1, s0, clk, rst;
reg [3: 0] Data_Out;


assign MSB_Out = Data_Out[3];
assign LSB_Out = Data_Out[0];

always @ (posedge clk) begin
  if (rst) Data_Out <= 0;
  else case ({s1, s0})
    0: Data_Out <= Data_Out; // Hold
    1: Data_Out <= {MSB_In, Data_Out[3:1]}; // Serial shift from MSB
    2: Data_Out <= {Data_Out[2: 0], LSB_In}; // Serial shift from LSB
    3: Data_Out <= Data_In; // Parallel Load
  endcase
end
endmodule
```

Simulation Results:

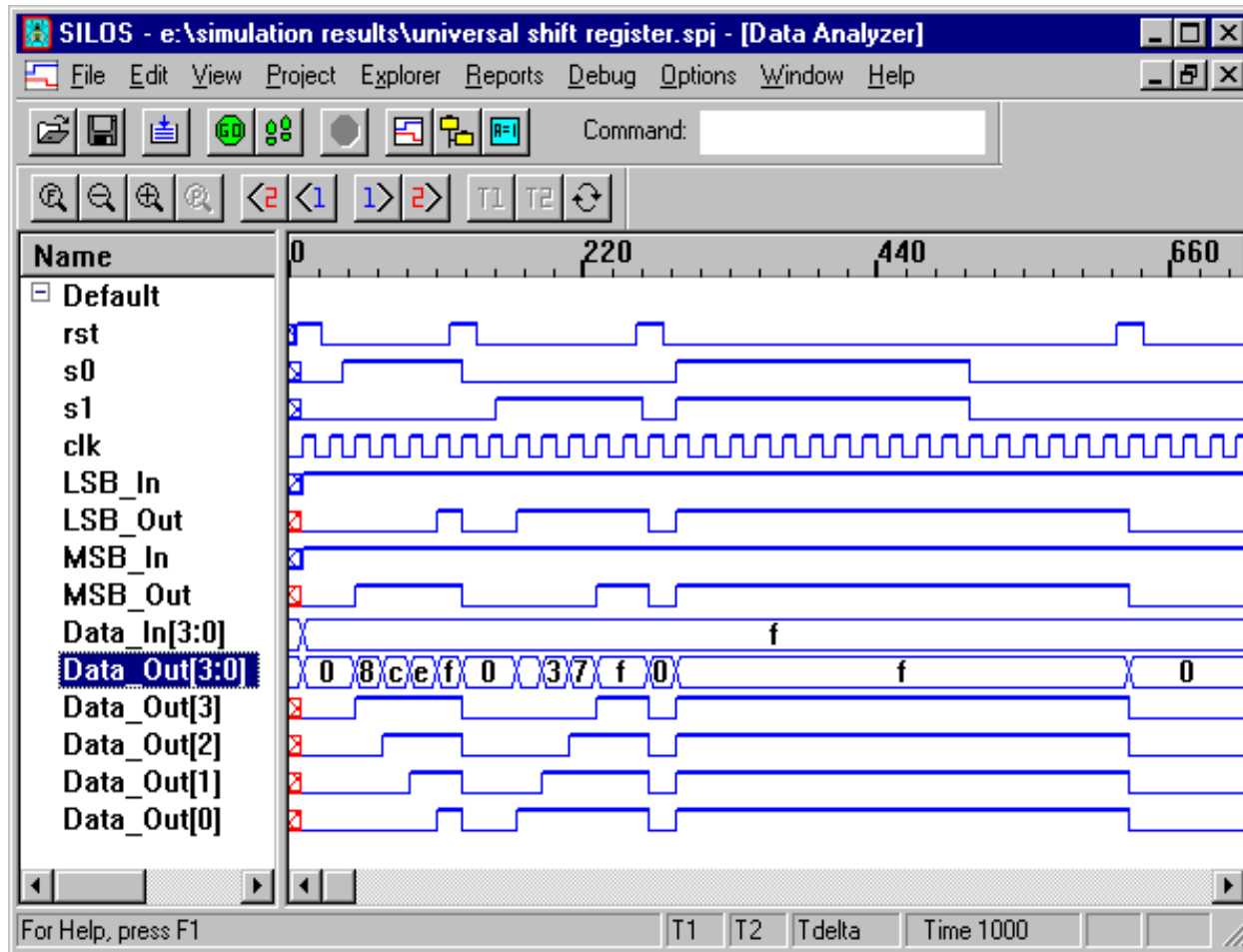

Example 5.47: Register File

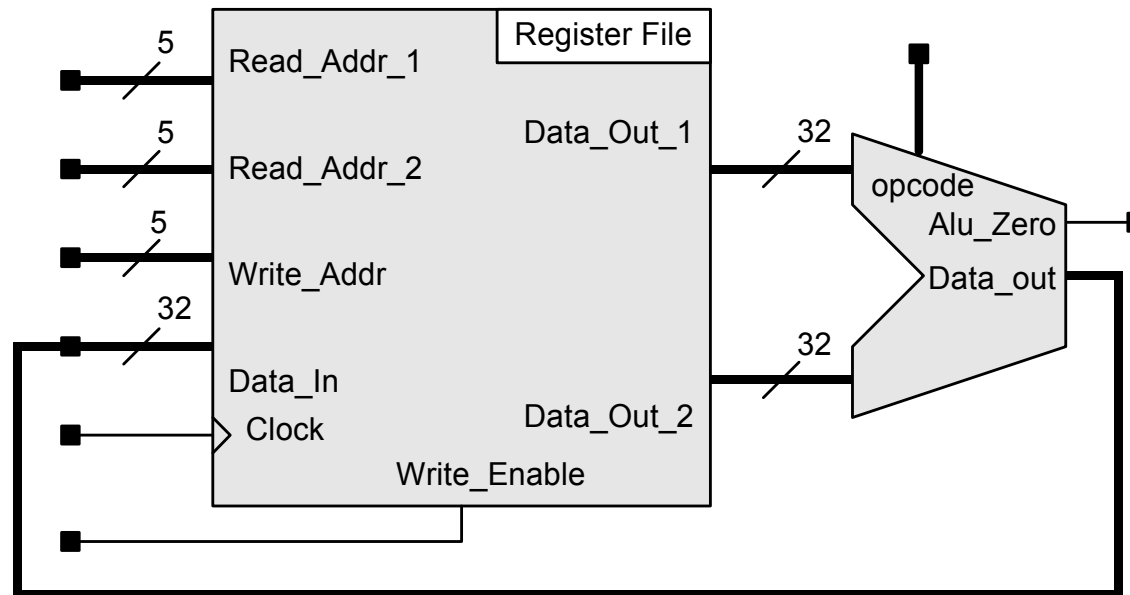


```

module Register_File (Data_Out_1, Data_Out_2, Data_in, Read_Addr_1, Read_Addr_2,
Write_Addr, Write_Enable, Clock);
output [31: 0] Data_Out_1, Data_Out_2;
input [31: 0] Data_in;
input [4: 0] Read_Addr_1, Read_Addr_2, Write_Addr;


```
 
```
input          Write_Enable, Clock;  
reg    [31: 0]  Reg_File [31: 0];    // 32bit x32 word memory declaration  
  
assign Data_Out_1 = Reg_File[Read_Addr_1];  
assign Data_Out_2 = Reg_File[Read_Addr_2];  
  
always @ (posedge Clock) begin  
  if (Write_Enable) Reg_File [Write_Addr] <= Data_in;  
end  
endmodule
```




Metastability and Synchronizers


Push-button device with closure bounce:

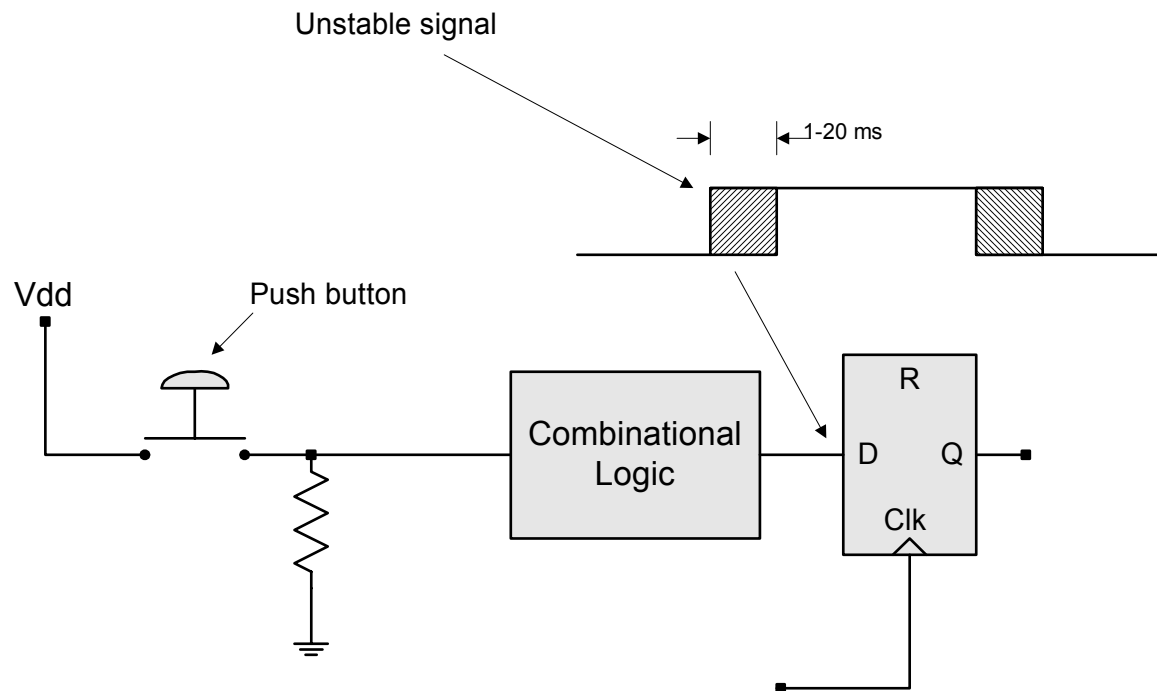


Nand latch Circuit

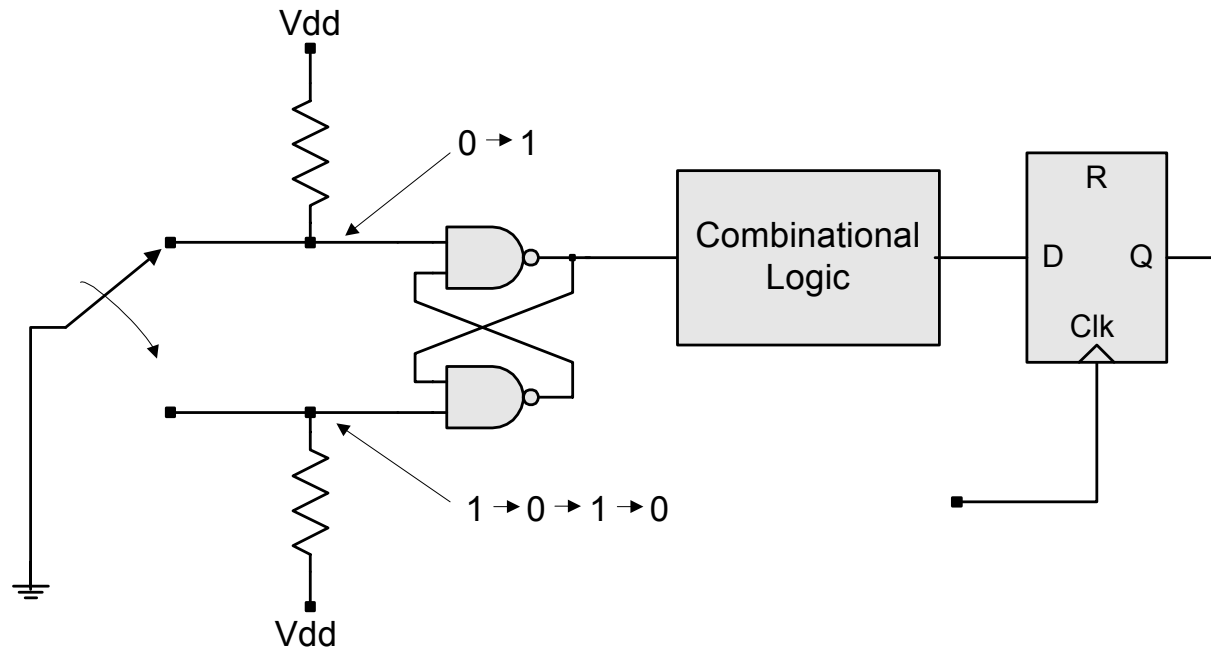


Metastability:

 

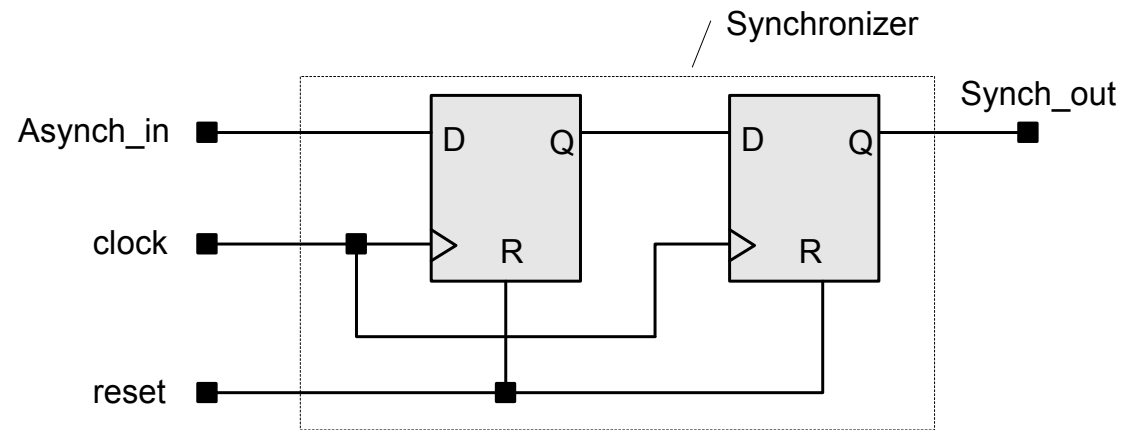
Synchronizer for relatively long asynchronous input pulse:



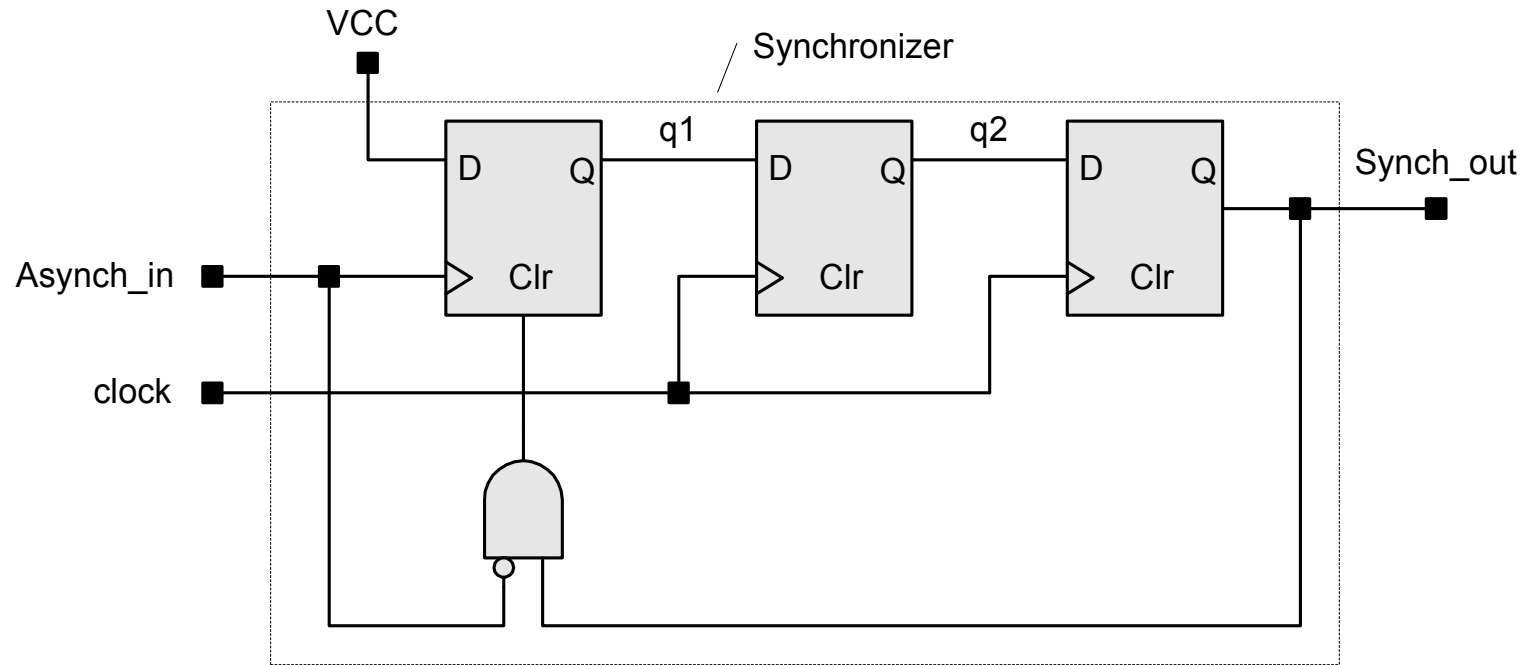
Synchronizer for relatively short asynchronous input pulse:



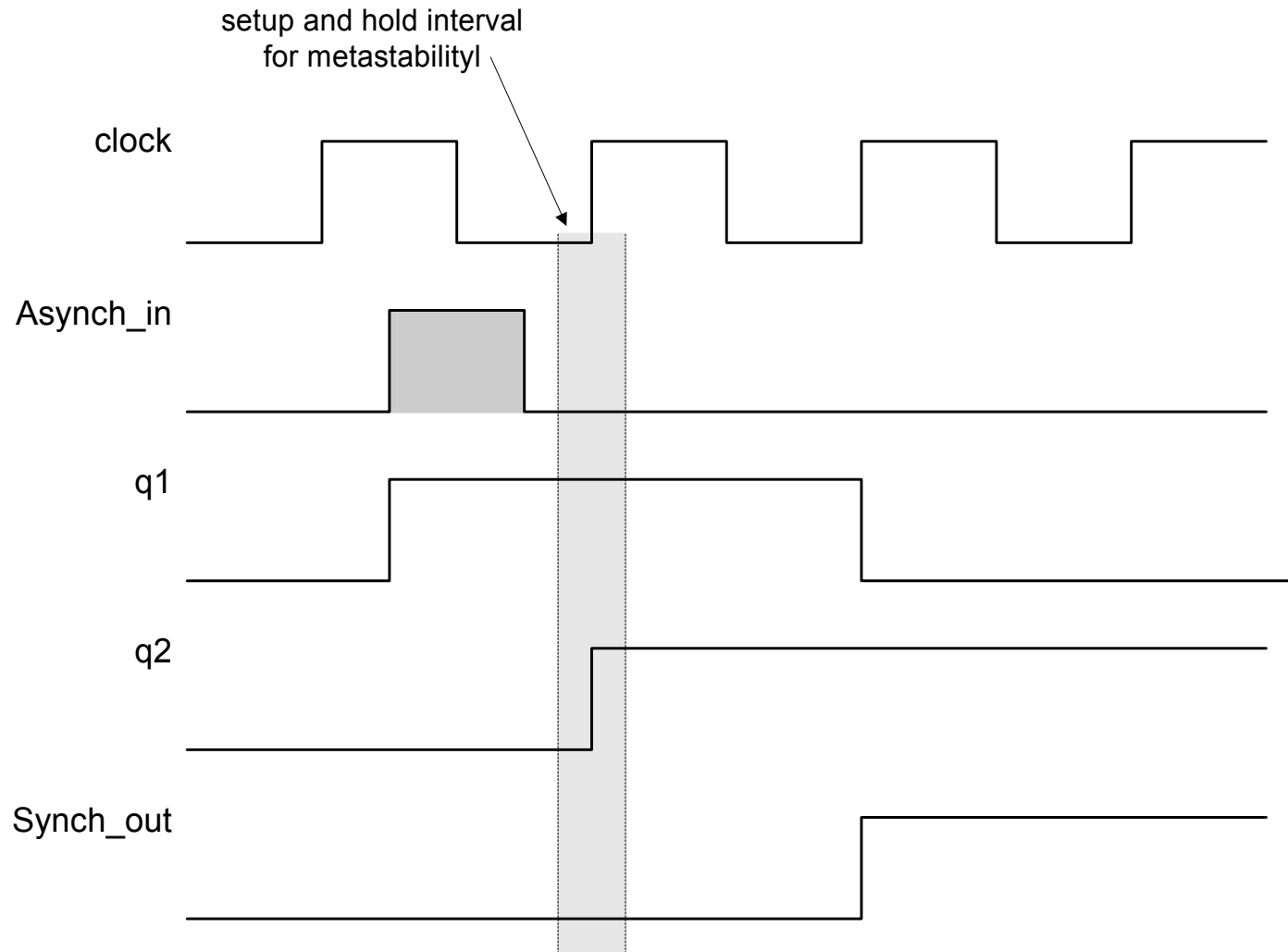
Waveforms without metastability condition:




Waveforms with metastability condition

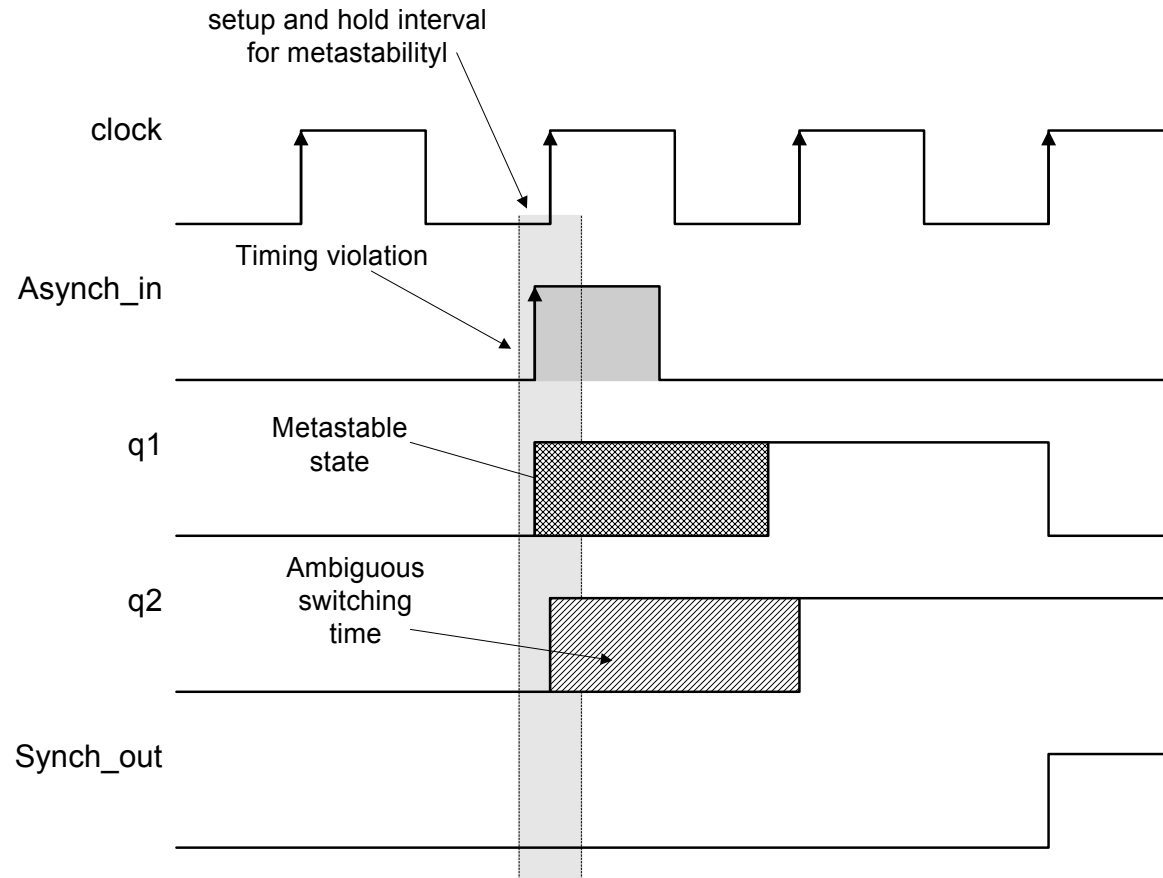

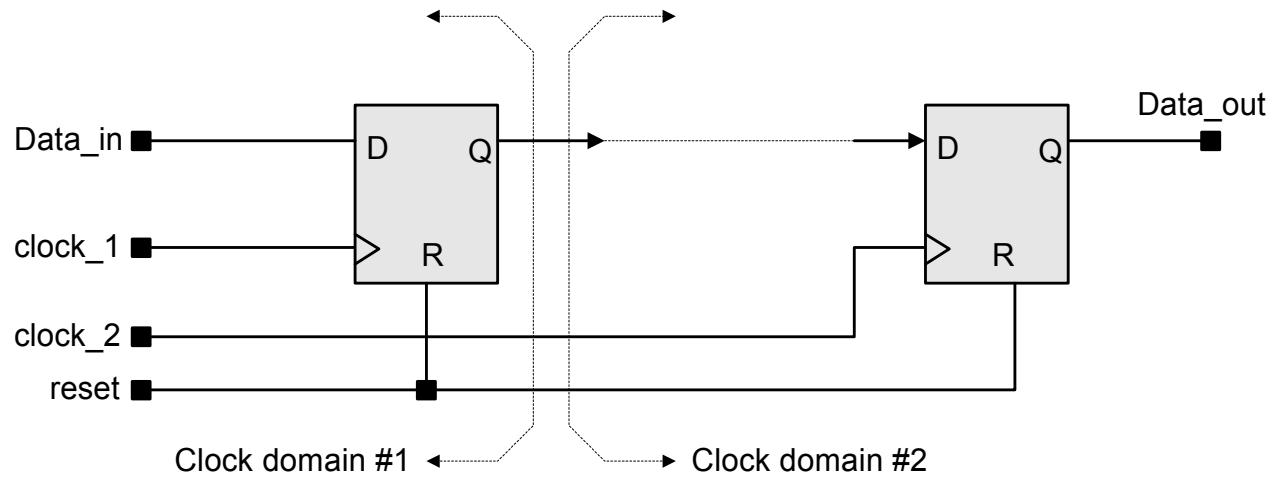Synchronization across clock domains (more later)




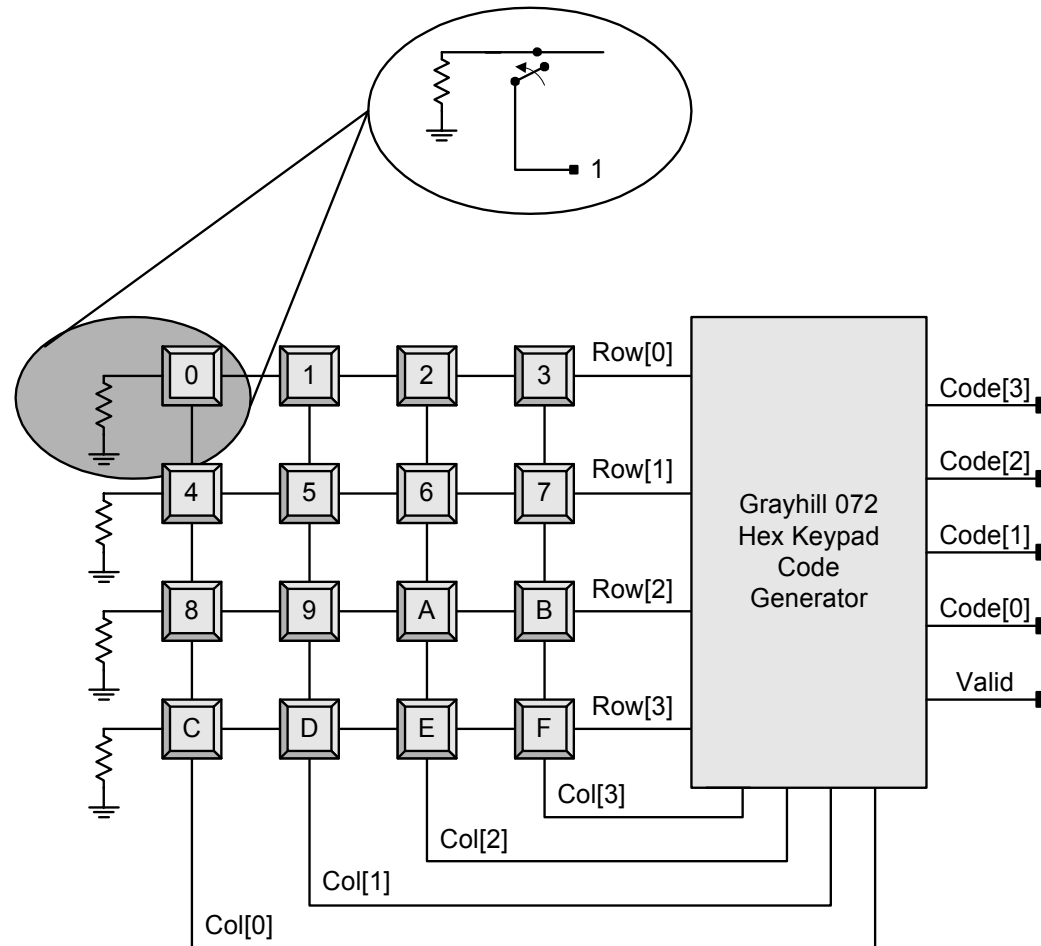Design Example: Keypad Scanner and Encoder (p 216)




Keypad Codes

Key	Row[3:0]	Col[3:0]	Code
0	0001	0001	0000
1	0001	0010	0001
2	0001	0100	0010
3	0001	1000	0011
4	0010	0001	0100
5	0010	0010	0101
6	0010	0100	0110
7	0010	1000	0111
8	0100	0001	1000
9	0100	0010	1001
A	0100	0100	1010
B	0100	1000	1011
C	1000	0001	1100
D	1000	0010	1101
E	1000	0100	1110
F	1000	1000	1111

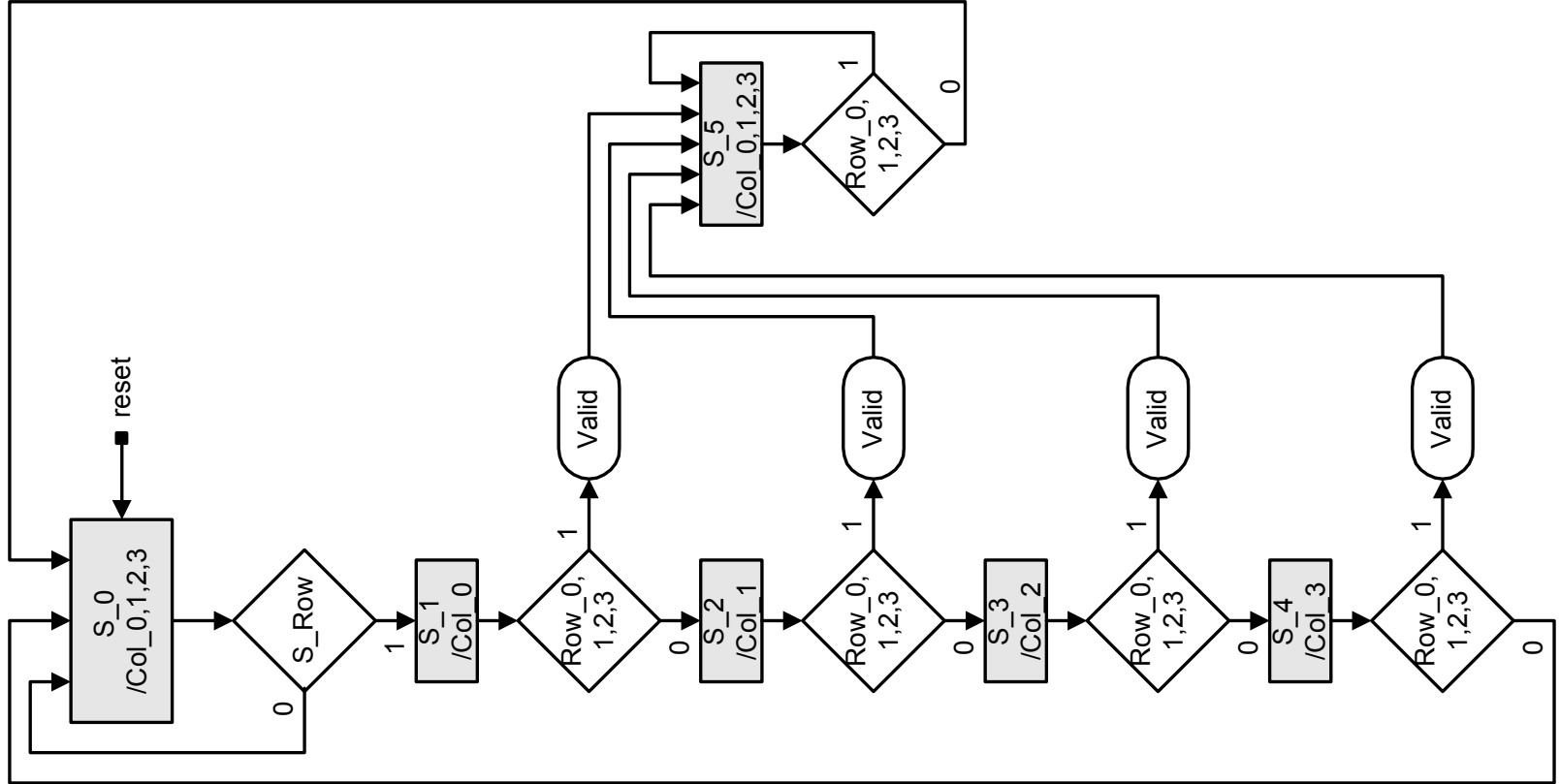

Test bench for Hex_Keypad_Grayhill_072

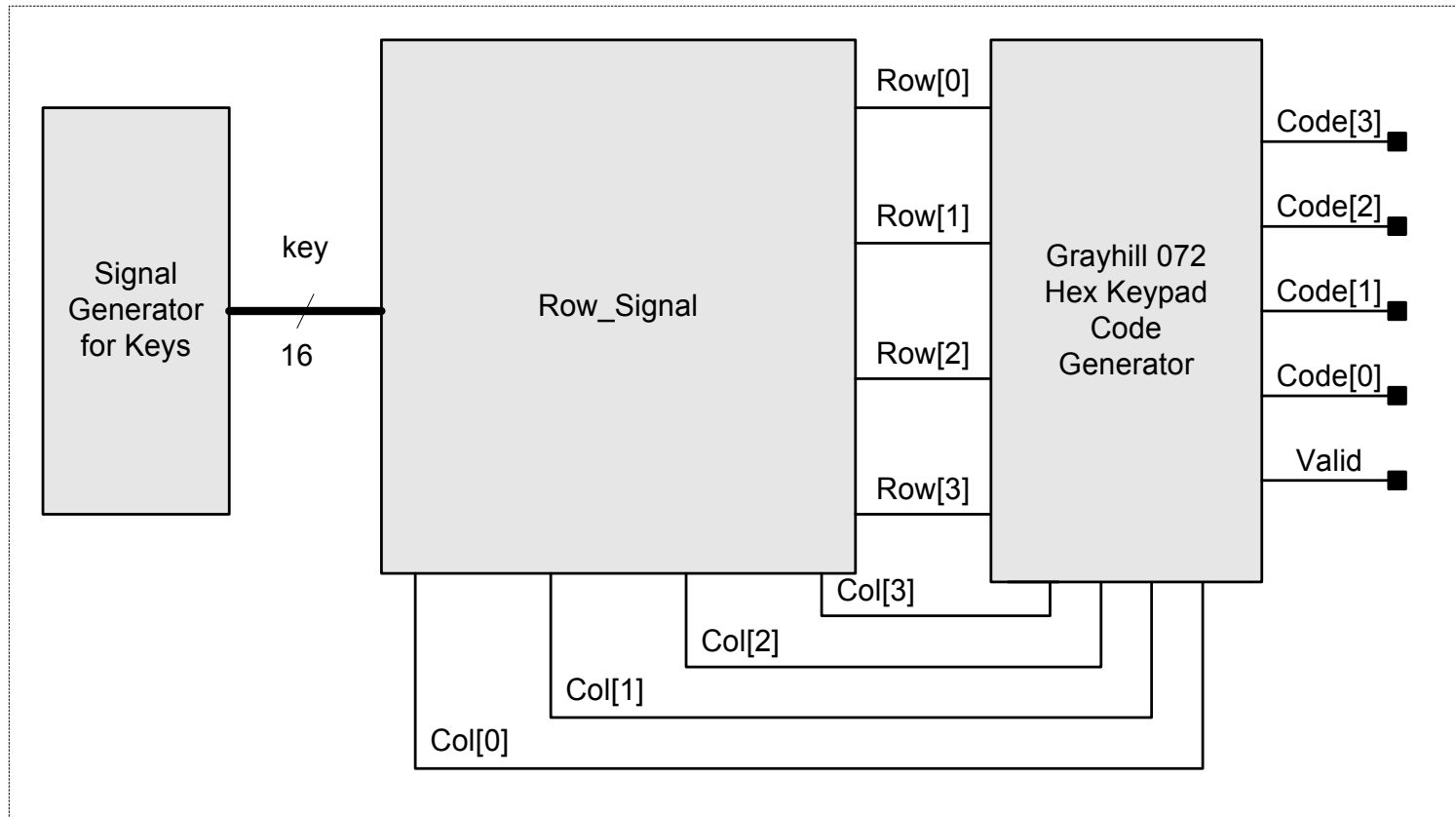

```
// Decode the asserted Row and Col
```

```
// Grayhill 072 Hex Keypad
```

```
//
```

```
//          Co[0]    Col[1]    Col[2]    Col[3]
// Row [0]  0       1         2         3
// Row [1]  4       5         6         7
// Row [2]  8       9         A         B
// Row [3]  C       D         E         F
```

```
module Hex_Keypad_Grayhill_072 (Code, Col, Valid, Row, S_Row, clock, reset);
```

```
  output [3: 0]    Code;
```

```
  output          Valid;
```

```
  output [3: 0]    Col;
```

```
  input  [3: 0]    Row;
```

```
  input          S_Row;
```

```
  input          clock, reset;
```

```
  reg    [3: 0]    Col, Code;
```

```
  reg          state;
```

```
  reg    [5: 0]    state, next_state;
```

```
// One-hot state codes
parameter S_0 = 6'b000001, S_1 = 6'b000010, S_2 = 6'b000100;
parameter S_3 = 6'b001000, S_4 = 6'b010000, S_5 = 6'b100000;
```

```
assign Valid = ((state == S_1) || (state == S_2)
                 || (state == S_3) || (state == S_4)) && Row;
```

```
// Does not matter if the row signal is not the debounced version.
// Assumed to settle before it is used at the clock edge
```

```
always @ (Row or Col)
case ({Row, Col})
  8'b0001_0001: Code = 0;
  8'b0001_0010: Code = 1;
  8'b0001_0100: Code = 2;
  8'b0001_1000: Code = 3;

  8'b0010_0001: Code = 4;
  8'b0010_0010: Code = 5;
  8'b0010_0100: Code = 6;
  8'b0010_1000: Code = 7;

  8'b0100_0001: Code = 8;
  8'b0100_0010: Code = 9;
  8'b0100_0100: Code = 10;
```

```
// A
```

```
8'b0100_1000: Code = 11;      // B
```

```
8'b1000_0001: Code = 12;      // C
```

```
8'b1000_0010: Code = 13;      // D
```

```
8'b1000_0100: Code = 14;      // E
```

```
8'b1000_1000: Code = 15;      // F
```

```
default:      Code = 0;      // Arbitrary choice
endcase
```

```
always @ (posedge clock or posedge reset)
if (reset) state <= S_0; else state <= next_state;
```

```
always @ (state or S_Row or Row) // Next-state logic
begin next_state = state; Col = 0;
case (state)
  // Assert all rows
  S_0: begin Col = 15; if (S_Row) next_state = S_1; end
  // Assert col 0
  S_1: begin Col = 1; if (Row) next_state = S_5; else next_state = S_2; end
  // Assert col 1
  S_2: begin Col = 2; if (Row) next_state = S_5; else next_state = S_3; end
  // Assert col 2
  S_3: begin Col = 4; if (Row) next_state = S_5; else next_state = S_4; end
  // Assert col 3
```

```

    S_4: begin Col = 8; if (Row) next_state = S_5; else next_state = S_0; end
    // Assert all rows
    S_5: begin Col = 15; if (Row == 0) next_state = S_0; end
endcase
end
endmodule

```

```

module Synchronizer (S_Row, Row, clock, reset);
    output          S_Row;
    input   [3: 0]  Row;
    input          clock, reset;
    reg           A_Row, S_Row;

    // Two stage pipeline synchronizer
    always @ (posedge clock or posedge reset) begin
        if (reset) begin A_Row <= 0;
                        S_Row <= 0;
        end
        else begin    A_Row <= (Row[0] || Row[1] || Row[2] || Row[3]);
                    S_Row <= A_Row;
        end
    end
endmodule

```

```

module Row_Signal (Row, Key, Col); // Scans for row of the asserted key
  output [3: 0] Row;
  input [15: 0] Key;
  input [3: 0] Col;
  reg [3: 0] Row;

  always @ (Key or Col) begin // Combinational logic for key assertion
    Row[0] = Key[0] && Col[0] || Key[1] && Col[1] || Key[2] && Col[2] || Key[3] &&
Col[3];
    Row[1] = Key[4] && Col[0] || Key[5] && Col[1] || Key[6] && Col[2] || Key[7] &&
Col[3];
    Row[2] = Key[8] && Col[0] || Key[9] && Col[1] || Key[10] && Col[2] || Key[11] &&
Col[3];
    Row[3] = Key[12] && Col[0] || Key[13] && Col[1] || Key[14] && Col[2] || Key[15] &&
Col[3];
  end
endmodule

```

```

//////////////////////////////////// Test Bench //////////////////////////////////////

```

```

module test_Hex_Keypad_Grayhill_072 ();
  wire [3: 0] Code;
  wire Valid;
  wire [3: 0] Col;
  wire [3: 0] Row;
  reg clock, reset;

```

```
reg    [15: 0]    Key;
integer    j, k;
reg[39: 0]    Pressed;
parameter [39: 0] Key_0 = "Key_0";
parameter [39: 0] Key_1 = "Key_1";
parameter [39: 0] Key_2 = "Key_2";
parameter [39: 0] Key_3 = "Key_3";
parameter [39: 0] Key_4 = "Key_4";
parameter [39: 0] Key_5 = "Key_5";
parameter [39: 0] Key_6 = "Key_6";
parameter [39: 0] Key_7 = "Key_7";
parameter [39: 0] Key_8 = "Key_8";
parameter [39: 0] Key_9 = "Key_9";
parameter [39: 0] Key_A = "Key_A";
parameter [39: 0] Key_B = "Key_B";
parameter [39: 0] Key_C = "Key_C";
parameter [39: 0] Key_D = "Key_D";
parameter [39: 0] Key_E = "Key_E";
parameter [39: 0] Key_F = "Key_F";
parameter [39: 0] None = "None";

always @ (Key) begin // "one-hot" code for pressed key
    case (Key)
        16'h0000: Pressed = None;
        16'h0001: Pressed = Key_0;
```

```
16'h0002: Pressed = Key_1;  
16'h0004: Pressed = Key_2;  
16'h0008: Pressed = Key_3;
```

```
16'h0010: Pressed = Key_4;  
16'h0020: Pressed = Key_5;  
16'h0040: Pressed = Key_6;  
16'h0080: Pressed = Key_7;
```

```
16'h0100: Pressed = Key_8;  
16'h0200: Pressed = Key_9;  
16'h0400: Pressed = Key_A;  
16'h0800: Pressed = Key_B;
```

```
16'h1000: Pressed = Key_C;  
16'h2000: Pressed = Key_D;  
16'h4000: Pressed = Key_E;  
16'h8000: Pressed = Key_F;
```

```
default: Pressed = None;  
endcase  
end
```



```
Hex_Keypad_Grayhill_072 M1(Code, Col, Valid, Row, S_Row, clock);  
Row_Signal M2 (Row, Key, Col);  
Synchronizer M3 (S_Row, Row, clock, reset);
```

```
initial #2000 $finish;
```

```
initial begin clock = 0; forever #5 clock = ~clock; end
```

```
initial begin reset = 1; #10 reset = 0; end
```

```
initial
```

```
  begin for (k = 0; k <= 1; k = k+1)
```

```
    begin Key = 0; #20 for (j = 0; j <= 16; j = j+1)
```

```
      begin
```

```
        #20 Key[j] = 1; #60 Key = 0; end end end
```

```
endmodule
```

