 


Advanced Digital Design with the Verilog HDL



M. D. Ciletti

**Department
of
Electrical and Computer Engineering
University of Colorado
Colorado Springs, Colorado**

ciletti@vlsic.uccs.edu

Draft: Chap 6a: Synthesis of Combinational and Sequential Logic

Copyright 2001, 2003. These notes are solely for classroom use by the instructor. No part of these notes may be copied, reproduced, or distributed to a third party, including students, in any form without the written permission of the author.

Note to the instructor: These slides are provided solely for classroom use in academic institutions by the instructor using the text, *Advance Digital Design with the Verilog HDL* by Michael Ciletti, published by Prentice Hall. This material may not be used in off-campus instruction, resold, reproduced or generally distributed in the original or modified format for any purpose without the permission of the Author. This material may not be placed on any server or network, and is protected under all copyright laws, as they currently exist. I am providing these slides to you subject to your agreeing that you will not provide them to your students in hardcopy or electronic format or use them for off-campus instruction of any kind. Please email to me your agreement to these conditions.

I will greatly appreciate your assisting me by calling to my attention any errors or any other revisions that would enhance the utility of these slides for classroom use.



COURSE OVERVIEW

- Review of combinational and sequential logic design
- Modeling and verification with hardware description languages
- Introduction to synthesis with HDLs
- Programmable logic devices
- State machines, datapath controllers, RISC CPU
- Architectures and algorithms for computation and signal processing
- Synchronization across clock domains
- Timing analysis
- Fault simulation and testing, JTAG, BIST

Synthesis of Combinational and Sequential Logic

Tasks for synthesis tools:

- detect and eliminate redundant logic
- detect combinational feedback loops
- exploit don't-care conditions
- detect unused states
- detect and collapse equivalent states
- make state assignments
- synthesize optimal, multilevel realizations of logic
subject to constraints on area and/or speed
physical technology.

Tasks for the Designer

Understand how to synthesize combinational logic

Understand how to synthesize sequential logic

Understand how language constructs synthesize

Anticipate the results of synthesis

Adhere to style conventions

Introduction to Synthesis

Three common levels of abstraction:

architectural: *sequence of operation*

transform input sequence to output sequence

no schedule for clock cycles

logical: *variables and Boolean functions*

Fixed architecture of registers, datapaths, and functional units

Synthesize an optimized netlist of gates and registers

physical: *geometric detail*

mask sets for transistor fabrication


Three Common Views

- behavioral: algorithm spec for data transformations (see Chapter 9)
- structural: datapath elements that implement the algorithm
- physical: mask set


Synthesis creates a sequence of transformations between views of a circuit, from a higher level of abstraction to a lower one, with each step leading to a more detailed description of the physical reality.

Modified Y-Chart (Fig. 6-1)

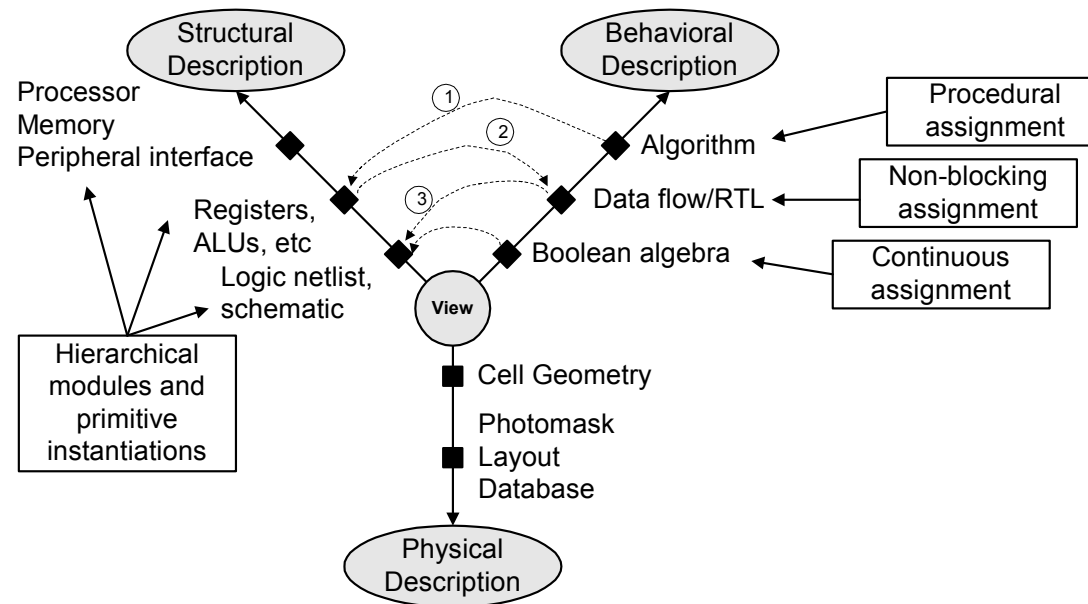- Behavioral synthesis transforms an algorithm to an architecture and a schedule of operations (clock cycles)
- Architecture is represented as an RTL model
- Synthesize RTL model is a netlist of gates and registers




Synthesis Tool Organization

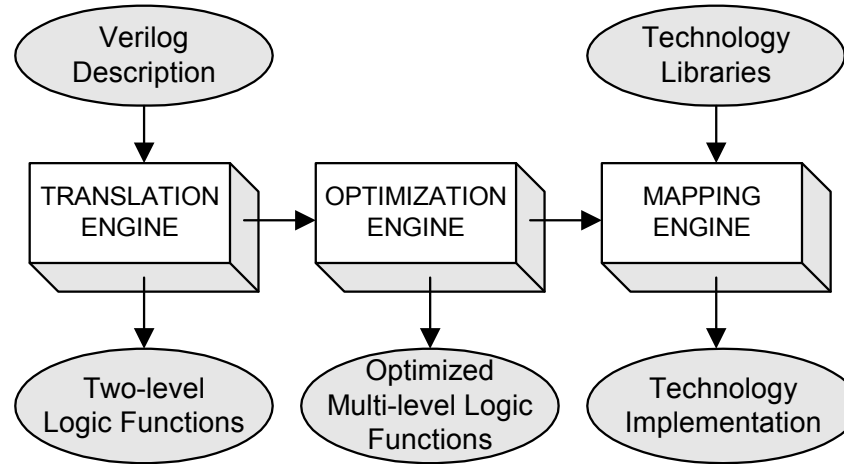

Design Goals: Functionality, area, timing, testability

Multi-Level Logic Optimization

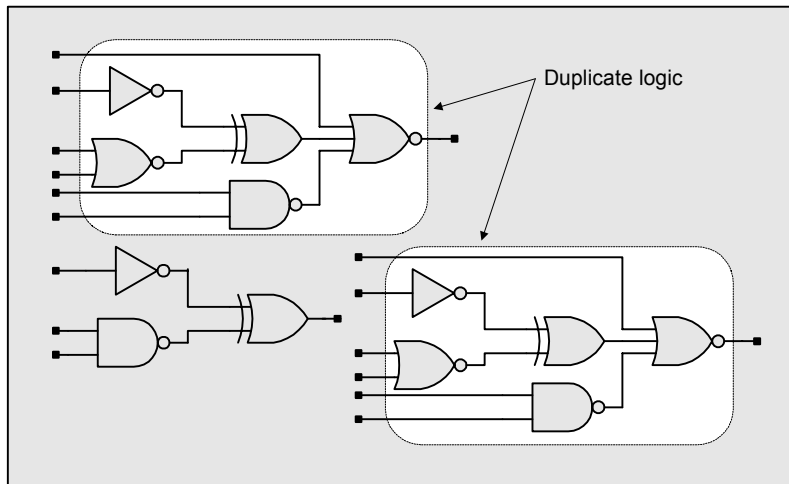


Logic Transformation: Decomposition


- Decompose a function into new nodes
- Re-use the new nodes in fanout paths

$$F = abc + abd + a'b'c' + b'c'd'$$

Two-level logic!

 
 
$$F = XY + X'Y'$$
$$X = ab$$
$$Y = c + d$$






Logic Transformation: Extraction

- Expresses a *set* of functions in terms of intermediate nodes
- Express each function in terms of its factors
- Detect which factors are shared among functions.

$F = (a + b)cd + e$ Multi-level logic!
 $G = (a + b) e'$
 $H = cde$

$X = a + b$
 $Y = cd$

 


  


Logic Transformation: Factoring

- Produce a set of functions in products of sum form
- Find a set of intermediate nodes to optimize the circuit's delay and area
- Share logic to reduce silicon area
- Create multi-level structure from two-level structure
- Sacrifice speed for area
- Key: minimize the number of literals in factored form

$$F = ac + ad + bc + bd + e$$

 

$$F = (a + b)(c + d) + e$$

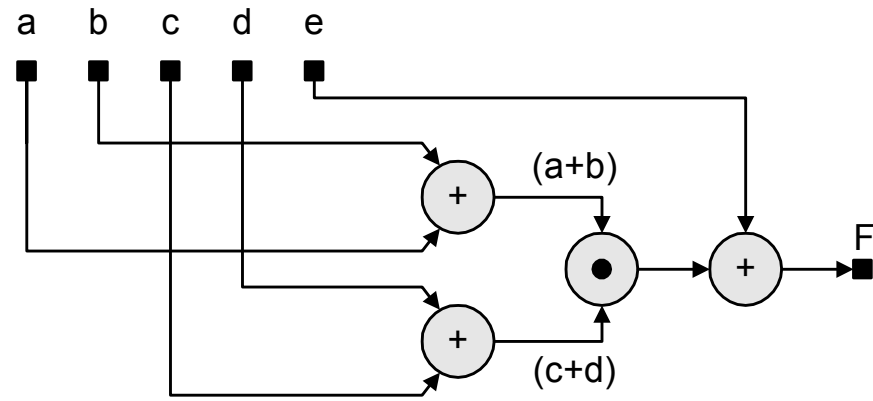

Logic Transformation: Substitution



- Express a Boolean function in terms of its inputs and another function
- Reduce replicated logic

$$G = a + b$$
$$F = a + b + c$$

After substitution:

$$F = G + c$$

New DAG:

  

Logic Transformation: Elimination (Flattening)

- Undoes decomposition
- Removes (collapses) a node in a function
- Reduces the structure of the circuit.
- Collapses levels of the circuit
- Sacrifices area to get speed


$$F = Ga + G' b$$

$$G = c + d$$

After elimination:

$$F = ac + ad + bc'd'$$

Revised DAG:

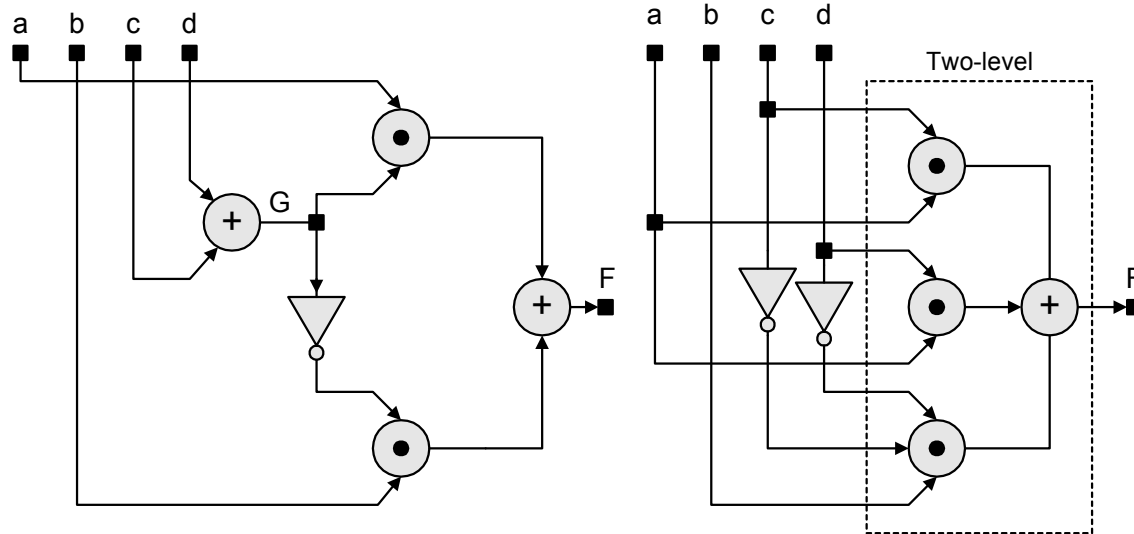

RTL Synthesis

Given an architecture, an allocation of resources, and a schedule of clock cycles

- Convert language based RTL statements into Boolean equations
- Optimize the Boolean equations
- Synthesize an optimal realization in target technology


Synthesis tools (Synopsis Design Compiler) work in this domain.

High-Level Synthesis

Also called *behavioral synthesis* or *architectural synthesis*

- Find an architecture whose resources can be scheduled and allocated to implement an algorithm
 - Difficulty: many architectures (Datapath elements, control unit, memory) may realize the same algorithm
 - Resource allocation:
 - Identify functional operators/units
 - Infer memory
 - Bind operators to functional units
 - Resource scheduling: Assign operations to clock cycles
-

Parse Trees and data Flow Graphs

 

Synthesis of Combinational Logic

Options:

- Netlist of primitives
 - User-defined primitive
 - Continuous assignments
 - Level-sensitive cyclic behavior
 - Procedural continuous assignment (***assign ... deassign***)
-


Synthesis: Netlist of Primitives

Value: remove redundant logic


Pre-Synthesis:

```
module boole_opt (y_out1, y_out2, a, b, c, d, e);  
output      y_out1, y_out2;  
input      a, b, c, d, e;  
  
  and      (y1, a, c);  
  and      (y2, a, d);  
  and      (y3, a, e);  
  or       (y4, y1, y2);  
  or       (y_out1, y3, y4);  
  and      (y5, b, c);  
  and      (y6, b, d);  
  and      (y7, b, e);  
  or       (y8, y5, y6);  
  or       (y_out2, y7, y8);  
endmodule
```

Pre-Synthesis:

 

Synthesis Result

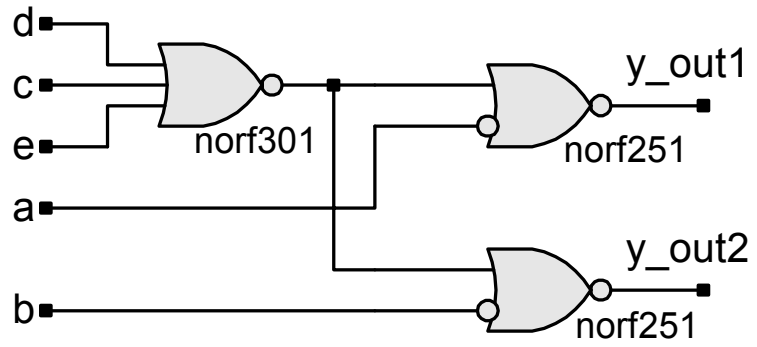


Synthesis: Continuous Assignment

- Built-in operators have physical counterparts
- Continuous assignment statements are synthesizable
- Will produce (1) combinational logic, (2) latch, (3) three-state output

Example 6.7

```
module or_nand (y, enable, x1, x2, x3, x4);  
  output y;  
  input   enable, x1, x2, x3, x4;  
  
  assign y = ~(enable & (x1 | x2) & (x3 | x4));  
endmodule
```

 

Synthesis: Level-Sensitive Cyclic Behavior

A level-sensitive cyclic behavior will synthesize to combinational logic if it assigns a value to each output for every possible value of its inputs.

- The event control expression of the behavior must be sensitive to every input
- Every path of the activity flow must assign value to every output.

Example 6.8 (Two-Bit Comparator Algorithm)

- The data words are identical if all of their bits match in each position
- Otherwise, the most significant bit at which the words differ determines their relative magnitude


```

module comparator (a_gt_b, a_lt_b, a_eq_b, a, b); // Alternative algorithm
parameter    size = 2;
output      a_gt_b, a_lt_b, a_eq_b;
input       [size: 1]    a, b;
reg        a_gt_b, a_lt_b, a_eq_b;
integer    k;

always @ ( a or b) begin: compare_loop
  for (k = size; k > 0; k = k-1) begin
    if (a[k] != b[k]) begin
      a_gt_b = a[k];
      a_lt_b = ~a[k];
      a_eq_b = 0;
      disable compare_loop;
    end          // if
  end          // for loop
  a_gt_b = 0;
  a_lt_b = 0;
  a_eq_b = 1;
end          // compare_loop
endmodule

```


Synthesis Result:

 

Example 6.9 (Mux with selector logic)

```
module mux_logic (y, select, sig_G, sig_max, sig_a, sig_b);  
  output      y;  
  input       select, sig_G, sig_max, sig_a, sig_b;  
  
  assign y = (select == 1) || (sig_G == 1) || (sig_max == 0) ? sig_a : sig_b;  
  
endmodule
```

Synthesis Result

 

sig_G

select

sig_max

sig_a

y

Synthesis of Priority Structures


- A **case** statement implicitly attaches higher priority to the first item that it decodes than to the last one
- If the case items are mutually exclusive the synthesis tool will treat them as though they had equal priority and will synthesize a mux rather than a priority structure.
- Even when the list of case items is not mutually exclusive a synthesis tool might allow the user to direct that they be treated without priority (e.g., Synopsys *parallel_case* directive). This would be useful if only one case item could be selected at a time in actual operation.

- An **if** statement implies higher priority to the first branch than to the remaining branches.
- If branching is mutually exclusive, synthesis produces a mux structure
- Otherwise create a priority structure

Example 6.10

```
module mux_4pri (y, a, b, c, d, sel_a, sel_b, sel_c);  
output y;  
input a, b, c, d, sel_a, sel_b, sel_c;  
reg y;  
  
  always @ (sel_a or sel_b or sel_c or a or b or c or d)  
  begin  
    if (sel_a == 1)      y = a; else // highest priority  
    if (sel_b == 0)      y = b; else  
    if (sel_c == 1)      y = c; else  
                          y = d; // lowest priority  
  
  end  
endmodule
```

Synthesis Result

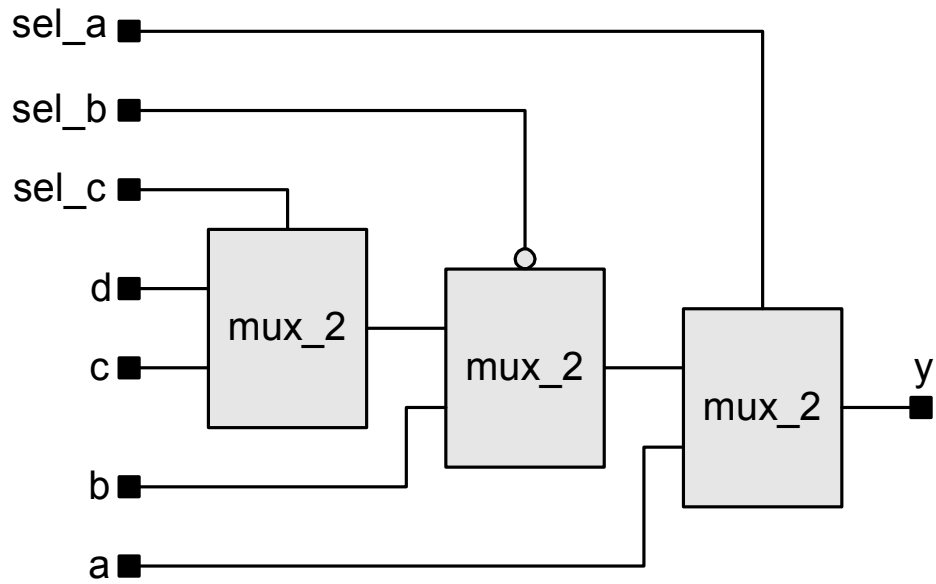


Exploiting Don't-Care Conditions


SYNTHESIS TIP

An assignment to **x** in a **case** or an **if** statement will be treated as a don't care condition in synthesis.

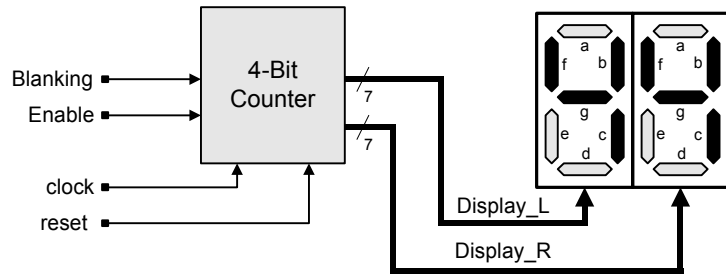Example 6.11 (Latched Seven Segment Display)



(a)

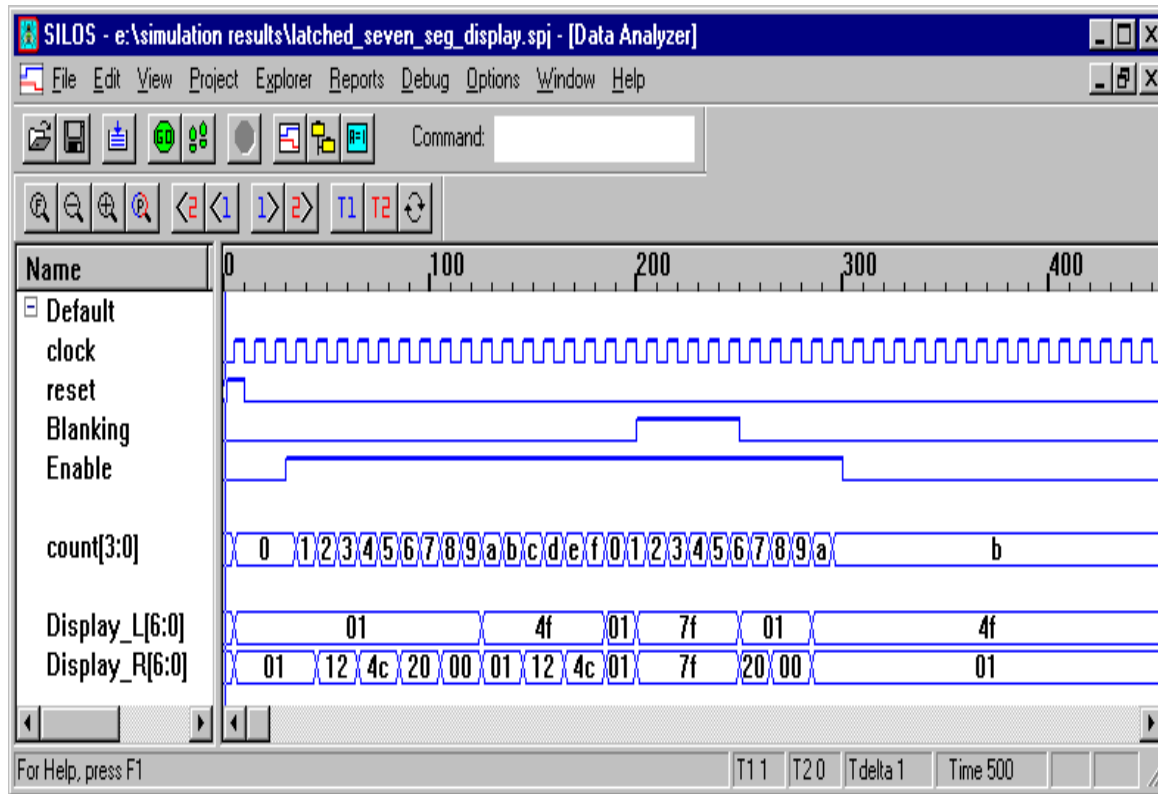

module Latched_Seven_Seg_Display

(Display_L, Display_R, Blanking, Enable, clock, reset);

output [6: 0] Display_L, Display_R;**input** Blanking, Enable, clock, reset;**reg** [6: 0] Display_L, Display_R;**reg** [3: 0] count;

//

abc_defg

parameter BLANK = 7'b111_1111;**parameter** ZERO = 7'b000_0001; // h01**parameter** ONE = 7'b100_1111; // h4f**parameter** TWO = 7'b001_0010; // h12**parameter** THREE = 7'b000_0110; // h06**parameter** FOUR = 7'b100_1100; // h4c**parameter** FIVE = 7'b010_0100; // h24**parameter** SIX = 7'b010_0000; // h20**parameter** SEVEN = 7'b000_1111; // h0f**parameter** EIGHT = 7'b000_0000; // h00**parameter** NINE = 7'b000_0100; // h04**always @ (posedge clock)****if** (reset) count <= 0;**else if** (Enable) count <= count +1;

```
always @ (count or Blanking)
if (Blanking) begin Display_L = BLANK; Display_R = BLANK; end else
  case (count)
    0:      begin Display_L = ZERO; Display_R = ZERO; end
    2:      begin Display_L = ZERO; Display_R = TWO; end
    4:      begin Display_L = ZERO; Display_R = FOUR; end
    6:      begin Display_L = ZERO; Display_R = SIX; end
    8:      begin Display_L = ZERO; Display_R = EIGHT; end
    10:     begin Display_L = ONE; Display_R = ZERO; end
    12:     begin Display_L = ONE; Display_R = TWO; end
    14:     begin Display_L = ONE; Display_R = FOUR; end
    //default: begin Display_L = BLANK; Display_R = BLANK; end
  endcase
endmodule
```


SYNTHESIS TIP

If a conditional operator assigns the value **z** to the right-hand side expression of a continuous assignment in a level-sensitive behavior, the statement will synthesize to a three-state device driven by combinational logic.


Example 6.12

```
module alu_with_z1 (alu_out, data_a, data_b, enable, opcode);  
  input   [2: 0]    opcode;  
  input   [3: 0]    data_a, data_b;  
  input           enable;  
  output           alu_out;      // scalar for illustration  
  reg      [3: 0]    alu_reg;  
  
  assign alu_out = (enable == 1) ? alu_reg : 4'bz;  
  
  always @ (opcode or data_a or data_b)  
  case (opcode)  
    3'b001:  alu_reg = data_a | data_b;  
    3'b010:  alu_reg = data_a ^ data_b;  
    3'b110:  alu_reg = ~data_b;  
    default: alu_reg = 4'b0; // alu_with_z2 has default: alu_reg = 4'bx;  
  endcase  
endmodule
```

Synthesis Result: alu_with_z1

 

 Synthesis Result: alu_with_z2 (Exploit don't-cares)




ASIC Cells and Resource Sharing


Example 6.13

```
module badd_4 (Sum, C_out, A, B, C_in);  
  output [3: 0] Sum;  
  output C_out;  
  input [3: 0] A, B;  
  input C_in;  
  
  assign {C_out, Sum} = A + B + C_in;  
endmodule
```

Synthesis Result (With Library Cells)

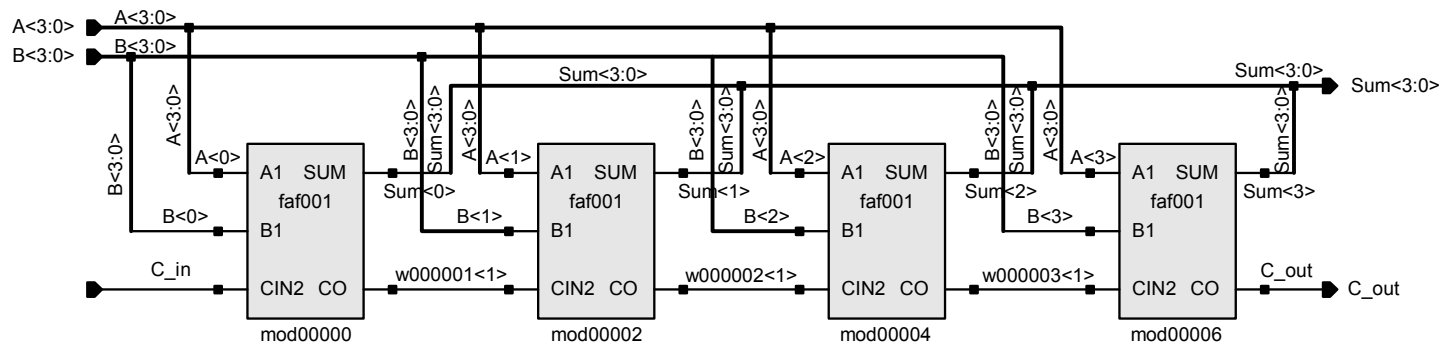

Synthesis Result (Without library cells)

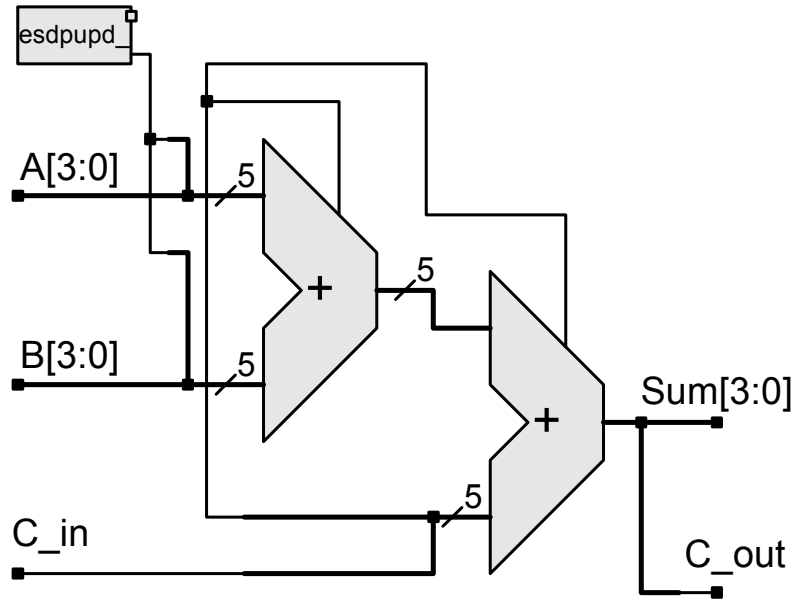


SYNTHESIS TIP

Use parentheses to control operator grouping and reduce the size of a circuit.

```
assign y_out = sel ? data_a + accum : data_a + data_b;
```

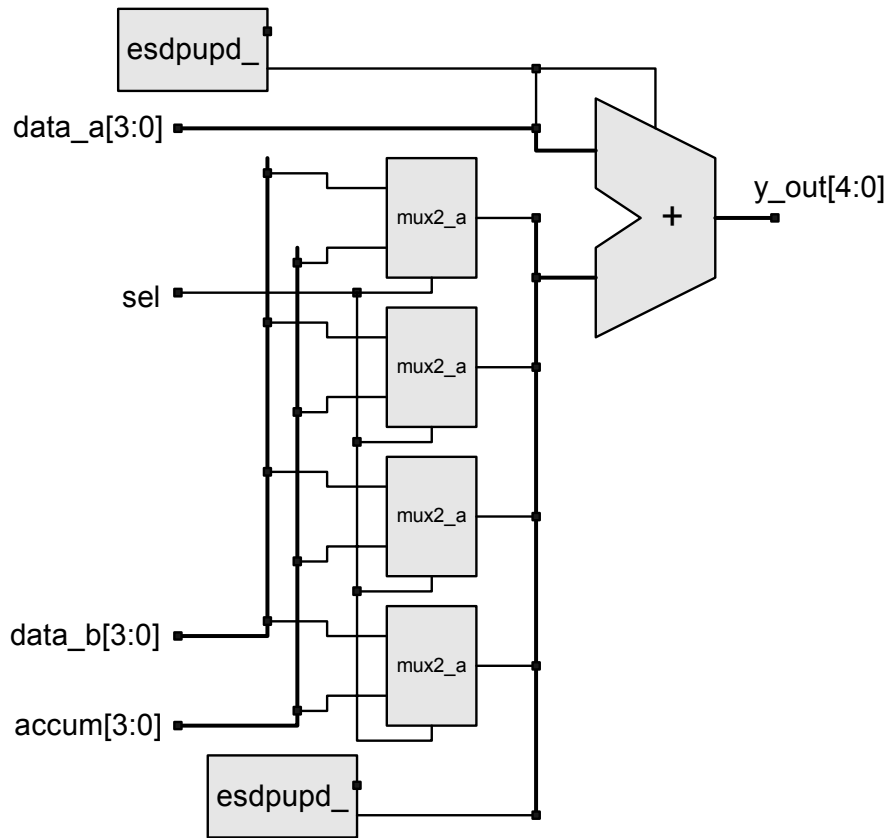Example 6.14 The use of parentheses in the description in *res_share* forces the synthesis tool to multiplex the datapaths and produce the circuit shown in Figure 6.21.

```
module res_share (y_out, sel, data_a, data_b, accum);  
  output [4: 0]    y_out;  
  input   [3: 0]    data_a, data_b, accum;  
  input                sel;  
  
  assign y_out = data_a + (sel ? accum : data_b);  
endmodule
```



Synthesis of Sequential Logic with Latches

SYNTHESIS TIP

A feedback-free netlist of *combinational primitives* will synthesize into latch-free combinational logic.

SYNTHESIS TIP

A continuous assignment with feedback in a conditional operator will synthesize into a latch.

SYNTHESIS TIP

A set of feedback-free *continuous assignments* will synthesize into latch-free combinational logic.

Example 6.15

```
assign data_out = (CS_b == 0) ? (WE_b == 0) ? data_in : data_out : 1'bz;
```





Accidental Synthesis of Latches


Example 6.16

```
module or4_behav (y, x_in);
    parameter    word_length = 4;
    output       y;
    input        [word_length - 1: 0] x_in;
    reg          y;
    integer      k;    // Eliminated in synthesis

    always @ x_in
    begin: check_for_1
        y = 0;
        for (k = 0; k <= word_length -1; k = k+1)
            if (x_in[k] == 1) begin
                y = 1;
                disable check_for_1;
            end
        end
    end
endmodule
```

```
module or4_behav_latch (y, x_in);  
  
  parameter    word_length = 4;  
  output      y;  
  input       [word_length - 1: 0] x_in;  
  reg        y;  
  integer    k;  
  
  always @ (x_in[3:1]) // incomplete event control expression  
  begin: check_for_1  
    y = 0;  
    for (k = 0; k <= word_length - 1; k = k+1)  
      if (x_in[k] == 1)  
        begin  
          y = 1;  
          disable check_for_1;  
        end  
    end  
end  
endmodule
```

  

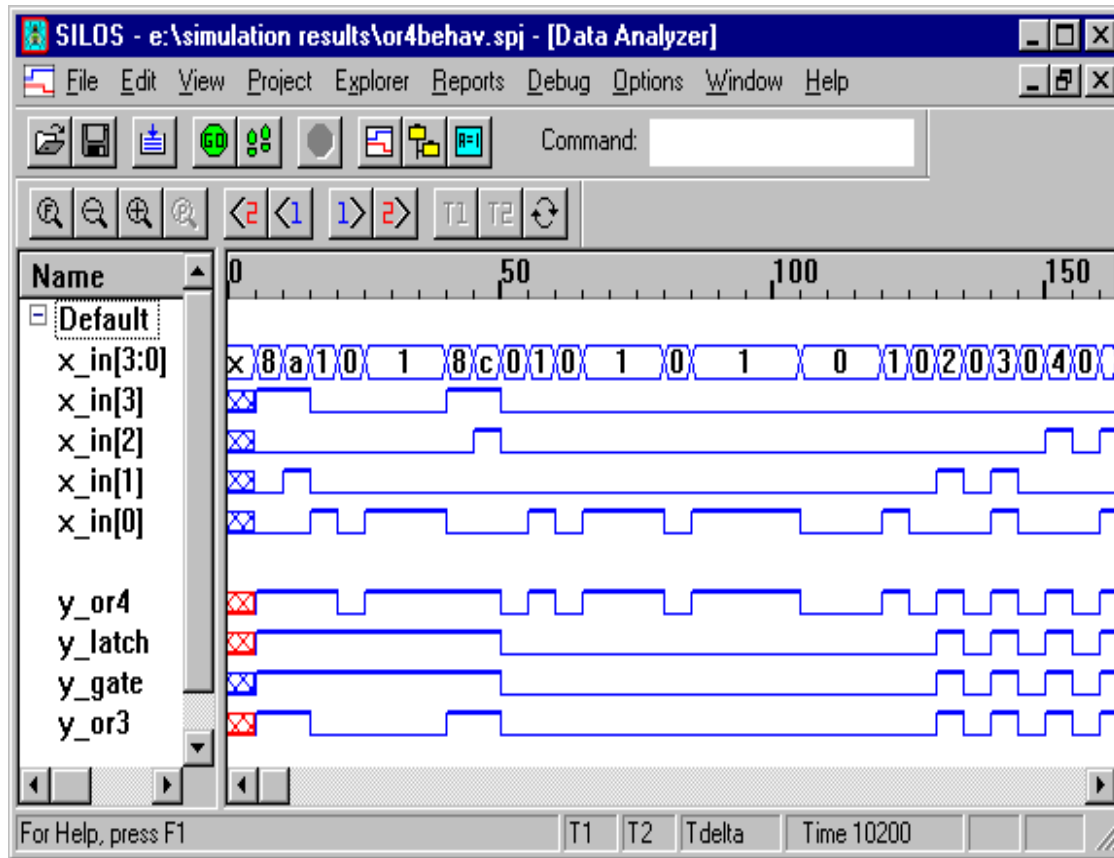



SYNTHESIS TIP

A Verilog description of combinational logic must assign value to the outputs for all possible values of the inputs.

 Example 6.17

```
module mux_latch (y_out, sel_a, sel_b, data_a, data_b);  
  output      y_out;  
  input       sel_a, sel_b, data_a, data_b;  
  reg         y_out;  
  
  always @ ( sel_a or sel_b or data_a or data_b )  
    case ({sel_a, sel_b})  
      2'b10: y_out = data_a;  
      2'b01: y_out = data_b;  
    endcase  
endmodule
```




 


Intentional Synthesis of Latches

 Example 6.18

```
module latch_if1(data_out, data_in, latch_enable);  
  output      [3: 0]    data_out;  
  input       [3: 0]    data_in;  
  input                               latch_enable;  
  reg         [3: 0]    data_out;  
  
  always @ (latch_enable or data_in)  
    if (latch_enable) data_out = data_in;  
    else data_out = data_out;  
endmodule
```




SYNTHESIS TIP

An **if** statement in a level-sensitive behavior will synthesize to a latch if the statement assigns value to a register variable in some, but not all, branches, i.e., the statement is incomplete.


Example 6.19

```
module latch_if2 (data_out, data_in, latch_enable);  
  output [3: 0] data_out;  
  input [3: 0] data_in;  
  input latch_enable;  
  reg [3: 0] data_out;  
  
  always @ (latch_enable or data_in)  
    if (latch_enable) data_out = data_in; // Incompletely specified  
endmodule
```

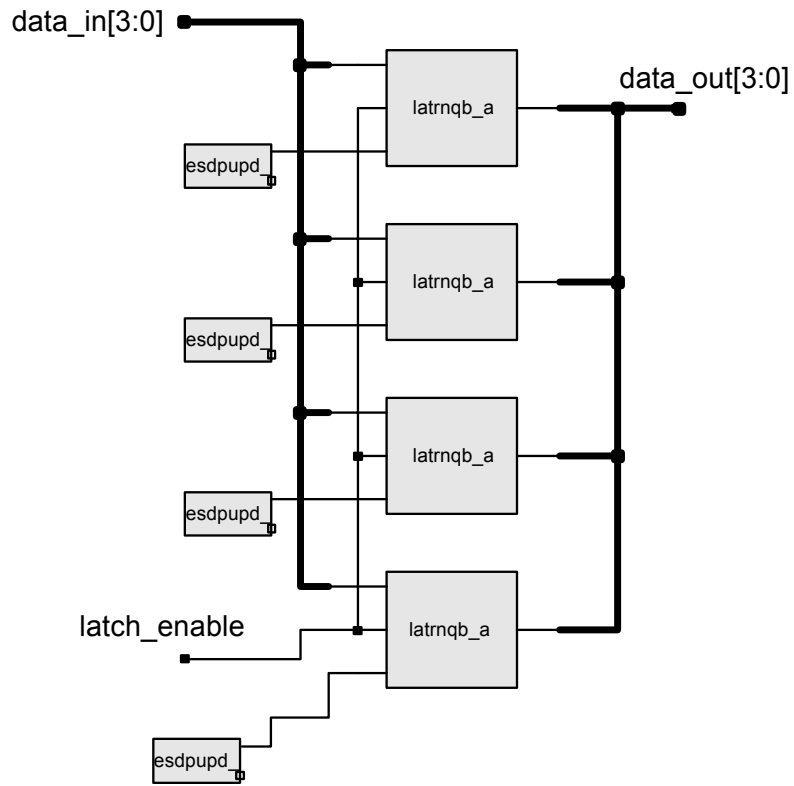

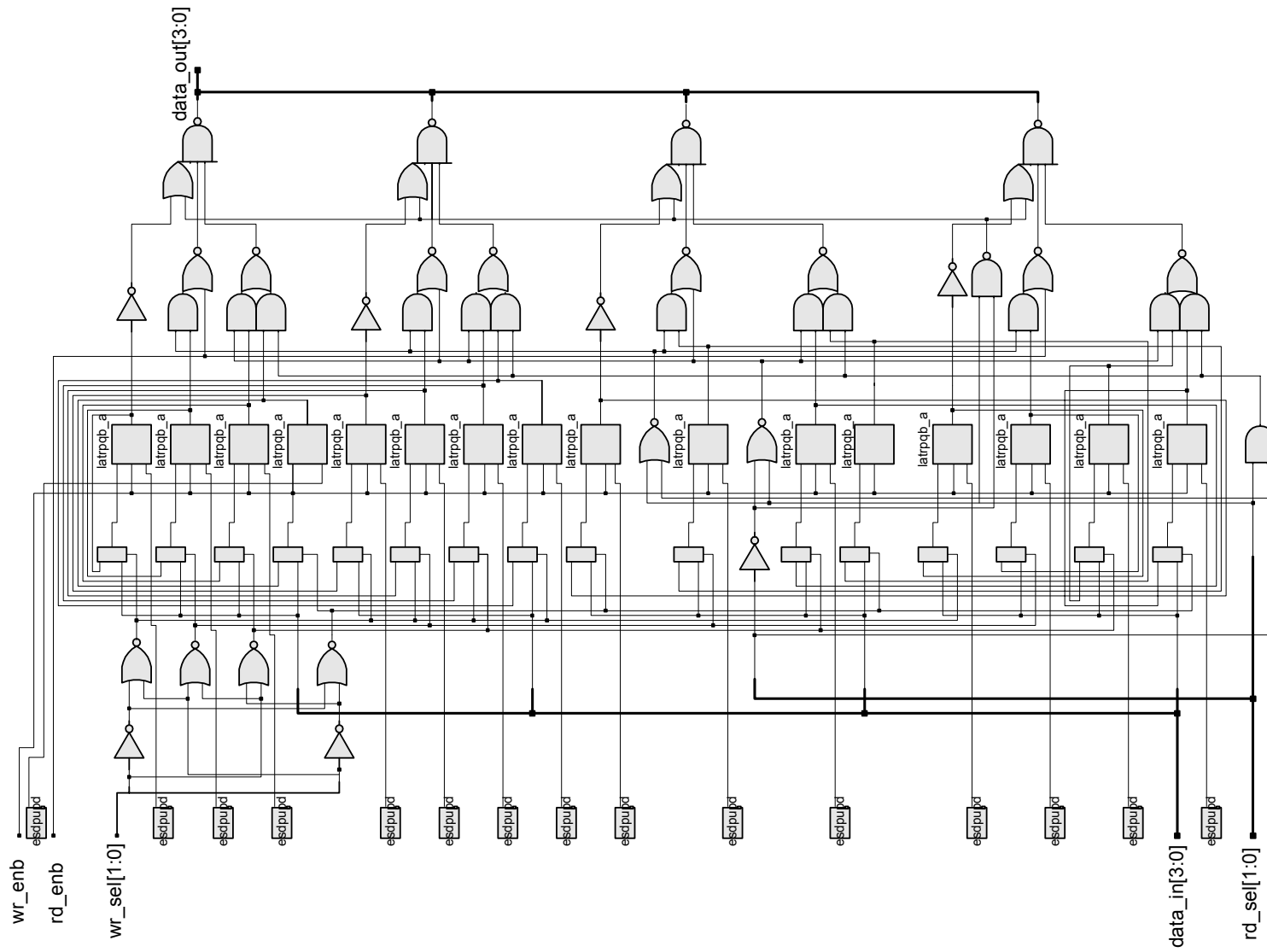Example 6.20 (Register File)

```
module sn54170 (data_out, data_in, wr_sel, rd_sel, wr_enb, rd_enb);  
  output      [3: 0]    data_out;  
  input       wr_enb, rd_enb;  
  input       [1: 0]    wr_sel, rd_sel;  
  input       [3: 0]    data_in;  
  
  reg         [3: 0]    latched_data [3: 0];  
  
  always @ (wr_enb or wr_sel or data_in) begin  
    if (!wr_enb) latched_data[wr_sel] = data_in;  
  end  
  
  assign data_out = (rd_enb) ? 4'b1111 : latched_data[rd_sel];  
  
endmodule
```



Synthesis of Three-State Devices and Bus Interfaces


Example 6.21 (Uni-directional Bus Interface)

```
module Uni_dir_bus ( data_to_bus, bus_enable);
  input          bus_enable;
  output [31: 0] data_to_bus;
  reg [31: 0]    ckt_to_bus;

  assign data_to_bus = (bus_enable) ? ckt_to_bus : 32'bz;

  // Description of core circuit goes here to drive ckt_to_bus

endmodule
```

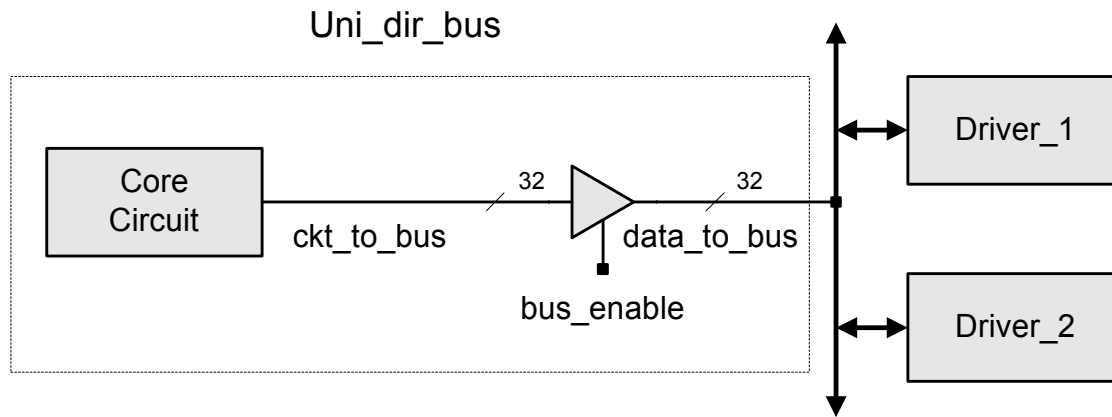

Example 6.22 (Bi-directional Bus Interface)

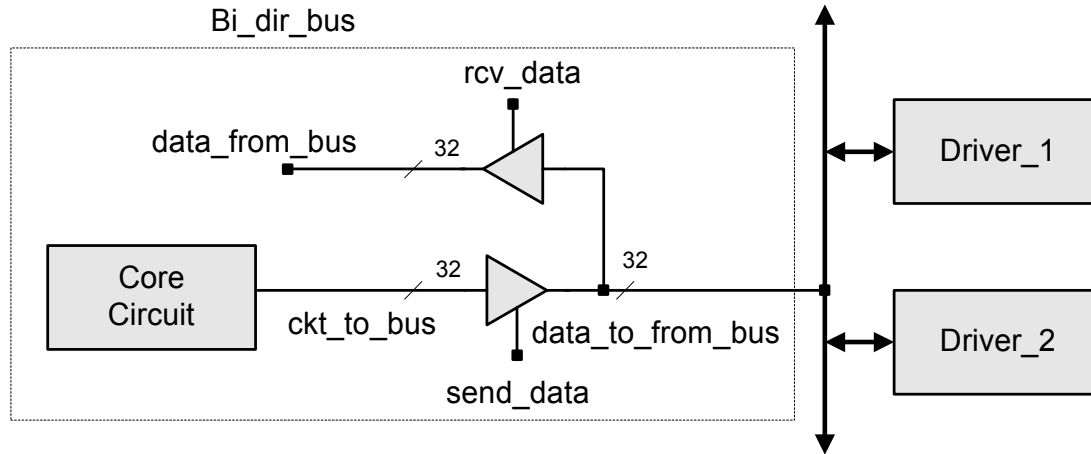


Figure 6.28 Bi-directional interface to a bi-directional bus.

```
module Bi_dir_bus (data_to_from_bus, send_data, rcv_data);  
  
  inout   [31: 0]   data_to_from_bus;  
  input   send_data, rcv_data;  
  wire    [31: 0]   ckt_to_bus;  
  wire    [31: 0]   data_to_from_bus, data_from_bus;  
  
  assign data_from_bus = (rcv_data) ? data_to_from_bus : 'bz;  
  assign data_to_from_bus = (send_data) ? ckt_to_bus : 32'bz;  
  
  // Behavior using data_from_bus and generating  
  // ckt_to_bus goes here  
  
endmodule
```