

# Microprocessors and Microcontrollers (EE-231)

## **Lecture-11**

# Main Objectives

- Hardware Specs of 8086/8088
  - Bus Timing
  - Ready and Wait state Generation
  - Maximum Mode vs Minimum Mode
  - 8288 Bus Controller

# Bus Timing


The 8086/8088 microprocessors use the memory and I/O in periods called **bus cycles**.

Each bus cycle consists of 4 clock cycles.

Thus for 8086 running at 5MHz it would take 800ns for a complete bus cycle.


Each read or write operation take 1 bus cycles.

# Read Timing (Simplified)

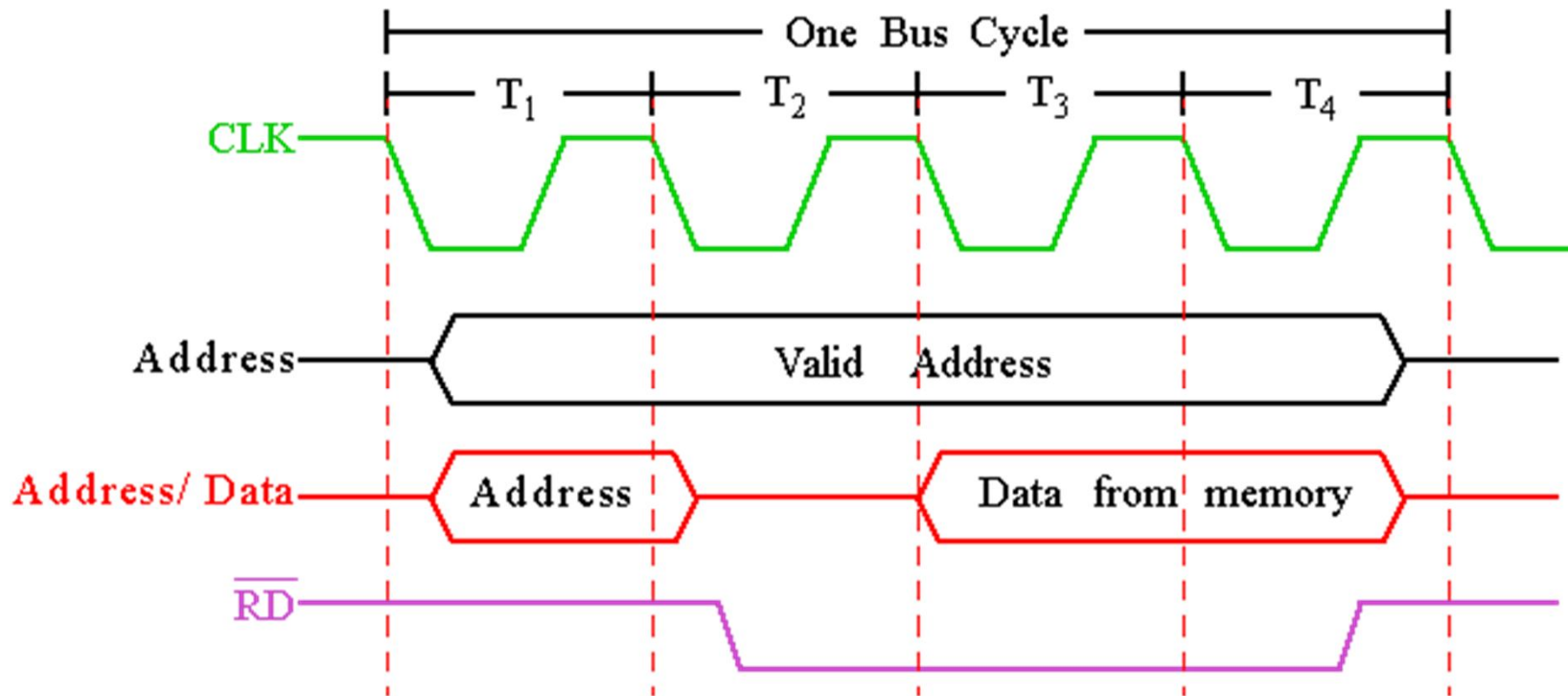


**Simplified 8086 Read Bus Cycle**

# Read Timing

 

**Bus Timing for a Read Operation**


# Read Timing

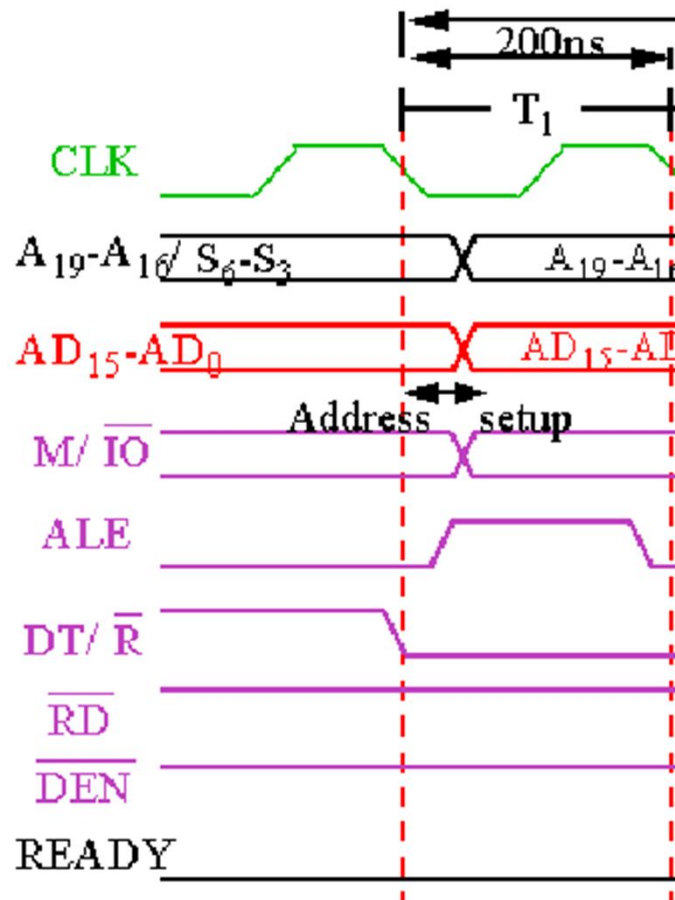

## During $T_1$ :

- The address is placed on the Address/Data bus.
- Control signals M/ $\overline{I}$ O , ALE and DT/ $\overline{R}$  specify memory or I/O, latch the address onto the address bus and set the direction of data transfer on data bus.

# Read Timing

 


*During T<sub>2</sub> :*

- 8086 issues the RD or WR signal, DEN , and, for a write, the data.

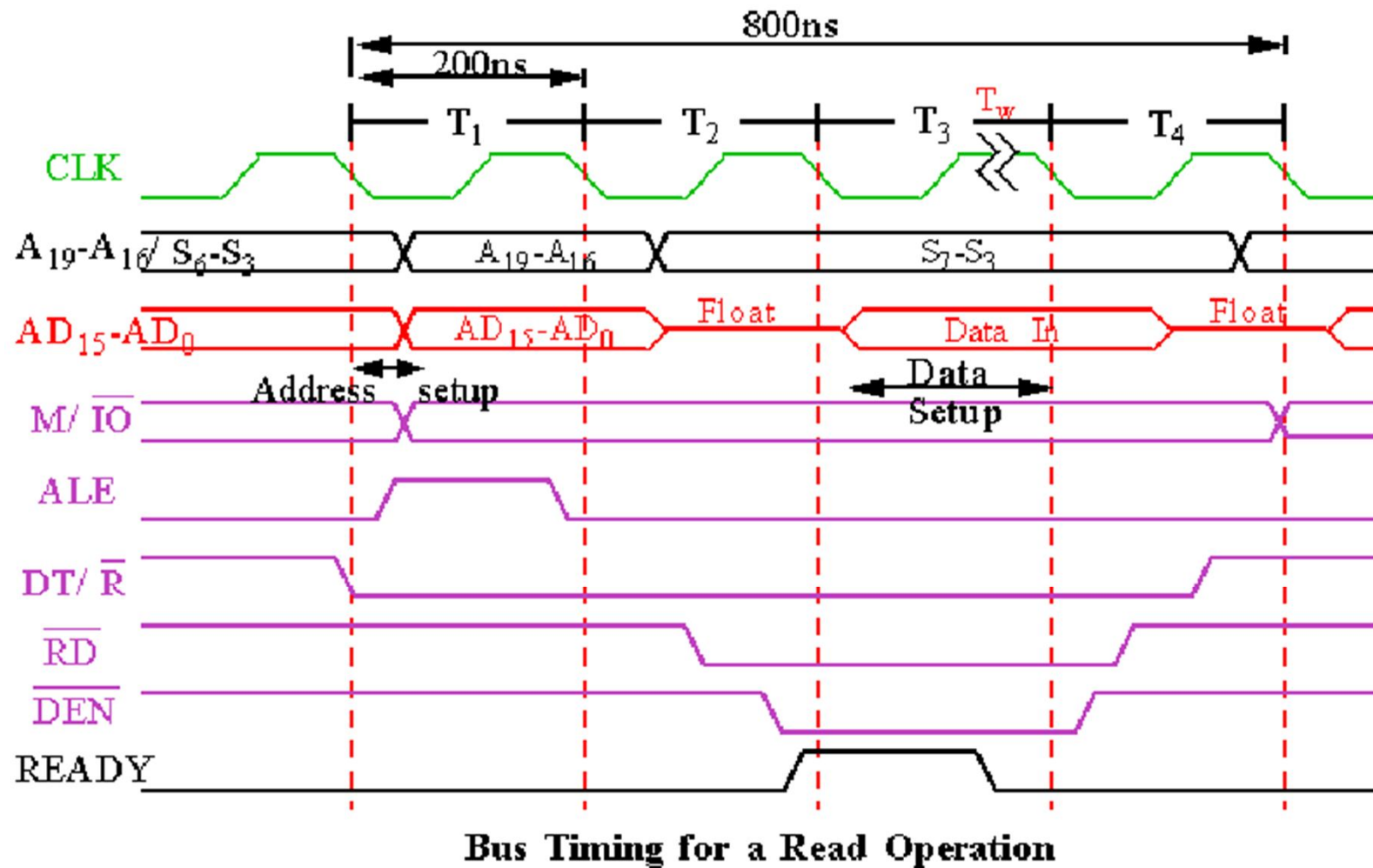- DEN enables the memory or I/O device to receive the data for writes and the 8086 to receive the data for reads.








**During  $T_4$ :**

- All bus signals are deactivated, in preparation for next bus cycle.
- Data is sampled for reads, writes occur for writes.

# Write Timing (simplified)

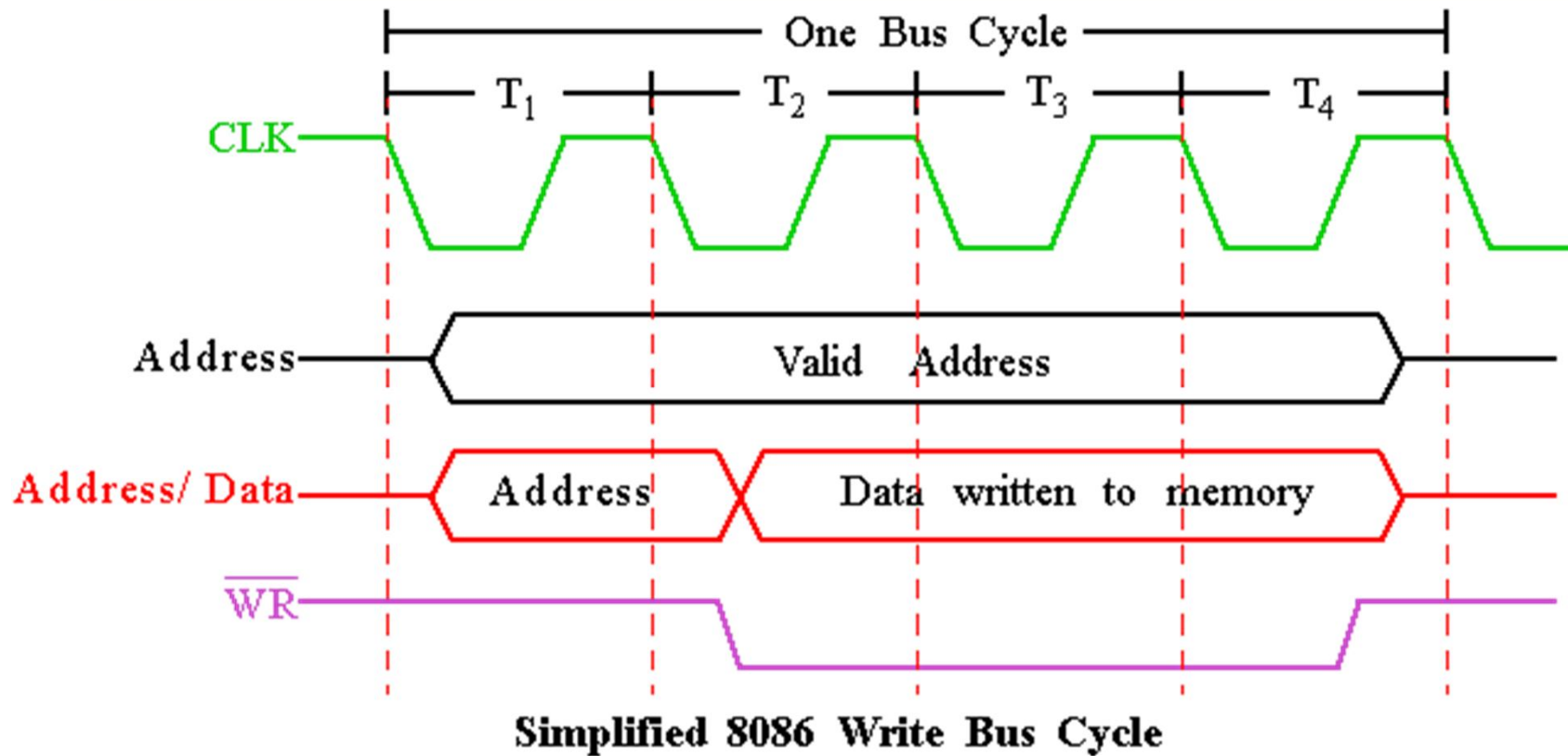


**Convert this simple timeline to include all the necessary pins**

# Ready and the Wait State

- Wait state( $T_W$ ) :
  - It is an extra clocking period, inserted between T2 & T3 in order to give memory and other **slow** devices to complete data transfer.
- READY input :
  - This input causes wait states for slower memory & I/O components
  - It is sampled at the end of T2, and if applicable, in middle of  $T_W$
  - if READY = 0 at end of T2 : T3 is delayed and  $T_W$  is inserted between T2 and T3
  - READY is next sampled at middle of  $T_W$  : to determine whether the next state is another  $T_W$  or T3

 
# Ready and the Wait State

- The timing requirements of the Ready signal are given below.
- These requirements are guaranteed by the 8284A clock generator.
- 8284A receives wait state information via its RDY input and then through its internal synchronization circuitry, it generates Ready signal for micro Processor.
- If one wait state is inserted, then the memory access time, normally 460 ns with a 5 MHz clock, is lengthened by one clocking period (200ns) to 660 ns.


 
# RDY and the 8284A


- Internal structure of 8284A
  - $RDY1 \cdot \overline{AEN1} + RDY2 \cdot \overline{AEN2}$  : to generate input to one or two stage of synchronization
  - $\overline{ASYNC} = 1$  (high) : select one stage of synchronization
    - RDY : kept from reaching 8086/88 READY pin until the next negative edge of clock
  - $\overline{ASYNC} = 0$  (ground): select two stage of synchronization
    - on 1<sup>st</sup> positive edge of clock : 1<sup>st</sup> FF capture RDY
    - output of 1<sup>st</sup> FF : fed to 2<sup>nd</sup> FF
    - on next negative edge of clock : 2<sup>nd</sup> FF capture RDY




# RDY and the 8284A

- A circuit that generates almost any no of wait states for  $\mu P$  can be implemented via **8-bit shift reg.(74LS164)**
- Its Q outputs all have zero whenever cleared.
- It is cleared back when  $RD'=WR'=INTA'=1$  ,this condition remains until state T2 and till then  $Q = 0$
- At positive edge of T2 :
  - shift right happens,  $Q_A = 1$  (because Serial Input(SI=1)).
  - $RDY1 = 0$  because  $CS' = 0$  ||  $Q_B = 0$
- Therefore a wait state is inserted
- At positive edge of Tw :
- Another shift right happens,  $Q_A = Q_B = 1$ 
  - $RDY1 = 1$  because  $CS' = 0$  ||  $Q_B = 1$
- Therefore no more wait state is inserted

# Wait state generation circuit

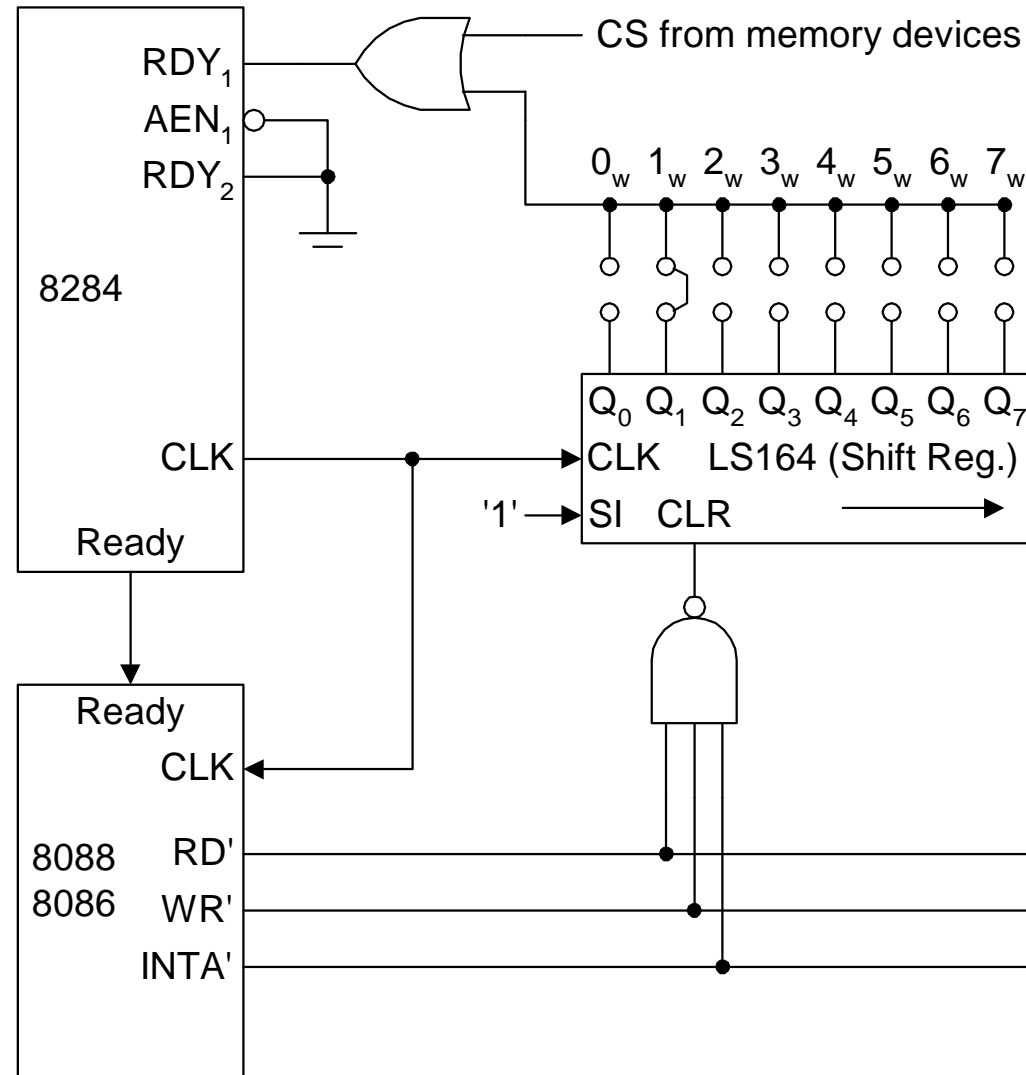

# Wait state generation Timing

 




# MIN and MAX Mode



- *Controlled through the MN/MX pin.*
- **Minimum mode** *is cheaper since all control signals for memory and I/O are generated by the microprocessor.*
- **Maximum mode** *is designed to be used when a coprocessor (8087) exists in the system. Some of the signals must be externally generated. This requires the addition of an external bus controller—the 8288 bus controller*
- This mode was dropped from Intel family starting from 80286

# What is the apparent difference ?

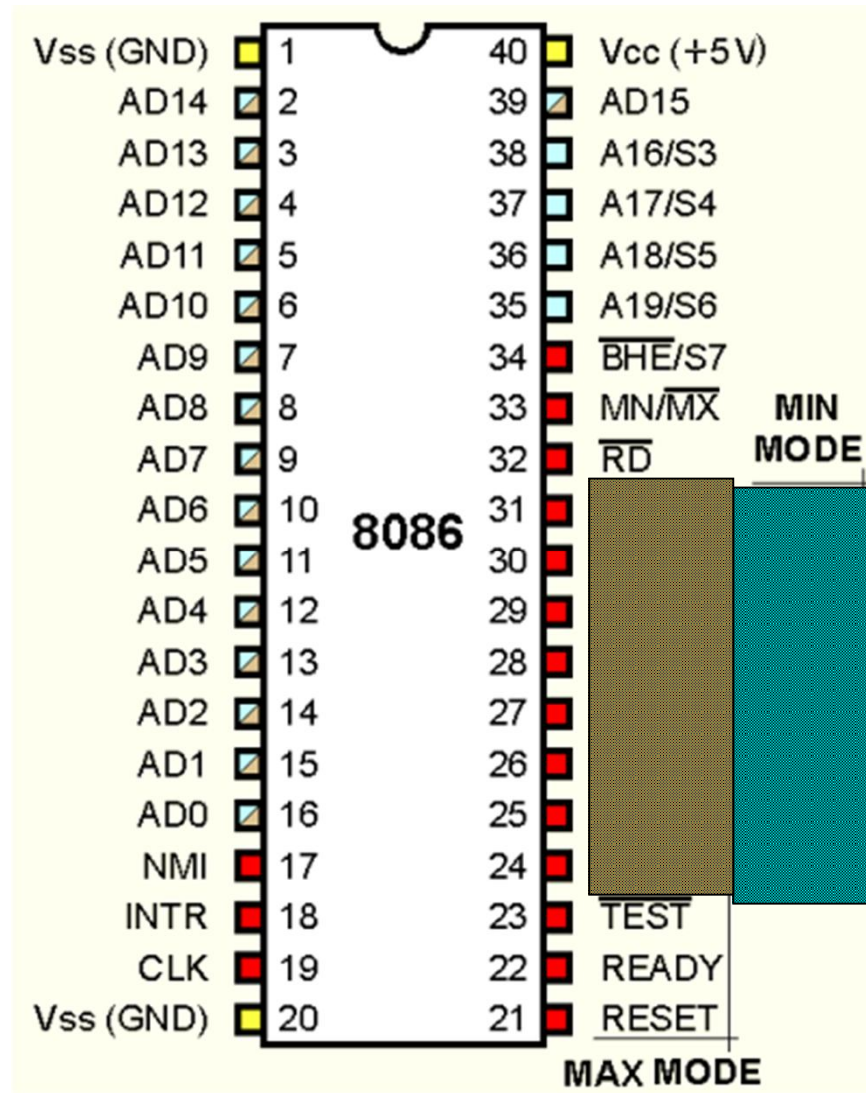
 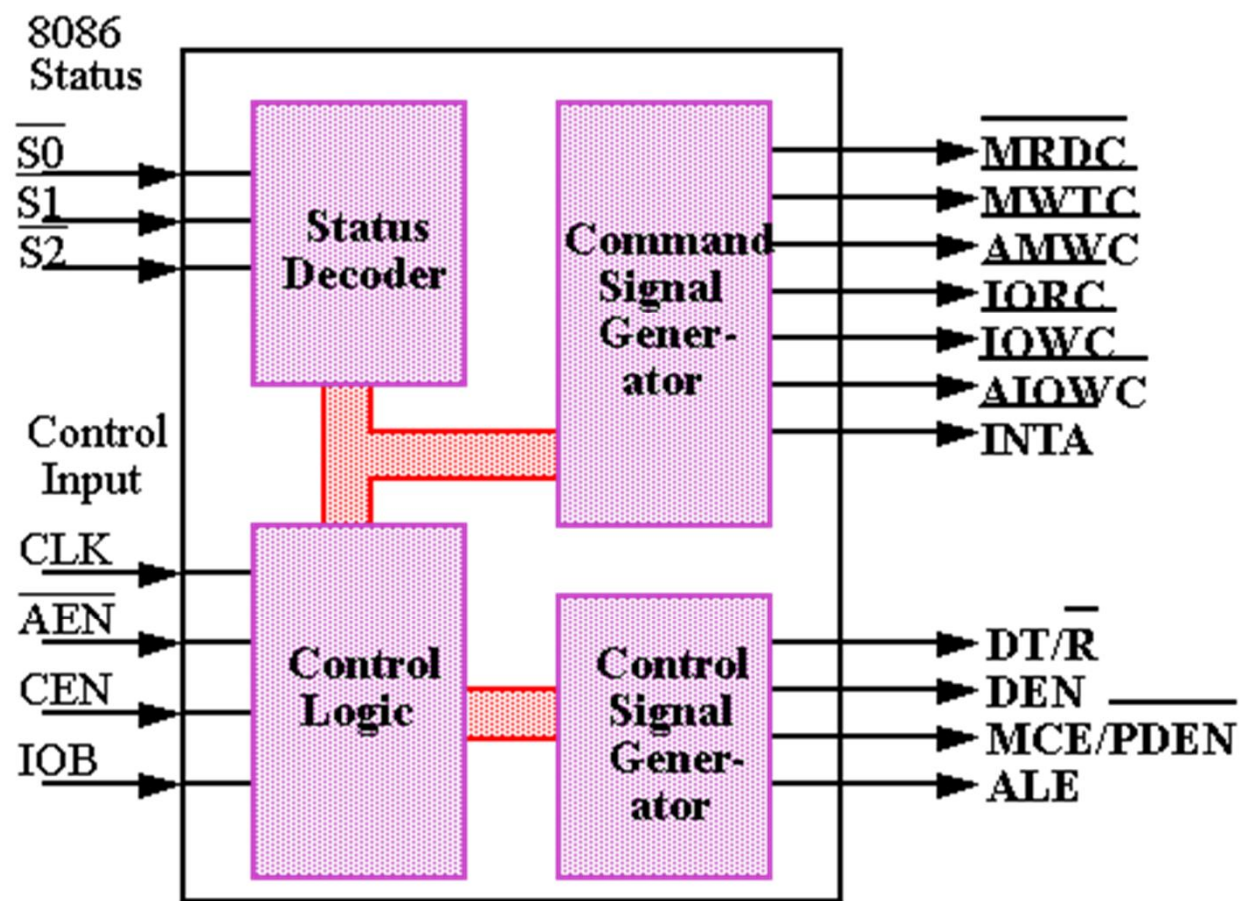
# The 8288 Bus Controller

- It provides signals eliminated from 8086/88 by maximum mode operation
- **S2,S1,S0 (status) input :**  
It is connected to status output on  $\mu$ P. It is devoted to generate the timing signals for the system by monitoring the current status of the  $\mu$ P
- **CLK input :**  
It is connected CLK output of 8284A. It provides internal timing.
- **ALE(address latch enable) output :**  
It is used to demultiplex the address/data bus.
- **DEN(data bus enable) output :**  
It controls bi-directional data bus buffers.
- **DT/R'(data transmit/receive) output :**  
It tells the direction of data to the buffers.



# The 8288 Bus Controller


- **AEN'(address enable) input :**  
It cause to enable memory control signals
- **CEN(control enable) input:**  
It enables the command output
- **IOB(I/O bus mode) input :**  
It selects either system bus or I/O bus mode operation
- **INTA'(interrupt acknowledge) output :**  
It generates acknowledgement whenever interrupt is requested, to tell the device that the interrupt is being serviced.
- **MCE/PDEN'(master cascade/peripheral data) output :**  
It selects cascade operation for interrupt controller if IOB is 0, and enable the I/O bus transceivers if IOB is 1

# The 8288 Bus Controller


Note that In 8288 Bus controller there are separate Read and Write control signals for memory and I/O

- **AIOWC'**(advanced I/O write command) output :  
It provide I/O with its advanced I/O write control signal
- **AMWC'**(advanced memory write command):  
It provides memory with an early or advanced write signal.
- **IOWC'**(I/O write) :  
It provide I/O with its main write signal
- **IORC'** (I/O Read command):  
It provides I/O with its read control signal.
- **MWTC'**(Memory write command):  
It provides memory with its normal write control signal.
- **MRDC'**(Memory Read command):  
It provides memory with a read control signal.

# 8088 Minimum Mode System Block Diagram

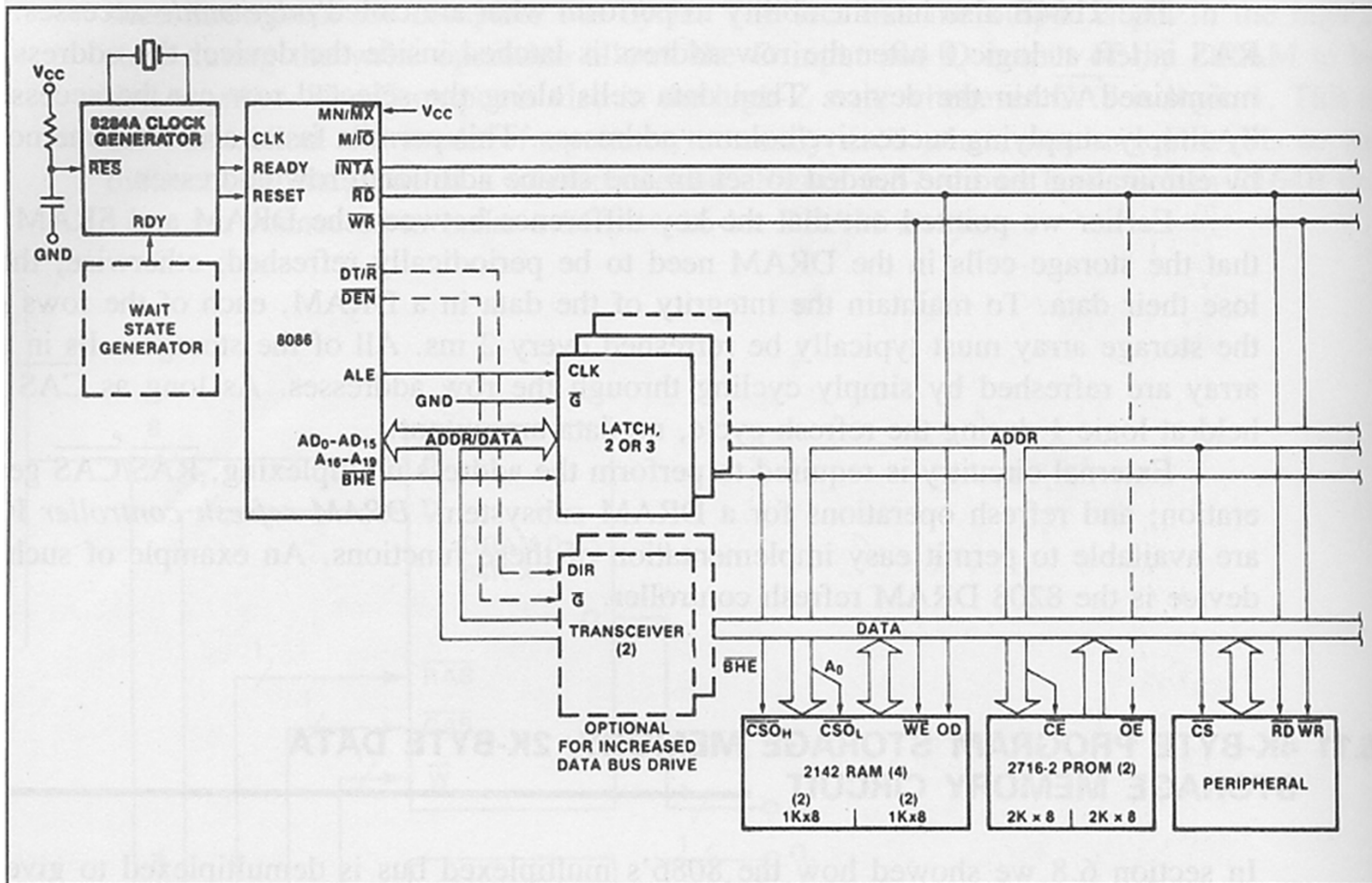


# 8088 Maximum Mode System Block Diagram

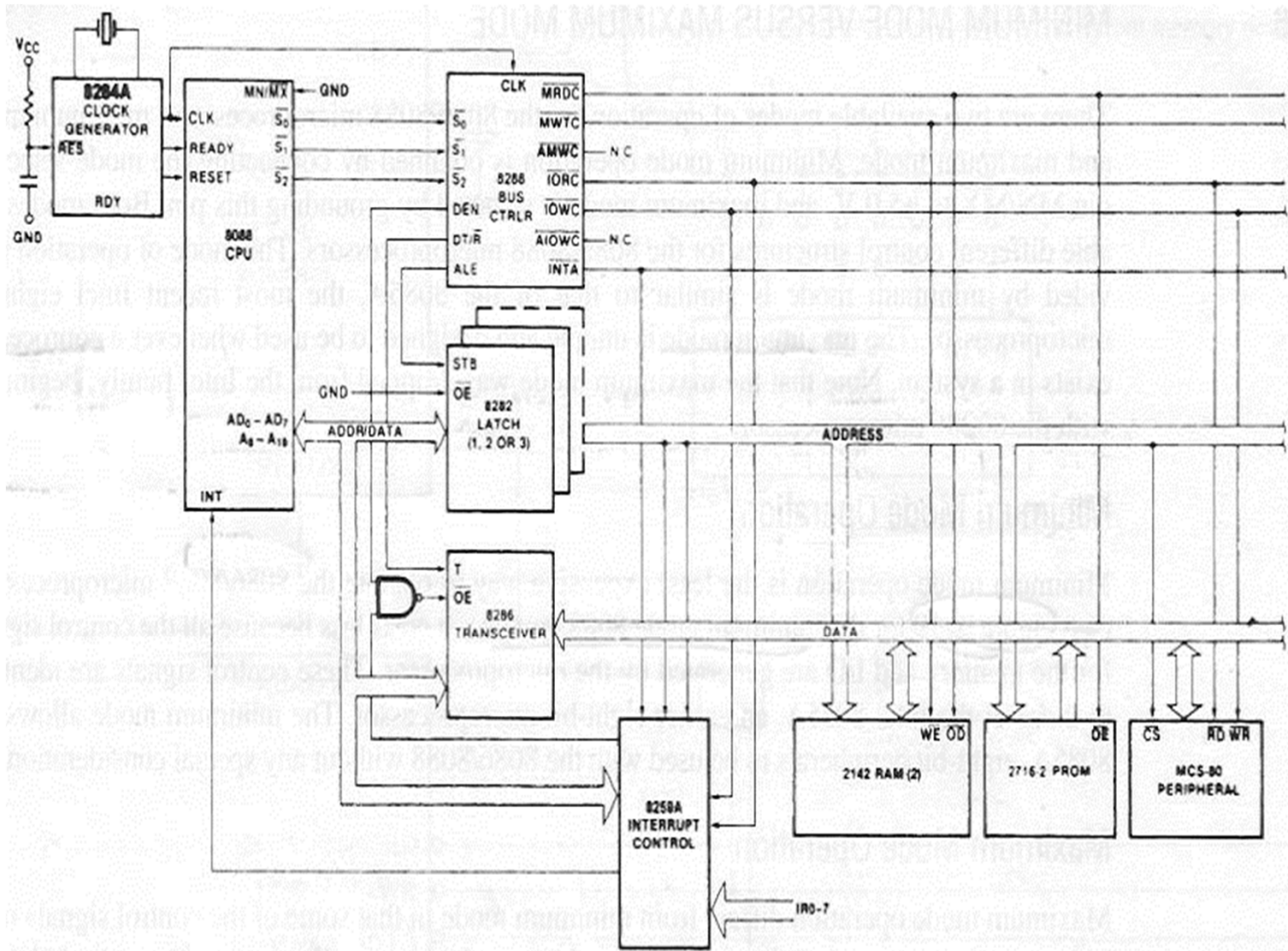


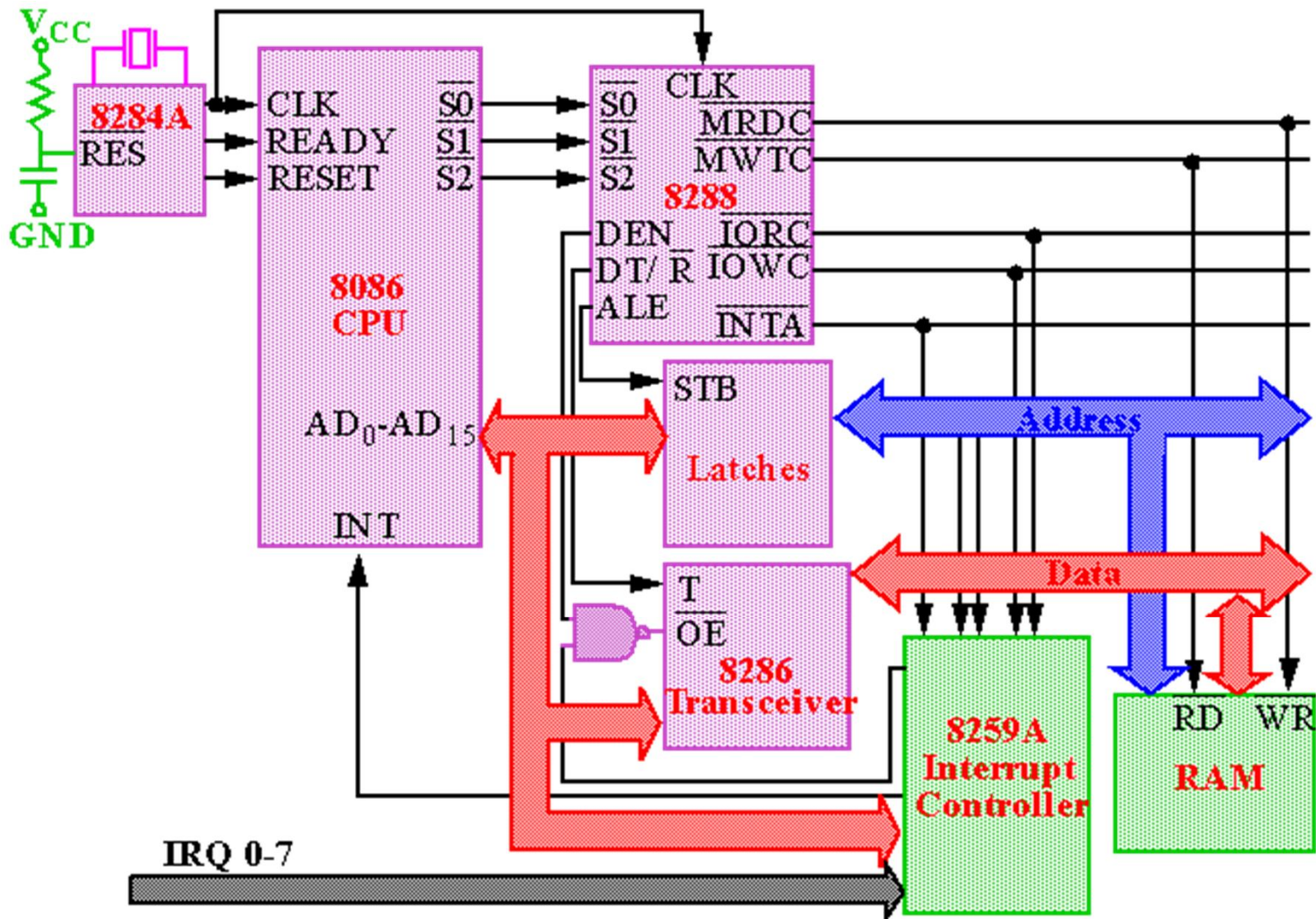
# 8086 Maximum Mode System simplified Block Diagram



# Memory Types

- Two basic types:
  - ROM: Read-only memory
  - RAM: Read-Write memory
- Four commonly used memories:
  - ROM
  - Flash (EEPROM)
  - [Difference between EEPROM and Flash](#)
  - Static RAM (SRAM)
  - Dynamic RAM (DRAM)

# Memory Chips

- The data pins are typically bi-directional in read-write memories.
  - The number of data pins is related to the size of the memory location. For example, an 8-bit wide (byte-wide) memory device has 8 data pins.
- Each memory device has at least one chip select (CS) or chip enable (CE) or select (S) pin that enables the memory device.
  - This enables read and/or write operations.
  - If more than one are present, then all must be 0 in order to perform a read or write.


# SRAM vs. DRAM

- SRAMs
  - SRAMs used for caches have access times as low as 10ns .
- DRAMs
  - SRAMs are limited in size (up to about 128Kb).
  - DRAMs are available in much larger sizes, e.g., 64M X 1.
  - DRAMs MUST be refreshed every 2 to 4 ms
  - Since they store their value on an integrated capacitor that loses charge over time.
  
  - What is SDRAM ?
  - What is EDO ?

# DRAM Addressing

- Dram has quite large addresses. Therefore it is not possible to provide all the signals at a time.
- Therefore, one way to provide address is to divide it into portions.
- We use signals CAS and RAS to select column and a Row address.
- First RAS is activated and the first half of address is latched on the row address latch.
- Second CAS is activated and second half of address is latched to the column address latch.

# DRAM Addressing

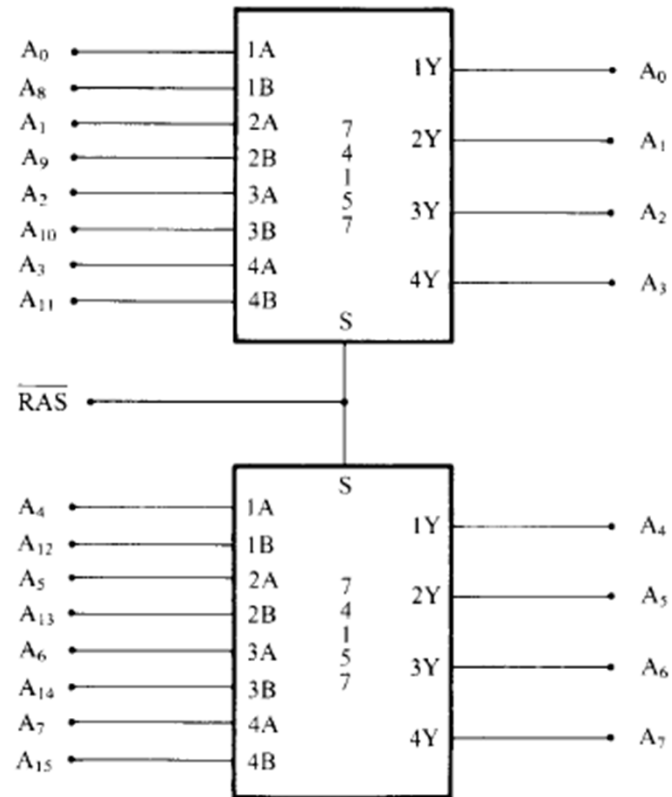


# Memory Address Decoding

- The processor can usually address a memory space that is much larger than the memory space covered by an individual memory chip.
- In order to splice a memory device into the address space of the processor, decoding is necessary.
- For example, the 8088 issues 20-bit addresses for a total of 1MB of memory address space.
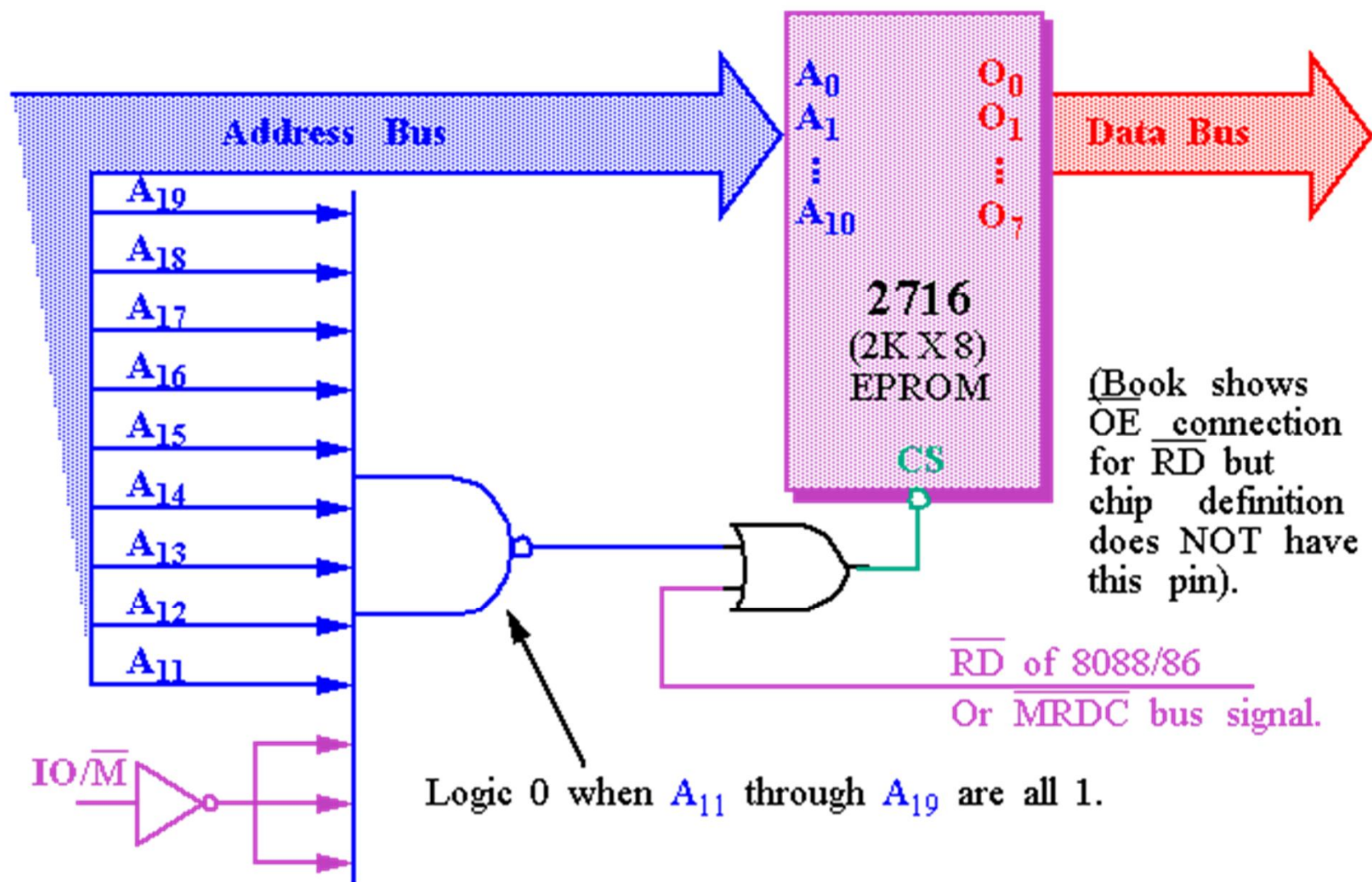
## Ex. Memory Address Decoding


- 2716 EPROM has only 2KB of memory and 11 address pins.
- A decoder can be used to decode the additional 9 address pins and allow the EPROM to be placed in any 2KB section of the 1MB address space.




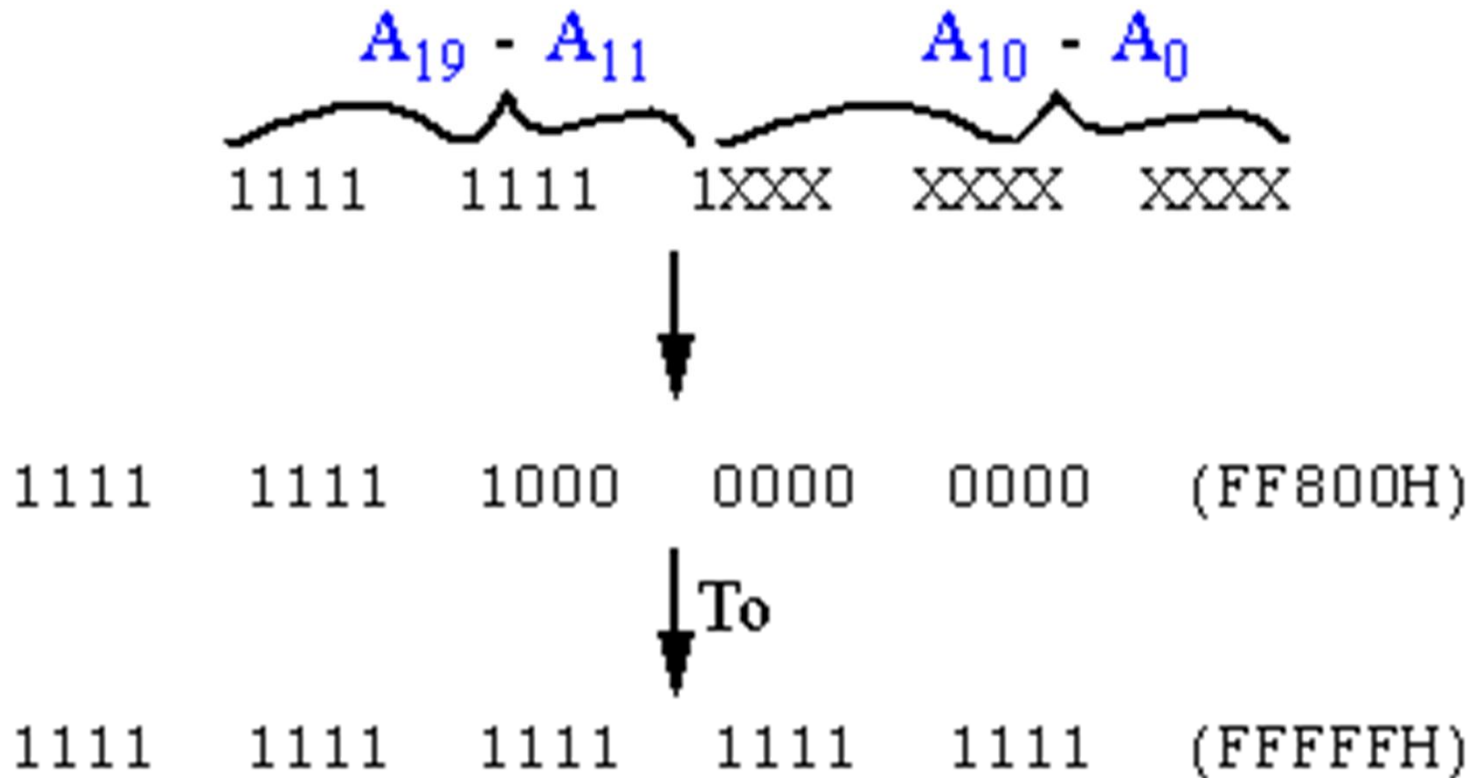
# Ex. Memory Address Decoding


- To determine the address range that a device is mapped into:



## Ex. Memory Address Decoding

- This 2KB memory segment maps into the reset location of the 8086/8088 (FFFF0H).
- NAND gate decoders are not often used. Rather the 3-to-8 Line Decoder (74LS138) is more common.


# 3-to-8 Line Decoder

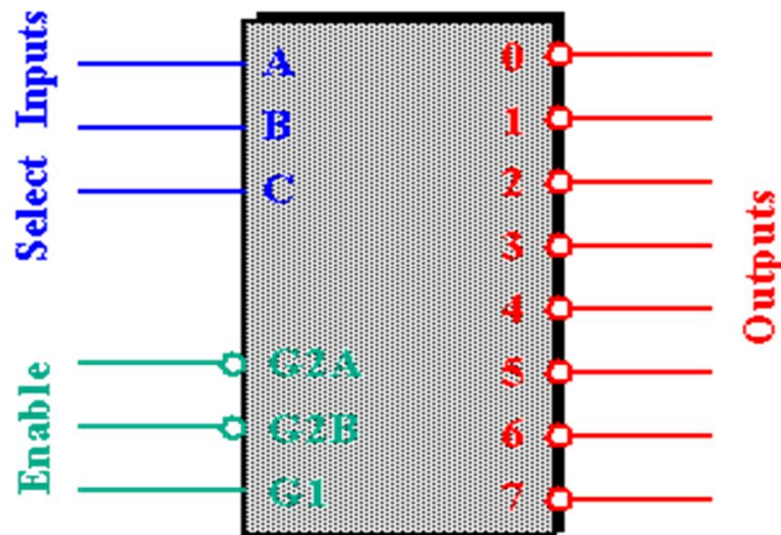

Inputs						Output							
Enable			Select										
G2A	G2B	G1	C	B	A	0	1	2	3	4	5	6	7
1	X	X	X	X	X	1	1	1	1	1	1	1	1
X	1	X	X	X	X	1	1	1	1	1	1	1	1
X	X	0	X	X	X	1	1	1	1	1	1	1	1
0	0	1	0	0	0	0	1	1	1	1	1	1	1
0	0	1	0	0	1	1	0	1	1	1	1	1	1
0	0	1	0	1	0	1	1	0	1	1	1	1	1
0	0	1	0	1	1	1	1	1	0	1	1	1	1
0	0	1	1	0	0	1	1	1	1	1	0	1	1
0	0	1	1	1	0	1	1	1	1	1	1	0	1
0	0	1	1	1	1	1	1	1	1	1	1	1	0


- G2A, G2B, and G1 must be active.
- Each output of the decoder can be attached to an 2764 EPROM ( 8K X 8 ).

# EPROM 2764 x 8

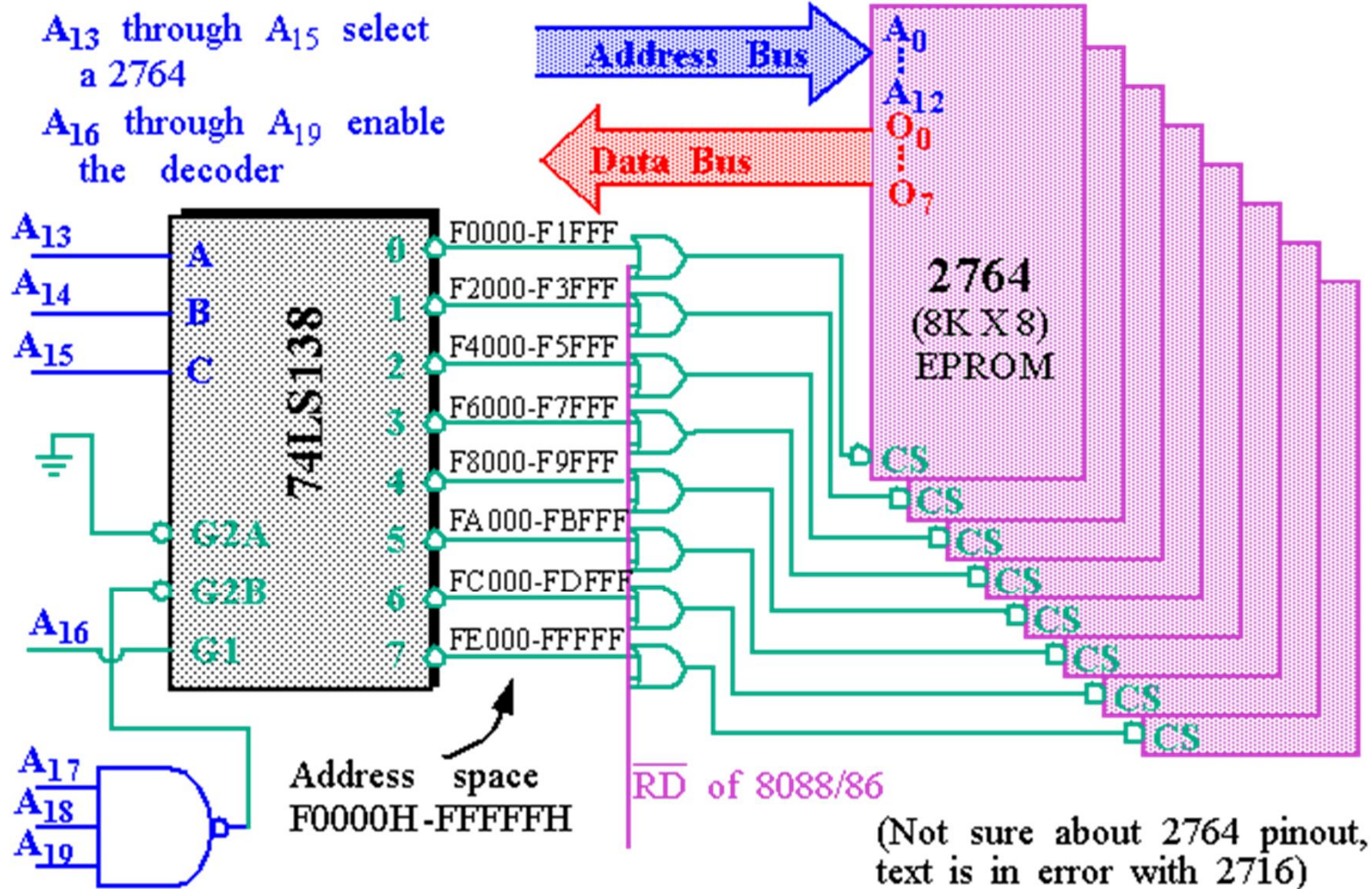



# 74LS139 Dual Decoder

 

Inputs			Outputs			
$\overline{E}$	A	B	$\overline{Y}_0$	$\overline{Y}_1$	$\overline{Y}_2$	$\overline{Y}_3$
0	0	0	0	1	1	1
0	0	1	1	0	1	1
0	1	0	1	1	0	1
0	1	1	1	1	1	0
1	X	X	1	1	1	1

# 74LS139 Dual Decoder

