 


Advanced Digital Design with the Verilog HDL



M. D. Ciletti

Department
of
Electrical and Computer Engineering
University of Colorado
Colorado Springs, Colorado

ciletti@vlsic.uccs.edu

Draft: Chap 7: Design and Synthesis of Datapath Controllers

REV 9/22/2003

Copyright 2000, 2002, 2003. These notes are solely for classroom use by the instructor. No part of these notes may be copied, reproduced, or distributed to a third party, including students, in any form without the written permission of the author.

Note to the instructor: These slides are provided solely for classroom use in academic institutions by the instructor using the text, *Advance Digital Design with the Verilog HDL* by Michael Ciletti, published by Prentice Hall. This material may not be used in off-campus instruction, resold, reproduced or generally distributed in the original or modified format for any purpose without the permission of the Author. This material may not be placed on any server or network, and is protected under all copyright laws, as they currently exist. I am providing these slides to you subject to your agreeing that you will not provide them to your students in hardcopy or electronic format or use them for off-campus instruction of any kind. Please email to me your agreement to these conditions.

I will greatly appreciate your assisting me by calling to my attention any errors or any other revisions that would enhance the utility of these slides for classroom use.

Course Overview

- Review of combinational and sequential logic design
- Modeling and verification with hardware description languages
- Introduction to synthesis with HDLs
- Programmable logic devices
- State machines, datapath controllers, RISC CPU
- Architectures and algorithms for computation and signal processing
- Synchronization across clock domains
- Timing analysis
- Fault simulation and testing, JTAG, BIST

Partitioned Sequential Machine

 


Figure 7.1 State machine controller for a datapath.

- Partitioning clarifies the architecture and reduces the complexity of design tasks.

Application-Driven Architecture

 


Figure 7.2 Application-driven architecture, instruction set, and control sequence for a datapath controller.

Control Units for a Partitioned Sequential Machine

- Orchestrate, coordinate, and synchronize the operations of datapath units
- Generate the signals that load, read and shift the contents of storage registers
- Fetch instructions and data from memory
- Store data in memory
- Steer signals through muxes
- Control three-state devices
- Control the operations of ALUs and other complex datapath units.

Sequential Machine

Common clock synchronizes the activities of the controller and datapath functional units

Descriptions of functional units:

- Datapath units are commonly described by data flow graphs
- Control units are commonly modeled by state transition graphs and/or ASM charts for finite state machines.

Partitioned sequential machines can be modeled by a FSMD chart, a combined control-data flow graph, which expresses datapath operations in the context of a STG.

ASMD chart: links and ASM chart for a control unit to the operations of the datapath that it controls.

Design Example: Binary Counter

- Synchronous 4-bit binary counter
- Incremented by a count of 1 at each active edge of the clock
- Wrap count to 0 when the count reaches 1111_2 .

Implicit machine: register transfer operation ($count \leq count + 1$) conditionally, in every clock cycle, depending on *enable*

Alternative Design: Partitioned machine: an architecture of separate datapath and control units,

Functional elements of the architecture of the datapath unit:

- 4-bit register to hold *count*,
- mux that steers either *count* or the sum of *count* and 0001_2 to the input of the register
- a 4-bit adder to increment *count*
- *enable* must be asserted for counting to occur
- *rst* overrides all activity and drives the count to a value of 0000_2 .

rst must be de-asserted and *enable* must be asserted for the machine to begin counting to begin and to continue counting.

Design Example: Binary Counter (Cont.)

Note: the control unit passes *enable* directly to the datapath unit

 


Figure 7.3 Architecture for a synchronous 4-bit binary counter.

Design Example: Binary Counter (Cont.)

Alternative Design: view the counter itself as an explicit state machine

Note: the size of the graph increases with the width of the datapath.

 


Figure 7.4 Simplified state transition graph for a synchronous 4-bit binary counter.

Design Example: Binary Counter (Cont.)

Comparisons:

- Implicit State Machine
- Simplest description
- Suppresses structural detail

- Partitioned Machine
- Has the most structural detail
- Has a simple controller
- State of the datapath register does not influence the design

STG-based Design

- Required a detailed STG
- State machine as a state for each state of the counter
- and lead to a state machine having 16 states

Design Example: Binary Counter (Cont.)

Alternative Design: The counter's *activity* has one state, *S_running*.

ASM Chart:

 


Figure 7.5 ASM chart for a synchronous 4-bit binary counter.

Design Example: Binary Counter (Cont.)

Alternative Design:

- Partition the machine into a control unit and a datapath unit
- Design an RTL behavioral model for the datapath unit, rather than a structural model
- Separates the design of the control unit from the design (and synthesis) of the datapath unit
- Simplifies the description of the datapath unit.

 


Figure 7.6 ASMD chart for a datapath unit, a synchronous 4-bit binary counter, controlled by a state machine.

Design Example: Binary Counter (Cont.)

Example 7.1

```
module Binary_Counter_Part_RTL (count, enable, clk, rst);
    parameter      size = 4;
    output [size -1: 0]   count;
    input          enable;
    input          clk, rst;
    wire           enable_DP;

    Control_Unit M0 (enable_DP, enable, clk, rst);
    Datapath_Unit M1 (count, enable_DP, clk, rst);
endmodule

module Control_Unit (enable_DP, enable, clk, rst);
    output      enable_DP;
    input       enable;
    input       clk, rst;          // Not needed
    wire        enable_DP = enable; // pass through
endmodule
```

```
module Datapath_Unit (count, enable, clk, rst);
    parameter size = 4;
    output      [size-1: 0] count;
    input       enable;
    input       clk, rst;
    reg        count;
    wire      [size-1: 0] next_count;

    always @ (posedge clk)
        if (rst == 1) count <= 0;
        else if (enable == 1) count <= next_count(count);

    function   [size-1: 0]   next_count;
        input      [size-1: 0]   count;
        begin
            next_count = count + 1;
        end
    endfunction
endmodule
```

 


Figure 7.7 Simulation results for *Binary_Counter_RTL*, a synchronous 4-bit binary counter controlled by a state machine.

Design Example: Binary Counter (Cont.)

Example: *Binary_Counter_Part_RTL_by_3* increments its count every third clock cycle. Only the control unit must change. Implicit Moore machine (See Pm 6.12):

```
module Control_Unit_by_3 (enable_DP, enable, clk, rst);
    output      enable_DP;
    input       enable;
    input       clk, rst;      // Not needed
    reg        enable_DP;

    always begin: Cycle_by_3
        @ (posedge clk) enable_DP <= 0;
        if ((rst == 1) || (enable != 1)) disable Cycle_by_3; else
            @ (posedge clk)
                if ((rst == 1) || (enable != 1)) disable Cycle_by_3; else
                    @ (posedge clk)
                        if ((rst == 1) || (enable != 1)) disable Cycle_by_3;
                        else enable_DP <= 1;
    end // Cycle_by_3
endmodule
```

 


Figure 7.8 Simulation results for *Binary_Counter_Part_RTL_by_3* with a control unit to increment the datapath counter every third cycle.

Synthesis Result:

Note: The synthesized circuit takes one extra cycle to recover from a reset condition


 


Figure 7.9 Circuit synthesized for *Control_Unit_by_3*

RISC Stored Program Machine

 

RISC SPM: Program-Directed Operation

- Fetch instruction from memory
- Decode instruction
- Execute instruction
 - ALU operations
 - Update storage registers
 - Update program counter (PC)
 - Update the instruction register (IR)
 - Update the address register (ADD_R)
 - Update memory
 - Control datapaths

RISC SPM: ALU

Instruction

ADD

SUB

AND

NOT

Action

Adds the datapaths to form *data_1 + data_2*

Subtracts the datapaths to form *data_1 - data_2*

Takes the bitwise-and of the datapaths, *data_1 & data_2*

Takes the bitwise Boolean complement of *data_1*

RISC SPM: Control Unit

Functions of the control unit:

- (1) determine when to load registers
- (2) select the path of data through the multiplexers
- (3) determine when data should be written to memory
- (4) control the three-state busses in the architecture.

RISC SPM: Control Signals

<u>Control Signal</u>	<u>Action</u>
<i>Load_Add_Reg</i>	Loads the address register
<i>Load_PC</i>	Loads <i>Bus_2</i> to the program counter
<i>Load_IR</i>	Loads <i>Bus_2</i> to the instruction register
<i>Inc_PC</i>	Increments the program counter
<i>Sel_Bus_1_Mux</i>	Selects among the <i>Program_Counter</i> , <i>R0</i> , <i>R1</i> , <i>R2</i> , and <i>R3</i> to drive <i>Bus_1</i>
<i>Sel_Bus_2_Mux</i>	Selects among <i>Alu_out</i> , <i>Bus_1</i> , and memory to drive <i>Bus_2</i>

<i>Load_R0</i>	Loads general purpose register <i>R0</i>
<i>Load_R1</i>	Loads general purpose register <i>R1</i>
<i>Load_R2</i>	Loads general purpose register <i>R2</i>
<i>Load_R3</i>	Loads general purpose register <i>R3</i>
<i>Load_Reg_Y</i>	Loads <i>Bus_2</i> to the register <i>Reg_Y</i>
<i>Load Reg_Z</i>	Stores output of <i>ALU</i> in register <i>Reg_Z</i>
<i>write</i>	Loads <i>Bus_1</i> into the <i>SRAM</i> memory at the location specified by the address register

RISC SPM: Instruction Set

- Note: The design of the controller depends on the processor's instruction set.
- RISC SPM has two types of instructions.

Short Instruction

opcode				source		destination	
0	0	1	0	0	1	1	0

Long Instruction

opcode				source			destination	
0	1	1	0	1	0	don't care	don't care	
address								
0	0	0	1	1	1	0	1	

RISC SPM: Instruction Mnemonics

<u>Single-Byte Instruction</u>	<u>Action</u>
NOP	No operation is performed; all registers retain their values The addresses of the source and destination register are don't-cares, they have no effect.
ADD	Adds the contents of the source and destination registers and stores the result into the destination register.
AND	Forms the bitwise-and of the contents of the source and destination registers and stores the result into the destination register.
NOT	Forms the bitwise complement of the content of the source register and stores the result into the destination register.
SUB	Subtracts the content of the source register from the destination register and stores the result into the destination register.

RISC SPM: Instruction Mnemonics (Cont.)

<u>Two-Byte Instruction</u>	<u>Action</u>
RD	Fetches a memory word from the location specified by the second byte and loads the result into the destination register. The source register bits are don't-cares, i.e., , unused.
WR	Writes the contents of the source register to the word in memory specified by the address held in the second byte. The destination register bits are don't-cares, i.e., , unused.
BR	Branches the activity flow by loading the program counter with the word at the location (address) specified by the second byte of the instruction. The source and destination bits are don't-cares, i.e., , unused.
BRZ	Branches the activity flow by loading the program counter with the word at the location (address) specified by the second byte of the instruction if the zero flag register is asserted.

RISC SPM: Summary of Instructions and Opcodes

Instr	Instruction Word			Action
	opcode	src	dest	
NOP	0000	??	??	none
ADD	0001	src	dest	dest <= src + dest
SUB	0010	src	dest	dest <= dest - src
AND	0011	src	dest	dest <= src && dest
NOT	0100	src	dest	dest <= ~src
RD*	0101	??	dest	dest <= memory[Add_R]
WR*	0110	src	??	memory[Add_R] <= src
BR*	0111	??	??	PC <= memory[Add_R]
BRZ*	1000	??	??	PC <= memory[Add_R]
HALT	1111	??	??	Halts execution until reset

* Requires a second word of data; ? denotes a don't care.

RISC SPM: Program Counter

Holds the address of the next instruction to be executed.

- When the external reset is asserted, the program counter is loaded with 0, indicating that the bottom of memory holds the next instruction that will be fetched.
- Under the action of the clock, for single-cycle instructions, the instruction at the address in the program counter is loaded into the instruction register and the program counter is incremented.
- An instruction decoder determines the resulting action on the datapaths and the ALU.
- A long instruction is held in two bytes, and an additional clock cycle is required to execute the instruction.
- In the second cycle of execution, the second byte is fetched from memory at the address held in the program counter, then the instruction is completed.

RISC SPM: Controller Design

Three phases of operation: *fetch*, *decode*, and *execute*.


- Fetching: Retrieves an instruction from memory (2 clock cycles)
- Decoding: Decodes the instruction, manipulates datapaths, and loads registers (1 cycle)
- Execution generates the results of the instruction (0, 1, or 2 cycles)


RISC SPM: Controller States


- S_idle** State entered after reset is asserted. No action.
- S_fet1** Load the address register with the contents of the program counter.
(Note: *PC* is initialized to the starting address by the reset action.)
The state is entered at the first active clock after reset is de-asserted, and is revisited after a *NOP* instruction is decoded.
- S_fet2** Load the instruction register with the word addressed by the address register, and increment the program counter to point to the next location in memory, in anticipation of the next instruction or data fetch.
- S_dec** Decode the instruction register and assert signals to control datapaths and register transfers.
- S_ex1** Execute the *ALU* operation for a single-byte instruction, conditionally assert the zero flag, and load the destination register.


RISC SPM: Controller States (Cont.)


- S_{rd1} Load the address register with the second byte of an *RD* instruction, and increment the *PC*.
- S_{rd2} Load the destination register with the memory word addressed by the byte loaded in S_{rd1} .
- S_{wr1} Load the address register with the second byte of a *WR* instruction, and increment the *PC*.
- S_{wr2} Load the destination register with the memory word addressed by the byte loaded in S_{wr1} .
- S_{br1} Load the address register with the second byte of a *BR* instruction, and increment the *PC*.
- S_{br2} Load the program counter with the memory word addressed by the byte loaded in S_{br1} .
- S_{halt} Default state to trap failure to decode a valid instruction.

 

 

 

 

 

S_id
0

S

1 l

S_d
3

RISC SPM: Verilog Model

```
module RISC_SPM (clk, rst);
    parameter word_size = 8;
    parameter Sel1_size = 3;
    parameter Sel2_size = 2;
    wire [Sel1_size-1: 0] Sel_Bus_1_Mux;
    wire [Sel2_size-1: 0] Sel_Bus_2_Mux;

    input clk, rst;

    // Data Nets
    wire zero;
    wire [word_size-1: 0] instruction, address, Bus_1, mem_word;

    // Control Nets
    wire Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC, Load_IR;
    wire Load_Add_R, Load_Reg_Y, Load_Reg_Z;
    wire write;
```

Processing_Unit M0_Processor

(instruction, zero, address, Bus_1, mem_word, Load_R0, Load_R1,
Load_R2, Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux, Load_IR,
Load_Add_R, Load_Reg_Y,
Load_Reg_Z, Sel_Bus_2_Mux, clk, rst);

Control_Unit M1_Controller (Load_R0, Load_R1, Load_R2, Load_R3,
Load_PC, Inc_PC, Sel_Bus_1_Mux, Sel_Bus_2_Mux , Load_IR,
Load_Add_R, Load_Reg_Y, Load_Reg_Z, write, instruction, zero,
clk, rst);

Memory_Unit M2_SRAM (

.data_out(mem_word),
.data_in(Bus_1),
.address(address),
.clk(clk),
.write(write));

endmodule

```
module Processing_Unit (instruction, Zflag, address, Bus_1, mem_word,  
Load_R0, Load_R1, Load_R2,  
Load_R3, Load_PC, Inc_PC, Sel_Bus_1_Mux, Load_IR, Load_Add_R,  
Load_Reg_Y, Load_Reg_Z,  
Sel_Bus_2_Mux, clk, rst);  
  
parameter word_size = 8;  
parameter op_size = 4;  
parameter Sel1_size = 3;  
parameter Sel2_size = 2;  
  
output [word_size-1: 0] instruction, address, Bus_1;  
output Zflag;  
  
input [word_size-1: 0] mem_word;  
input Load_R0, Load_R1, Load_R2, Load_R3, Load_PC,  
Inc_PC;  
input [Sel1_size-1: 0] Sel_Bus_1_Mux;  
input [Sel2_size-1: 0] Sel_Bus_2_Mux;  
input Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z;  
input clk, rst;
```

```
wire          Load_R0, Load_R1, Load_R2, Load_R3;
wire [word_size-1: 0]    Bus_2;
wire [word_size-1: 0]    R0_out, R1_out, R2_out, R3_out;
wire [word_size-1: 0]    PC_count, Y_value, alu_out;
wire          alu_zero_flag;
wire [op_size-1 : 0]
    opcode = instruction [word_size-1: word_size-op_size];

Register_Unit      R0  (R0_out, Bus_2, Load_R0, clk, rst);
Register_Unit      R1  (R1_out, Bus_2, Load_R1, clk, rst);
Register_Unit      R2  (R2_out, Bus_2, Load_R2, clk, rst);
Register_Unit      R3  (R3_out, Bus_2, Load_R3, clk, rst);
Register_Unit      Reg_Y (Y_value, Bus_2, Load_Reg_Y, clk, rst);
D_flop            Reg_Z  (Zflag, alu_zero_flag, Load_Reg_Z, clk, rst);
Address_Register  Add_R  (address, Bus_2, Load_Add_R, clk, rst);
Instruction_Register IR    (instruction, Bus_2, Load_IR, clk, rst);
Program_Counter   PC    (PC_count, Bus_2, Load_PC, Inc_PC,
                        clk, rst);
```

```
Multiplexer_5ch      Mux_1  (Bus_1, R0_out, R1_out, R2_out, R3_out,
                           PC_count, Sel_Bus_1_Mux);
Multiplexer_3ch      Mux_2  (Bus_2, alu_out, Bus_1, mem_word,
                           Sel_Bus_2_Mux);
Alu_RISC            ALU(alu_zero_flag, alu_out, Y_value, Bus_1, opcode);
endmodule
```

```
module Register_Unit (data_out, data_in, load, clk, rst);
  parameter    word_size = 8;
  output [word_size-1: 0]  data_out;
  input  [word_size-1: 0]  data_in;
  input          load;
  input          clk, rst;
  reg           data_out;

  always @ (posedge clk or negedge rst)
    if (rst == 0) data_out <= 0; else if (load) data_out <= data_in;
endmodule
```

```
module D_flop (data_out, data_in, load, clk, rst);
    output      data_out;
    input       data_in;
    input       load;
    input      clk, rst;
    reg        data_out;

    always @ (posedge clk or negedge rst)
        if (rst == 0) data_out <= 0; else if (load == 1) data_out <= data_in;
endmodule

module Address_Register (data_out, data_in, load, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0]  data_out;
    input  [word_size-1: 0]  data_in;
    input          load, clk, rst;
    reg            data_out;
    always @ (posedge clk or negedge rst)
        if (rst == 0) data_out <= 0; else if (load) data_out <= data_in;
endmodule
```

```
module Instruction_Register (data_out, data_in, load, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0] data_out;
    input [word_size-1: 0] data_in;
    input load;
    input clk, rst;
    reg data_out;
    always @ (posedge clk or negedge rst)
        if (rst == 0) data_out <= 0; else if (load) data_out <= data_in;
endmodule
```

```
module Program_Counter (count, data_in, Load_PC, Inc_PC, clk, rst);
    parameter word_size = 8;
    output [word_size-1: 0] count;
    input [word_size-1: 0] data_in;
    input Load_PC, Inc_PC;
    input clk, rst;
    reg count;
    always @ (posedge clk or negedge rst)
        if (rst == 0) count <= 0; else if (Load_PC) count <= data_in; else if
        (Inc_PC) count <= count +1;
endmodule
```

```
module Multiplexer_5ch (mux_out, data_a, data_b, data_c, data_d, data_e,
sel);
  parameter word_size = 8;
  output [word_size-1: 0] mux_out;
  input [word_size-1: 0] data_a, data_b, data_c, data_d, data_e;
  input [2: 0] sel;

  assign mux_out = (sel == 0) ? data_a: (sel == 1)
    ? data_b : (sel == 2)
    ? data_c: (sel == 3)
    ? data_d : (sel == 4)
    ? data_e : 'bx;
endmodule
```

```
module Multiplexer_3ch (mux_out, data_a, data_b, data_c, sel);
parameter word_size = 8;
output [word_size-1: 0] mux_out;
input [word_size-1: 0] data_a, data_b, data_c;
input [1: 0] sel;

assign mux_out = (sel == 0) ? data_a: (sel == 1) ? data_b : (sel == 2) ?
data_c: 'bx;
endmodule
```

```
/*ALU Instruction      Action
ADD                  Adds the datapaths to form data_1 + data_2.
SUB                  Subtracts the datapaths to form data_1 - data_2.
AND                  Takes the bitwise-and of the datapaths, data_1 & data_2.
NOT                 Takes the bitwise Boolean complement of data_1.
*/
// Note: the carries are ignored in this model.
```

```
module Alu_RISC (alu_zero_flag, alu_out, data_1, data_2, sel);
parameter word_size = 8;
parameter op_size = 4;
// Opcodes
parameter NOP      = 4'b0000;
parameter ADD       = 4'b0001;
parameter SUB       = 4'b0010;
parameter AND       = 4'b0011;
parameter NOT      = 4'b0100;
parameter RD        = 4'b0101;
parameter WR        = 4'b0110;
parameter BR        = 4'b0111;
parameter BRZ      = 4'b1000;
```

```
output alu_zero_flag;
output [word_size-1: 0] alu_out;
input [word_size-1: 0] data_1, data_2;
input [op_size-1: 0] sel;
reg alu_out;

assign alu_zero_flag = ~|alu_out;
always @(sel or data_1 or data_2)
case (sel)
    NOP:   alu_out = 0;
    ADD:   alu_out = data_1 + data_2; // Reg_Y + Bus_1
    SUB:   alu_out = data_2 - data_1;
    AND:   alu_out = data_1 & data_2;
    NOT:   alu_out = ~ data_2;     // Gets data from Bus_1
    default: alu_out = 0;
endcase
endmodule
```

```
module Control_Unit (
    Load_R0, Load_R1,
    Load_R2, Load_R3,
    Load_PC, Inc_PC,
    Sel_Bus_1_Mux, Sel_Bus_2_Mux,
    Load_IR, Load_Add_R, Load_Reg_Y, Load_Reg_Z,
    write, instruction, zero, clk, rst);

parameter word_size = 8, op_size = 4, state_size = 4;
parameter src_size = 2, dest_size = 2, Sel1_size = 3, Sel2_size = 2;
// State Codes
parameter S_idle = 0, S_fet1 = 1, S_fet2 = 2, S_dec = 3;
parameter S_ex1 = 4, S_rd1 = 5, S_rd2 = 6;
parameter S_wr1 = 7, S_wr2 = 8, S_br1 = 9, S_br2 = 10, S_halt = 11;
// Opcodes
parameter NOP = 0, ADD = 1, SUB = 2, AND = 3, NOT = 4;
parameter RD = 5, WR = 6, BR = 7, BRZ = 8;
// Source and Destination Codes
parameter R0 = 0, R1 = 1, R2 = 2, R3 = 3;
```

```
output Load_R0, Load_R1, Load_R2, Load_R3;
output Load_PC, Inc_PC;
output [Sel1_size-1: 0] Sel_Bus_1_Mux;
output Load_IR, Load_Add_R;
output Load_Reg_Y, Load_Reg_Z;
output [Sel2_size-1: 0] Sel_Bus_2_Mux;
output write;
input [word_size-1: 0] instruction;
input zero;
input clk, rst;

reg [state_size-1: 0] state, next_state;
reg Load_R0, Load_R1, Load_R2, Load_R3, Load_PC, Inc_PC;
reg Load_IR, Load_Add_R, Load_Reg_Y;
reg Sel_ALU, Sel_Bus_1, Sel_Mem;
reg Sel_R0, Sel_R1, Sel_R2, Sel_R3, Sel_PC;
reg Load_Reg_Z, write;
reg err_flag;

wire [op_size-1: 0] opcode = instruction [word_size-1: word_size - op_size];
wire [src_size-1: 0] src = instruction [src_size + dest_size -1: dest_size];
wire [dest_size-1: 0] dest = instruction [dest_size -1: 0];
```

```
// Mux selectors
assign Sel_Bus_1_Mux[Sel1_size-1: 0] = Sel_R0 ? 0:
                                              Sel_R1 ? 1:
                                              Sel_R2 ? 2:
                                              Sel_R3 ? 3:
                                              Sel_PC ? 4: 3'bx; // 3-bits, sized number

assign Sel_Bus_2_Mux[Sel2_size-1: 0] = Sel_ALU ? 0:
                                              Sel_Bus_1 ? 1:
                                              Sel_Mem ? 2: 2'bx;

always @ (posedge clk or negedge rst) begin: State_transitions
  if (rst == 0) state <= S_idle; else state <= next_state; end
```

```
/* always @ (state or instruction or zero) begin: Output_and_next_state
```

Note: The above event control expression leads to incorrect operation. The state transition causes the activity to be evaluated once, then the resulting instruction change causes it to be evaluated again, but with the residual value of *opcode*. On the second pass the value seen is the value *opcode* had before the state change, which results in *Sel_PC* = 0 in state 3, which will cause a return to state 1 at the next clock. Finally, *opcode* is changed, but this does not trigger a re-evaluation because it is not in the event control expression. So, the caution is to be sure to use *opcode* in the event control expression. That way, the final execution of the behavior uses the value of *opcode* that results from the state change, and leads to the correct value of *Sel_PC*.

```
*/
```

```
always @ (state or opcode or src or dest or zero)
begin: Output_and_next_state
    Sel_R0 = 0;    Sel_R1 = 0;      Sel_R2 = 0;
    Sel_R3 = 0;    Sel_PC = 0;
    Load_R0 = 0;   Load_R1 = 0;     Load_R2 = 0;
    Load_R3 = 0;   Load_PC = 0;

    Load_IR = 0;   Load_Add_R = 0; Load_Reg_Y = 0; Load_Reg_Z = 0;
    Inc_PC = 0;
    Sel_Bus_1 = 0;
    Sel_ALU = 0;
    Sel_Mem = 0;
    write = 0;
    err_flag = 0;   // Used for de-bug in simulation
    next_state = state;
```

```
case (state)
    S_idle:      next_state = S_fet1;

    S_fet1: begin
        next_state = S_fet2;
        Sel_PC = 1;
        Sel_Bus_1 = 1;
        Load_Add_R = 1;
    end
    S_fet2: begin
        next_state = S_dec;
        Sel_Mem = 1;
        Load_IR = 1;
        Inc_PC = 1;
    end
```

```
S_dec: case (opcode)
        NOP: next_state = S_fet1;
        ADD, SUB, AND: begin
            next_state = S_ex1;
            Sel_Bus_1 = 1;
            Load_Reg_Y = 1;
            case (src)
                R0:      Sel_R0 = 1;
                R1:      Sel_R1 = 1;
                R2:      Sel_R2 = 1;
                R3:      Sel_R3 = 1;
                default: err_flag = 1;
            endcase
        end // ADD, SUB, AND
```

```
NOT: begin
    next_state = S_fet1;
    Load_Reg_Z = 1;
    Sel_Bus_1 = 1;
    Sel_ALU = 1;
    case (src)
        R0:      Sel_R0 = 1;
        R1:      Sel_R1 = 1;
        R2:      Sel_R2 = 1;
        R3:      Sel_R3 = 1;
        default : err_flag = 1;
    endcase
    case (dest)
        R0:      Load_R0 = 1;
        R1:      Load_R1 = 1;
        R2:      Load_R2 = 1;
        R3:      Load_R3 = 1;
        default: err_flag = 1;
    endcase
end // NOT
```

RD: begin

```
next_state = S_rd1;  
Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;  
end // RD
```

WR: begin

```
next_state = S_wr1;  
Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;  
end // WR
```

BR: begin

```
next_state = S_br1;  
Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;  
end // BR
```

```
BRZ: if (zero == 1) begin
    next_state = S_br1;
    Sel_PC = 1; Sel_Bus_1 = 1; Load_Add_R = 1;
end // BRZ
else begin
    next_state = S_fet1;
    Inc_PC = 1;
end
    default : next_state = S_halt;
endcase // (opcode)
```

```
S_ex1: begin
    next_state = S_fet1;
    Load_Reg_Z = 1;
    Sel_ALU = 1;
    case (dest)
        R0: begin Sel_R0 = 1; Load_R0 = 1; end
        R1: begin Sel_R1 = 1; Load_R1 = 1; end
        R2: begin Sel_R2 = 1; Load_R2 = 1; end
        R3: begin Sel_R3 = 1; Load_R3 = 1; end
        default : err_flag = 1;
    endcase
end
```

```
S_rd1: begin
    next_state = S_rd2;
    Sel_Mem = 1;
    Load_Add_R = 1;
    Inc_PC = 1;
end
```

```
S_wr1: begin
    next_state = S_wr2;
    Sel_Mem = 1;
    Load_Add_R = 1;
    Inc_PC = 1;
end

S_rd2: begin
    next_state = S_fet1;
    Sel_Mem = 1;
    case (dest)
        R0:      Load_R0 = 1;
        R1:      Load_R1 = 1;
        R2:      Load_R2 = 1;
        R3:      Load_R3 = 1;
    default:   err_flag = 1;
    endcase
end
```

```
S_wr2: begin
    next_state = S_fet1;
    write = 1;
    case (src)
        R0:      Sel_R0 = 1;
        R1:      Sel_R1 = 1;
        R2:      Sel_R2 = 1;
        R3:      Sel_R3 = 1;
        default : err_flag = 1;
    endcase
end

S_br1:      begin next_state = S_br2; Sel_Mem = 1;
Load_Add_R = 1; end
S_br2:      begin next_state = S_fet1; Sel_Mem = 1; Load_PC =
1; end
S_halt:     next_state = S_halt;
default:     next_state = S_idle;
endcase
end
endmodule
```

```
module Memory_Unit (data_out, data_in, address, clk, write);
    parameter word_size = 8;
    parameter memory_size = 256;

    output [word_size-1: 0] data_out;
    input [word_size-1: 0] data_in;
    input [word_size-1: 0] address;
    input clk, write;
    reg [word_size-1: 0] memory [memory_size-1: 0];

    assign data_out = memory[address];

    always @ (posedge clk)
        if (write) memory[address] = data_in;
endmodule
```

RISC SPM: Program Execution

- (1) Read memory and load the data into the registers of the processor
- (2) Execute subtraction to decrement a loop counter
- (3) Add register contents while executing the loop
- (4) Branch to a halt when the loop index is 0

```
module test_RISC_SPM ();
    reg rst;
    wire clk;
    parameter word_size = 8;
    reg [8: 0] k;

    Clock_Unit M1 (clk);
    RISC_SPM M2 (clk, rst);
```

```
// define probes
wire [word_size-1: 0] word0, word1, word2, word3, word4, word5, word6;
wire [word_size-1: 0] word7, word8, word9, word10, word11,
    word12, word13;
wire [word_size-1: 0] word14;

wire [word_size-1: 0] word128, word129, word130, word131,
    word132, word255;
wire [word_size-1: 0] word133, word134, word135, word136, word137;
wire [word_size-1: 0] word138, word139, word140;
```

```
assign word0 = M2.M2_SRAM.memory[0];
assign word1 = M2.M2_SRAM.memory[1];
assign word2 = M2.M2_SRAM.memory[2];
assign word3 = M2.M2_SRAM.memory[3];
assign word4 = M2.M2_SRAM.memory[4];
assign word5 = M2.M2_SRAM.memory[5];
assign word6 = M2.M2_SRAM.memory[6];
assign word7 = M2.M2_SRAM.memory[7];
assign word8 = M2.M2_SRAM.memory[8];
assign word9 = M2.M2_SRAM.memory[9];
assign word10 = M2.M2_SRAM.memory[10];
assign word11 = M2.M2_SRAM.memory[11];
assign word12 = M2.M2_SRAM.memory[12];
assign word13 = M2.M2_SRAM.memory[13];
assign word14 = M2.M2_SRAM.memory[14];
```

```
assign word128 = M2.M2_SRAM.memory[128];
assign word129 = M2.M2_SRAM.memory[129];
assign word130 = M2.M2_SRAM.memory[130];
assign word131 = M2.M2_SRAM.memory[131];
assign word132 = M2.M2_SRAM.memory[132];
assign word133 = M2.M2_SRAM.memory[133];
assign word134 = M2.M2_SRAM.memory[134];
assign word135 = M2.M2_SRAM.memory[135];
assign word136 = M2.M2_SRAM.memory[136];
assign word137 = M2.M2_SRAM.memory[137];
assign word138 = M2.M2_SRAM.memory[138];
assign word139 = M2.M2_SRAM.memory[139];
assign word140 = M2.M2_SRAM.memory[140];

assign word255 = M2.M2_SRAM.memory[255];

initial #2800 $finish;
```

//Flush Memory

initial begin: Flush_Memory

```
#2 rst = 0; for (k=0; k<=255; k=k+1)M2.M2_SRAM.memory[k] = 0; #10 rst =  
1;  
end
```

initial begin: Load_program

#5

M2.M2_SRAM.memory[0] = 8'b0000_00_00;	// opcode_src_dest	
M2.M2_SRAM.memory[1] = 8'b0101_00_10;		// NOP
M2.M2_SRAM.memory[2] = 130;		// Read 130 to R2
M2.M2_SRAM.memory[3] = 8'b0101_00_11;		// Read 131 to R3
M2.M2_SRAM.memory[4] = 131;		
M2.M2_SRAM.memory[5] = 8'b0101_00_01;		// Read 128 to R1
M2.M2_SRAM.memory[6] = 128;		
M2.M2_SRAM.memory[7] = 8'b0101_00_00;		// Read 129 to R0
M2.M2_SRAM.memory[8] = 129;		
M2.M2_SRAM.memory[9] = 8'b0010_00_01;		// Sub R1-R0 to R1


```

M2.M2_SRAM.memory[10] = 8'b1000_00_00;           // BRZ
M2.M2_SRAM.memory[11] = 134;                     // Holds address for BRZ
M2.M2_SRAM.memory[12] = 8'b0001_10_11;           // Add R2+R3 to R3
M2.M2_SRAM.memory[13] = 8'b0111_00_11;           // BR
M2.M2_SRAM.memory[14] = 140;


// Load data
M2.M2_SRAM.memory[128] = 6;
M2.M2_SRAM.memory[129] = 1;
M2.M2_SRAM.memory[130] = 2;
M2.M2_SRAM.memory[131] = 0;
M2.M2_SRAM.memory[134] = 139;
//M2.M2_SRAM.memory[135] = 0;
M2.M2_SRAM.memory[139] = 8'b1111_00_00;         // HALT
M2.M2_SRAM.memory[140] = 9;                      // Recycle

end
endmodule

```

 


Design Example: UART

 


- Exchange text data in an ASCII format
- Encode each alphabetical character by 7 bits
- Augmented by a parity bit for error detection.
- 10-Bit Data Transmission Format
- *start-bit* in the LSB
- 8-bit data/parity word
- *stop-bit* in the MSB,

- Transmit the first 9 data bits in sequence, beginning with the start-bit
- Assert each bit being asserted at the serial line for one cycle of the modem clock
- Assert the stop-bit for one or more cycles of the clock

Data Format:

 


UART: Architecture

 

UART: Transmitter

Transmitter interface signals:

 


Input Signals:

<i>Byte_ready</i>	Asserted by host machine to indicate that <i>Data_Bus</i> has valid data
<i>Load_XMT_datareg</i>	Assertion transfers <i>Data_Bus</i> to the transmitter data storage register, <i>XMT_datareg</i>
<i>T_byte</i>	Assertion initiates transmission of a byte of data, including the stop, start, and parity bits
<i>bit_count</i>	Counts bits in the word during transmission
<i>state</i>	State of the transmitter controller state machine


Output Signals

<i>Load_XMT_shfreg</i>	Assertion loads the contents of <i>XMT_data_reg</i> into <i>XMT_shfreg</i>
<i>start</i>	Signals the start of transmission
<i>shift</i>	Directs <i>XMT_shfreg</i> to shift by one bit towards the LSB and to backfill with a stop bit (1).
<i>clear</i>	Clears <i>bit_count</i>
<i>next_state</i>	The next state of the state machine controlling the data path of the transmitter

ASM Chart:

 

 Note: Only the branch corresponding to a true decision is annotated at a decision diamond; signals that are not shown explicitly asserted are de-asserted. Conditional assertions are indicated by the name of the asserted signal



```
module UART_Transmitter_Arch
  (Serial_out, Data_Bus, Byte_ready, Load_XMT_datareg, T_byte, Clock,
  reset_);
  parameter word_size = 8;                      // Size of data word, e.g., 8 bits
  parameter one_hot_count = 3;                   // Number of one-hot states
  parameter state_count = one_hot_count;         // Number of bits in state
  parameter size_bit_count = 3;                  // Size of the bit counter, e.g., 4
                                                // Must count to word_size + 1
  parameter idle = 3'b001;                       // one-hot state encoding
  parameter waiting = 3'b010;
  parameter sending = 3'b100;
  parameter all_ones = 9'b1_1111_1111;           // Word + 1 extra bit

  output Serial_out;
  input [word_size - 1 : 0] Data_Bus;
  input Byte_ready;
  input Load_XMT_datareg;
  input T_byte;
```

// Serial output to data channel
// Host data bus containing
// data word
// Used by host to signal ready
// Used by host to load the
// data register
// Used by host to signal start
// of transmission

```
input          Clock;           // Bit clock of the transmitter
input          reset_;;         // Resets internal registers,
                                // loads the XMT_shftreg with
                                // ones

reg [word_size -1: 0]      XMT_datareg;    // Transmit Data Register
reg [word_size: 0]          XMT_shftreg;   // Transmit Shift Register:
                                              // {data, start bit}
reg                  Load_XMT_shftreg; // Flag to load the XMT_shftreg
reg [state_count -1: 0]    state, next_state; // State machine controller
reg [size_bit_count: 0]    bit_count;       // Counts the bits that
                                              // are transmitted
reg          clear;          // Clears bit_count after last bit is sent
reg          shift;          // Causes shift of data in XMT_shftreg
reg          start;          // Signals start of transmission


assign Serial_out = XMT_shftreg[0];        // LSB of shift register
```


```
always @ (state or Byte_ready or bit_count or T_byte)
begin: Output_and_next_state
    Load_XMT_shftreg = 0;
    clear = 0;
    shift = 0;
    start = 0;
    next_state = state;
    case (state)
        idle:      if (Byte_ready == 1) begin
                    Load_XMT_shftreg = 1;
                    next_state = waiting;
                end
        waiting:   if (T_byte == 1)  begin
                    start = 1;
                    next_state = sending;
                end
```


```
sending: if (bit_count != word_size + 1)
        shift = 1;
    else begin
        clear = 1;
        next_state = idle;
    end


    default: next_state = idle;
endcase
end
```

```
always @ (posedge Clock or negedge reset_) begin: State_Transitions
  if (reset_ == 0) state <= idle; else state <= next_state; end
always @ (posedge Clock or negedge reset_) begin: Register_Transfers
  if (reset_ == 0) begin
    XMT_shftreg <= all_ones; bit_count <= 0;
  end
  else begin
    if (Load_XMT_datareg == 1)
      XMT_datareg <= Data_Bus;                                // Get the data bus
    if (Load_XMT_shftreg == 1)
      XMT_shftreg <= {XMT_datareg,1'b1};                      // Load shift reg,
                                                               // insert stop bit
    if (start == 1)
      XMT_shftreg[0] <= 0;                                    // Signal start of transmission
    if (clear == 1) bit_count <= 0;
    else if (shift == 1) bit_count <= bit_count + 1;
    if (shift == 1)
      XMT_shftreg <= {1'b1, XMT_shftreg[word_size:1]}; // Shift right, fill
with 1's
  end
end
endmodule
```

 


 

 

 

UART: Receiver

 

UART: Receiver (cont.)

Receiver action:

- Receives the serial bit-stream of data
- Removes the start-bit
- Transfer data in a parallel format to a storage register connected to the host data bus.


Clock Regeneration:

- Data arrives at a standard bit rate
- Data is not necessarily synchronized with the internal clock at the host of the receiver
- Transmitter's clock is not available to the receiver
- Generate a *local* clock at a higher frequency, and using it to sample the received data in a manner that preserves the integrity of the data.
- *Sample_clock* is generated at the receiver's host.
- Count the cycles of *Sample_clock* to ensure that the data is sampled in the middle of a bit time,


Sampling algorithm:

- (1) Verify that a start bit has been received
- (2) Generate samples from 8 bits of the data (including parity bit)
- (3) Load the data onto the local bus

UART Receiver Sampling Format:

 

Controller:

 


Inputs:

<i>read_not_ready_in</i>	Signals that the host is not ready to receive data
<i>Serial_in</i>	Serial bit stream received by the unit
<i>reset_</i>	Active low reset
<i>Sample_counter</i>	Counts the samples of a bit
<i>Bit_counter</i>	Counts the bits that have been sampled
<i>state</i>	The state of the state machine controlling the data path of the receiver

Outputs:

<i>clr_Sample_counter</i>	Clears <i>Sample_counter</i>
<i>clr_Bit_counter</i>	Clears <i>Bit_counter</i>
<i>shift</i>	Causes <i>RCV_shftreg</i> to shift towards the LSB
<i>load</i>	Causes <i>RCV_shftreg</i> to transfer data to <i>RCV_datareg</i>
<i>Error1</i>	Asserted if host is not ready to receive data after last bit has been sampled
<i>Error2</i>	Asserts if the stop bit is missing
<i>next_state</i>	The next state of the state machine controlling the data path of the receiver

ASM chart:

 

UART: Receiver Verilog Model

```
module UART8_Receiver
  (RCV_datareg, read_not_ready_out, Error1, Error2, Serial_in,
   read_not_ready_in, Sample_clk, reset_);
  // Sample_clk is 8x Bit_clk

  parameter word_size      = 8;
  parameter half_word      = word_size / 2;
  parameter Num_counter_bits = 4;    // Must hold count of word_size
  parameter Num_state_bits  = 2;    // Number of bits in state
  parameter idle           = 2'b00;
  parameter starting        = 2'b01;
  parameter receiving       = 2'b10;

  output [word_size-1: 0] RCV_datareg;
  output read_not_ready_out, Error1, Error2;
  input  Serial_in,
         Sample_clk, reset_,
         read_not_ready_in;
```

```
reg RCV_datareg;
reg [word_size-1: 0] RCV_shftreg;
reg [Num_counter_bits -1: 0] Sample_counter;
reg [Num_counter_bits: 0] Bit_counter;
reg [Num_state_bits -1: 0] state, next_state;
reg inc_Bit_counter,
    clr_Bit_counter;
reg inc_Sample_counter,
    clr_Sample_counter;
reg shift, load, read_not_ready_out;
reg Error1, Error2;
```

```
//Combinational logic for next state and conditional outputs

always @(state or Serial_in or read_not_ready_in or Sample_counter
or Bit_counter) begin
    read_not_ready_out = 0;
    clr_Sample_counter = 0;
    clr_Bit_counter = 0;
    inc_Sample_counter = 0;
    inc_Bit_counter = 0;
    shift = 0;
    Error1 = 0;
    Error2 = 0;
    load = 0;
    next_state = state;
```

```
case (state)
    idle:      if (Serial_in == 0) next_state = starting;


    starting:   if (Serial_in == 1) begin
        next_state = idle;
        clr_Sample_counter = 1;
    end else


        if (Sample_counter == half_word -1) begin
            next_state = receiving;
            clr_Sample_counter = 1;
        end else inc_Sample_counter = 1;
```

```
receiving: if (Sample_counter < word_size-1) inc_Sample_counter = 1;  
          else begin  
            clr_Sample_counter = 1;  
            if (Bit_counter != word_size) begin  
              shift = 1;  
              inc_Bit_counter = 1;  
            end  
            else begin  
              next_state = idle;  
              read_not_ready_out = 1;  
              clr_Bit_counter = 1;  
              if (read_not_ready_in == 1) Error1 = 1;  
              else if (Serial_in == 0) Error2 = 1;  
              else load = 1;  
            end  
          end  
          default: next_state = idle;  
  
endcase  
end
```

```
// state_transitions_and_register_transfers

always @ (posedge Sample_clk) begin
    if (reset_ == 0) begin // synchronous reset_
        state <= idle;
        Sample_counter <= 0;
        Bit_counter <= 0;
        RCV_datareg <= 0;
        RCV_shftreg <= 0;
    end
    else begin
        state <= next_state;
        if (clr_Sample_counter == 1) Sample_counter <= 0;
        else if (inc_Sample_counter == 1)
            Sample_counter <= Sample_counter + 1;
        if (clr_Bit_counter == 1) Bit_counter <= 0;
        else if (inc_Bit_counter == 1) Bit_counter <= Bit_counter + 1;
        if (shift == 1) RCV_shftreg <= {Serial_in, RCV_shftreg[word_size-1:1]};
        if (load == 1) RCV_datareg <= RCV_shftreg;
    end
end
endmodule
```

 

 

UART Receiver: Partitioned Model

```
module UART8_rcvr_partition  (RCV_datareg, read_not_ready_out,  
    Error1, Error2, Serial_in,  
    read_not_ready_in, Sample_clk, reset_);  
  
    // partitioned UART receiver          // Sample_clk is 8x Bit_clk  
  
    parameter word_size      = 8;  
    parameter half_word      = word_size / 2;  
    parameter Num_counter_bits = 4; // Must hold count of word_size  
    parameter Num_state_bits   = 2; // Number of bits in state  
    parameter idle           = 2'b00;  
    parameter starting        = 2'b01;  
    parameter receiving       = 2'b10;
```

```
output [word_size -1: 0] RCV_datareg;
output  
Error1,  
Error2; // Handshake to host processor  
  
input Serial_in, // Serial data input  
Sample_clk, // Clock to sample serial data  
reset_, // Active-low reset  
read_not_ready_in; // Status bit from host processor  
  
wire [Num_counter_bits -1: 0] Sample_counter;  
wire [Num_counter_bits: 0] Bit_counter;  
wire [Num_state_bits -1: 0] state, next_state;
```

controller_part M2

(next_state, shift, load, read_not_ready_out, Error1, Error2,
inc_Sample_counter, inc_Bit_counter, clr_Bit_counter,
clr_Sample_counter, state, Sample_counter, Bit_counter,
Serial_in, read_not_ready_in);

state_transition_part M1

(RCV_datareg, Sample_counter, Bit_counter, state, next_state,
clr_Sample_counter,
inc_Sample_counter, clr_Bit_counter, inc_Bit_counter, shift, load,
Serial_in, Sample_clk, reset_);

endmodule

```
module controller_part (next_state, shift, load, read_not_ready_out,
Error1, Error2, inc_Sample_counter,
inc_Bit_counter, clr_Bit_counter, clr_Sample_counter, state,
Sample_counter, Bit_counter,
Serial_in, read_not_ready_in);

parameter word_size = 8;
parameter half_word = word_size / 2;
parameter Num_counter_bits = 4; // Must hold count of word_size
parameter Num_state_bits = 2; // Number of bits in state
parameter idle = 2'b00;
parameter starting = 2'b01;
parameter receiving = 2'b10;

output [Num_state_bits -1: 0] next_state;
output shift, load, inc_Sample_counter;
output inc_Bit_counter, clr_Bit_counter,
clr_Sample_counter;
output read_not_ready_out, Error1, Error2;

output state;
output Sample_counter;

input [Num_state_bits -1: 0]
input [Num_counter_bits -1: 0]
```

```
input [Num_counter_bits: 0] Bit_counter;
input Serial_in, read_not_ready_in;

reg next_state;
reg inc_Sample_counter, inc_Bit_counter, clr_Bit_counter,
clr_Sample_counter;
reg shift, load,  read_not_ready_out, Error1, Error2;

always @ (state or Serial_in or read_not_ready_in or Sample_counter or
Bit_counter) begin
    read_not_ready_out = 0;      //Combinational logic for next state and
conditional outputs
    clr_Sample_counter = 0;
    clr_Bit_counter = 0;
    inc_Sample_counter = 0;
    inc_Bit_counter = 0;
    shift = 0;
    Error1 = 0;
    Error2 = 0;
    load = 0;
    next_state = state;
```

```
case (state)
    idle:      if (Serial_in == 0) next_state = starting;

    starting:   if (Serial_in == 1) begin
        next_state = idle;
        clr_Sample_counter = 1;
    end else

        if (Sample_counter == half_word -1) begin
            next_state = receiving;
            clr_Sample_counter = 1;
        end else inc_Sample_counter = 1;
```

```
receiving:if (Sample_counter < word_size-1) inc_Sample_counter = 1;  
  else begin  
    clr_Sample_counter = 1;  
    if (Bit_counter != word_size) begin  
      shift = 1;  
      inc_Bit_counter = 1;  
    end  
    else begin  
      next_state = idle;  
      read_not_ready_out = 1;  
      clr_Bit_counter = 1;  
      if (read_not_ready_in == 1) Error1 = 1;  
      else if (Serial_in == 0) Error2 = 1;  
      else load = 1;  
    end  
  end  
  default: next_state = idle;  
endcase  
end  
endmodule
```

```
module state_transition_part (RCV_datareg, Sample_counter, Bit_counter,
state, next_state, clr_Sample_counter, inc_Sample_counter, clr_Bit_counter,
inc_Bit_counter, shift, load, Serial_in, Sample_clk, reset_);

parameter word_size = 8;
parameter half_word = word_size / 2;
parameter Num_counter_bits = 4; // Must hold count of word_size
parameter Num_state_bits = 2; // Number of bits in state
parameter idle = 2'b00;
parameter starting = 2'b01;
parameter receiving = 2'b10;

output [word_size -1: 0] RCV_datareg;
output [Num_counter_bits -1: 0] Sample_counter;
output [Num_counter_bits: 0] Bit_counter;
output [Num_state_bits -1: 0] state;

input [Num_state_bits -1: 0] next_state;
input Serial_in;
input inc_Sample_counter, inc_Bit_counter;
input clr_Bit_counter, clr_Sample_counter,
shift, load;
input Sample_clk, reset_;
```

```
reg                                Sample_counter, Bit_counter;
reg [word_size-1: 0]                  RCV_shftreg, RCV_datareg;
reg                                state;

// state_transitions_and_datapath_register_transfers

always @ (posedge Sample_clk) begin
    if (reset_ == 0) begin                      // synchronous reset_
        state <= idle;
        Sample_counter <= 0;
        Bit_counter <= 0;
        RCV_datareg <= 0;
        RCV_shftreg <= 0;
    end
    else begin
        state <= next_state;

        if (clr_Sample_counter == 1) Sample_counter <= 0;
        else if (inc_Sample_counter == 1) Sample_counter <= Sample_counter
+ 1;
```

```
if (clr_Bit_counter == 1) Bit_counter <= 0;
else if (inc_Bit_counter == 1) Bit_counter <= Bit_counter + 1;
if (shift == 1) RCV_shftreg <= {Serial_in, RCV_shftreg[word_size-1: 1]};
if (load == 1) RCV_datareg <= RCV_shftreg;
end
end
endmodule
```

