

**LINEAR CIRCUIT ANALYSIS** |  
**(EED) – U.E.T. TAXILA** |  
**ENGR. M. MANSOOR ASHRAF**

**09**

## **INTRODUCTION**

Thus far our analysis has been restricted for the most part to dc circuits: those circuits excited by constant or time-invariant sources.

We now begin the analysis of circuits in which the source voltage or current is time-varying.


A sinusoid is a signal that has the form of the sine or cosine function.

A sinusoidal current is usually referred to as alternating current (ac).
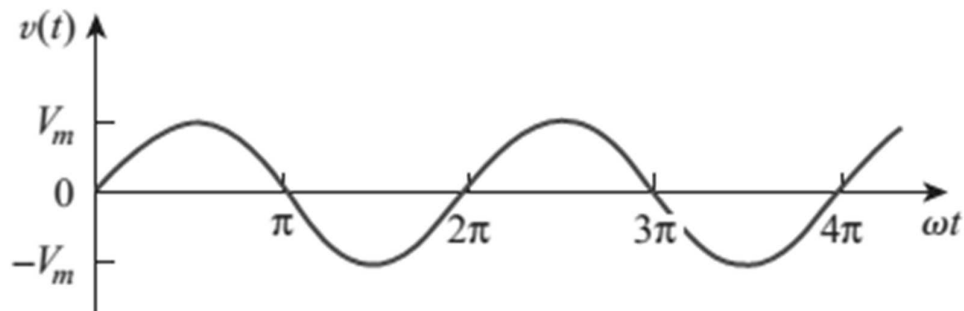
# SINUSOIDS

Consider the sinusoidal voltage;  $v(t) = V_m \sin \omega t$


Where  $V_m =$  the *amplitude* of the sinusoid  
 $\omega =$  the *angular frequency* in radians/s  
 $\omega t =$  the *argument* of the sinusoid



It is evident that sinusoid repeats itself every  $T$  seconds; where  $T$  is called period of sinusoid.
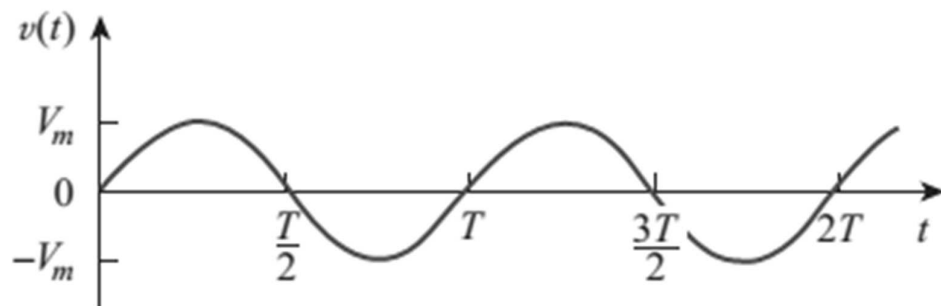
# SINUSOIDS

Time period of sinusoid;  $T = \frac{2\pi}{\omega}$



A Periodic Function is one that satisfies  $f(t) = f(t + nT)$ , for all  $t$  and for all integers  $n$ .

For sinusoid;  $v(t + T) = v(t)$

Period of periodic function is time for complete cycle.

# SINUSOIDS

The reciprocal of time period is number of cycles per second, known as the Cyclic Frequency, measured in hertz (Hz).

$$f = \frac{1}{T} \quad \omega = 2\pi f$$


Consider general sinusoid;

$$v(t) = V_m \sin(\omega t + \phi)$$

Lets examine two sinusoid;

$$v_1(t) = V_m \sin \omega t \quad v_2(t) = V_m \sin(\omega t + \phi)$$

# SINUSOIDS

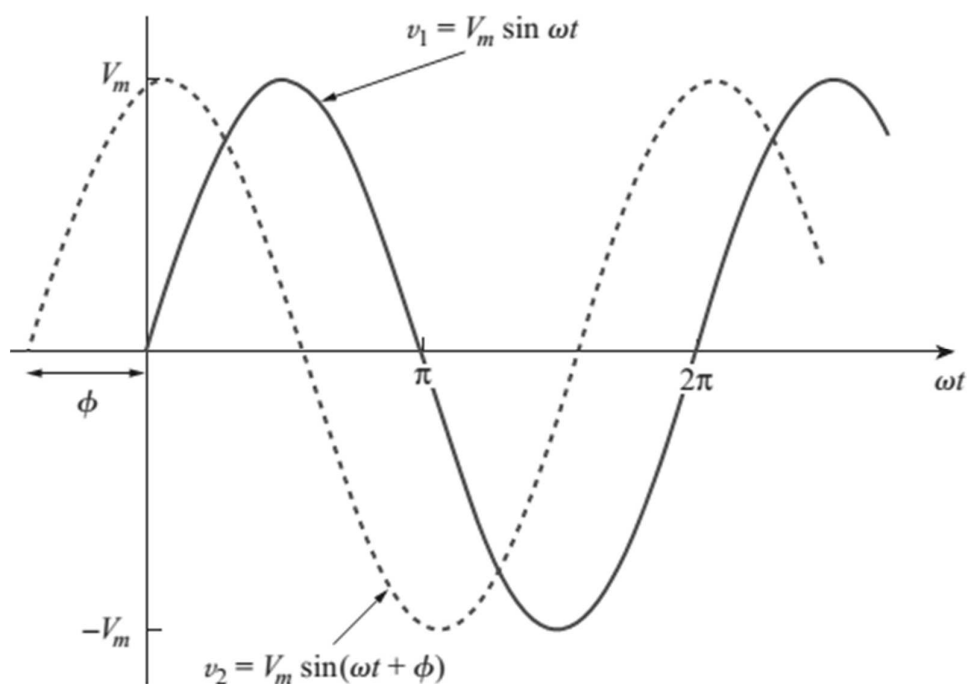

## SINUSOIDS

The sinusoid can be expressed in either sine or cosine form.

Following trigonometric identities may be used;

$$\sin(A \pm B) = \sin A \cos B \pm \cos A \sin B$$

$$\cos(A \pm B) = \cos A \cos B \mp \sin A \sin B$$

To interchange sine and cosine functions;

$$\sin(\omega t \pm 180^\circ) = -\sin \omega t$$

$$\cos(\omega t \pm 180^\circ) = -\cos \omega t$$

$$\sin(\omega t \pm 90^\circ) = \pm \cos \omega t$$

$$\cos(\omega t \pm 90^\circ) = \mp \sin \omega t$$

## PROBLEMS

Find amplitude, phase, period and frequency of sinusoid:

$$v(t) = 12 \cos(50t + 10^\circ)$$

(12 V,  $10^\circ$ , 50 rad/s, 0.1257 s, 7.958 Hz)

Calculate the phase angle between two sinusoids and state which sinusoid is leading?

$$v_1 = -10 \cos(\omega t + 50^\circ)$$

$$v_2 = 12 \sin(\omega t - 10^\circ) \quad (30^\circ, v_2)$$

# PHASORS

A Phasor is a complex number that represents the amplitude and phase of a sinusoid.

A complex number can be represented in three forms as;

$$z = x + jy \quad \text{Rectangular form}$$

$$z = r \angle \phi \quad \text{Polar form}$$

$$z = re^{j\phi} \quad \text{Exponential form}$$

The relationship between the rectangular form and the polar form is;

$$r = \sqrt{x^2 + y^2}, \quad \phi = \tan^{-1} \frac{y}{x}$$


$$x = r \cos \phi, \quad y = r \sin \phi$$

# PHASORS

The complex may be written and interpreted as;

$$z = x + jy = r \angle \phi = r(\cos \phi + j \sin \phi)$$

Imaginary axis

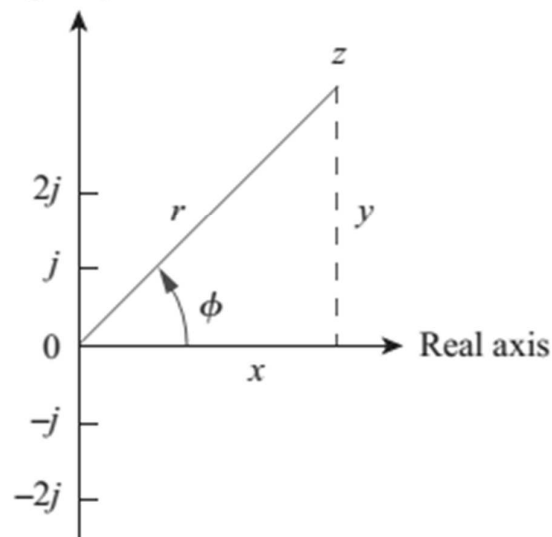

## PHASORS

Addition and subtraction of complex numbers are better performed in rectangular form while multiplication and division in polar form.

$$z = x + jy = r \angle \phi, \quad z_1 = x_1 + jy_1 = r_1 \angle \phi_1$$

$$z_2 = x_2 + jy_2 = r_2 \angle \phi_2$$

Addition;  $z_1 + z_2 = (x_1 + x_2) + j(y_1 + y_2)$

Subtraction;  $z_1 - z_2 = (x_1 - x_2) + j(y_1 - y_2)$

Multiplication;  $z_1 z_2 = r_1 r_2 \angle \phi_1 + \phi_2$

Division;  $\frac{z_1}{z_2} = \frac{r_1}{r_2} \angle \phi_1 - \phi_2$

## PHASORS

Reciprocal;

$$\frac{1}{z} = \frac{1}{r} \angle -\phi$$

Square Root;  $\sqrt{z} = \sqrt{r} \angle \phi/2$

Complex Conjugate;

$$z^* = x - jy = r \angle -\phi = r e^{-j\phi}$$

In complex numbers;

$$\frac{1}{j} = -j$$

# PHASORS

The idea of phasor representation is based on Euler's identity.

$$e^{\pm j\phi} = \cos\phi \pm j \sin\phi$$

where;

$$\cos\phi = \text{Re}(e^{j\phi})$$

$$\sin\phi = \text{Im}(e^{j\phi})$$

Given a sinusoid;  $v(t) = V_m \cos(\omega t + \phi)$

$$v(t) = V_m \cos(\omega t + \phi) = \text{Re}(V_m e^{j(\omega t + \phi)})$$

$$v(t) = \text{Re}(V_m e^{j\phi} e^{j\omega t})$$

$$v(t) = \text{Re}(\mathbf{V} e^{j\omega t})$$


where;

$$\mathbf{V} = V_m e^{j\phi} = V_m \angle \phi$$
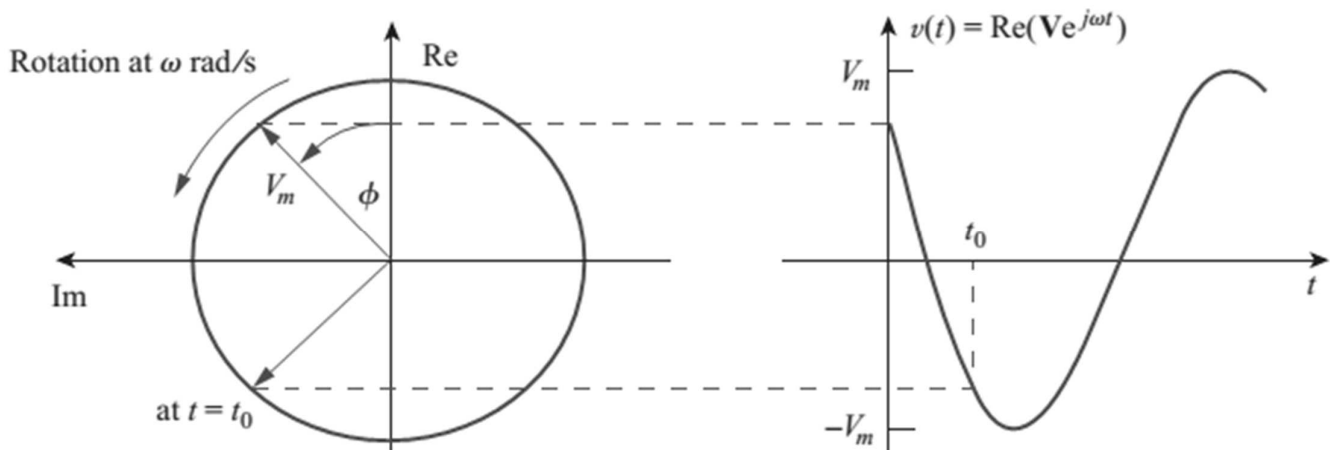
# PHASORS

' $\mathbf{V}$ ' is the phasor representation of the sinusoid  $v(t)$ .

The phasor rotates in complex plane to plot sine wave in time domain using its projection.



# PHASORS

The transformation is summarized as;

$$\begin{array}{ccc} v(t) = V_m \cos(\omega t + \phi) & \Leftrightarrow & \mathbf{V} = V_m \underline{\angle \phi} \\ \text{(Time-domain} & & \text{(Phasor-domain} \\ \text{representation)} & & \text{representation)} \end{array}$$

Time domain and phasor domain representation can be interchanged as;

<u>Time domain representation</u>	<u>Phasor domain representation</u>
$V_m \cos(\omega t + \phi)$	$V_m \underline{\angle \phi}$
$V_m \sin(\omega t + \phi)$	$V_m \underline{\angle \phi - 90^\circ}$
$I_m \cos(\omega t + \theta)$	$I_m \underline{\angle \theta}$
$I_m \sin(\omega t + \theta)$	$I_m \underline{\angle \theta - 90^\circ}$

# PHASORS

Time domain is also known as Instantaneous domain and phasor domain is also known as Frequency domain.

Consider sinusoid;

$$v(t) = \text{Re}(\mathbf{V}e^{j\omega t}) = V_m \cos(\omega t + \phi)$$

Differentiating;

$$\frac{dv}{dt} = -\omega V_m \sin(\omega t + \phi) = \omega V_m \cos(\omega t + \phi + 90^\circ)$$

$$= \text{Re}(\omega V_m e^{j\omega t} e^{j\phi} e^{j90^\circ}) = \text{Re}(j\omega \mathbf{V}e^{j\omega t})$$

Transformation of derivative from time domain to phasor domain is;

$$\begin{array}{ccc} \frac{dv}{dt} & \Leftrightarrow & j\omega \mathbf{V} \\ \text{(Time domain)} & & \text{(Phasor domain)} \end{array}$$



# PHASORS

Transformation of integral from time domain to phasor domain is;

$$\int v dt \quad \Leftrightarrow \quad \frac{\mathbf{V}}{j\omega}$$

(Time domain)  (Phasor domain)

The  $v(t)$  is time dependent, while  $\mathbf{V}$  is not.

The  $v(t)$  is always real with no complex term, while  $\mathbf{V}$  is generally complex.

# PROBLEMS

Evaluate these complex numbers:

(a)  $(40\angle 50^\circ + 20\angle -30^\circ)^{1/2}$

(b)  $\frac{10\angle -30^\circ + (3 - j4)}{(2 + j4)(3 - j5)^*}$

Transform these sinusoids to phasors:

(a)  $i = 6 \cos(50t - 40^\circ)$  A

(b)  $v = -4 \sin(30t + 50^\circ)$  V

Find the sinusoids represented by these phasors:

(a)  $\mathbf{I} = -3 + j4$  A

(b)  $\mathbf{V} = j8e^{-j20^\circ}$  V

## PROBLEMS

Given  $i_1(t) = 4 \cos(\omega t + 30^\circ)$  A and  $i_2(t) = 5 \sin(\omega t - 20^\circ)$  A, find their sum.

$$i(t) = 3.218 \cos(\omega t - 56.97^\circ) \text{ A}$$

Using the phasor approach, determine the current  $i(t)$  in a circuit described by the integrodifferential equation

$$4i + 8 \int i dt - 3 \frac{di}{dt} = 50 \cos(2t + 75^\circ)$$

$$i(t) = 4.642 \cos(2t + 143.2^\circ) \text{ A}$$

## PHASOR RELATIONSHIPS FOR CIRCUIT ELEMENTS


If the current through the resistor R is  $i = I_m \cos(\omega t + \phi)$ , voltage across resistor is given by Ohm's law.

$$v = iR = RI_m \cos(\omega t + \phi)$$

Phasor form;

$$V = RI_m \angle \phi$$

$$\mathbf{V} = R\mathbf{I}$$

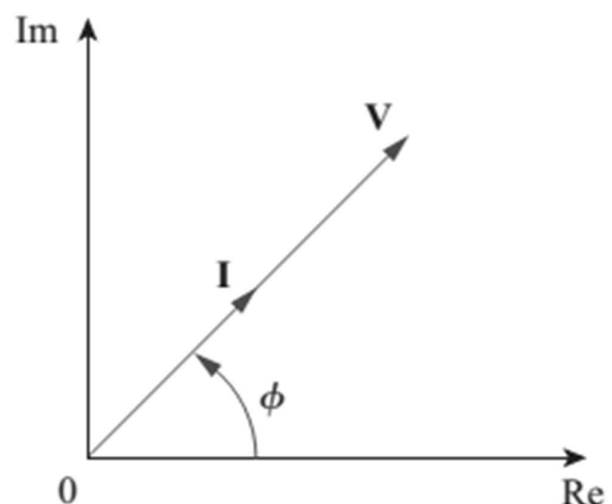

## PHASOR RELATIONSHIPS FOR CIRCUIT ELEMENTS


If the current through the inductor  $L$  is  $i = I_m \cos(\omega t + \phi)$ , voltage across inductor is given by;

$$v = L \frac{di}{dt} = -\omega L I_m \sin(\omega t + \phi) \quad v = \omega L I_m \cos(\omega t + \phi + 90^\circ)$$

$$V = \omega L I_m e^{j(\phi + 90^\circ)} = \omega L I_m e^{j\phi} e^{j90^\circ} = \omega L I_m \angle \phi + 90^\circ$$

$$e^{j90^\circ} = j.$$


$$V = j\omega L I$$

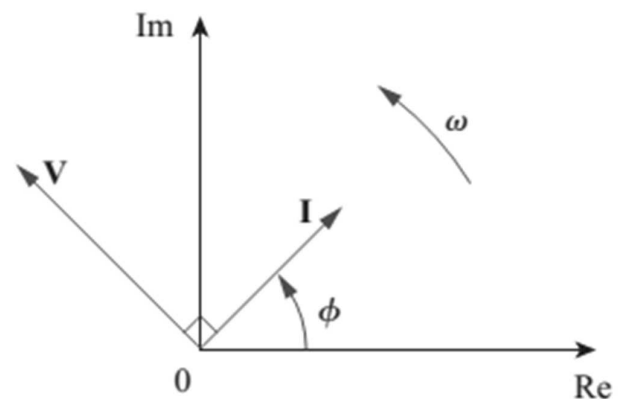
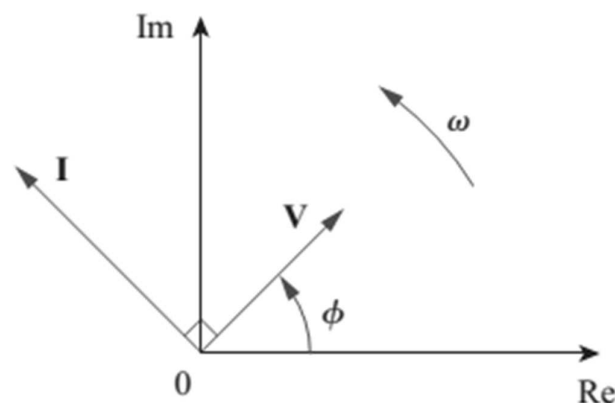
## PHASOR RELATIONSHIPS FOR CIRCUIT ELEMENTS

If the voltage across capacitor  $C$  is  $v = V_m \cos(\omega t + \phi)$ , current through capacitor is given by;

$$i = C \frac{dv}{dt} \quad I = j\omega C V \quad \Rightarrow \quad V = \frac{I}{j\omega C}$$



# PHASOR RELATIONSHIPS FOR CIRCUIT ELEMENTS

## Summary

Element	Time domain	Frequency domain
$R$	$v = Ri$	$\mathbf{V} = R\mathbf{I}$
$L$	$v = L\frac{di}{dt}$	$\mathbf{V} = j\omega L\mathbf{I}$
$C$	$i = C\frac{dv}{dt}$	$\mathbf{V} = \frac{\mathbf{I}}{j\omega C}$

## PROBLEMS

The voltage  $v = 12 \cos(60t + 45^\circ)$  is applied to a 0.1-H inductor. Find the steady-state current through the inductor.

$$i(t) = 2 \cos(60t - 45^\circ) \text{ A}$$

If voltage  $v = 10 \cos(100t + 30^\circ)$  is applied to a  $50 \mu\text{F}$  capacitor, calculate the current through the capacitor.

$$50 \cos(100t + 120^\circ) \text{ mA}$$

## IMPEDANCE AND ADMITTANCE

The voltage across resistor, inductor and capacitor are;

$$\begin{aligned} V &= RI, & V &= j\omega LI, & V &= \frac{I}{j\omega C} \\ \frac{V}{I} &= R, & \frac{V}{I} &= j\omega L, & \frac{V}{I} &= \frac{1}{j\omega C} \end{aligned}$$

$$\mathbf{Z} = \frac{\mathbf{V}}{\mathbf{I}} \quad \text{or} \quad \mathbf{V} = \mathbf{ZI}$$

Where  $Z$  is a frequency dependent quantity known as impedance, measured in ohms.

The Impedance of a circuit is the ratio of the phasor voltage to the phasor current, measured in Ohms.

## IMPEDANCE AND ADMITTANCE

The Admittance ( $Y$ ) is the reciprocal of impedance, measured in Siemens.

$$\mathbf{Y} = \frac{1}{\mathbf{Z}} = \frac{\mathbf{I}}{\mathbf{V}}$$

Impedances and admittances of passive elements.

<u>Element</u>	<u>Impedance</u>	<u>Admittance</u>
$R$	$\mathbf{Z} = R$	$\mathbf{Y} = \frac{1}{R}$
$L$	$\mathbf{Z} = j\omega L$	$\mathbf{Y} = \frac{1}{j\omega L}$
$C$	$\mathbf{Z} = \frac{1}{j\omega C}$	$\mathbf{Y} = j\omega C$

## IMPEDANCE AND ADMITTANCE

The impedance may be expressed in rectangular form;

$$\mathbf{Z} = R + jX$$

$R = \text{Re } \mathbf{Z}$  is the *resistance*       $X = \text{Im } \mathbf{Z}$  is the *reactance*

Reactance may be positive or negative depending on circuit element.

Inductive reactance for inductor;

$$\mathbf{Z} = R + jX$$

Capacitive reactance for capacitor;

$$\mathbf{Z} = R - jX$$

## IMPEDANCE AND ADMITTANCE

The impedance may be expressed in polar form;

$$\mathbf{Z} = |\mathbf{Z}| \angle \theta$$

$$\mathbf{Z} = R + jX = |\mathbf{Z}| \angle \theta$$

Relationship between rectangular and polar forms of impedance.

$$|\mathbf{Z}| = \sqrt{R^2 + X^2}, \quad \theta = \tan^{-1} \frac{X}{R}$$

$$R = |\mathbf{Z}| \cos \theta, \quad X = |\mathbf{Z}| \sin \theta$$

# IMPEDANCE AND ADMITTANCE

Admittance is reciprocal of impedance and is combination of Conductance and Susceptance as real and imaginary parts.


$$\mathbf{Y} = G + jB$$

$$G + jB = \frac{1}{R + jX}$$

$$G = \frac{R}{R^2 + X^2}, \quad B = -\frac{X}{R^2 + X^2}$$

# PROBLEMS

Find  $v(t)$  and  $i(t)$ ?

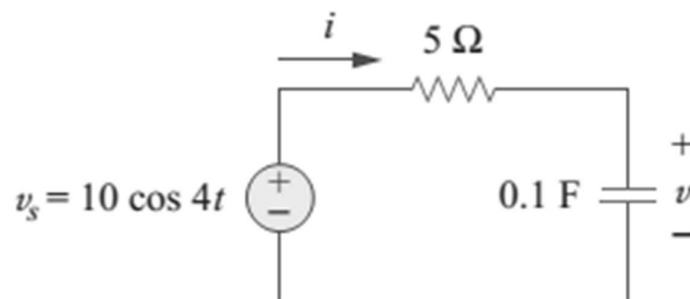

## KIRCHHOFF'S LAWS IN FREQUENCY DOMAIN

KVL holds in phasor domain as in time domain.

$$v_1 + v_2 + \cdots + v_n = 0$$

$$\mathbf{V}_1 + \mathbf{V}_2 + \cdots + \mathbf{V}_n = 0$$


KCL also holds in phasor domain as in time domain.

$$i_1 + i_2 + \cdots + i_n = 0$$

$$\mathbf{I}_1 + \mathbf{I}_2 + \cdots + \mathbf{I}_n = 0$$

## IMPEDANCE COMBINATIONS

Equivalent impedance in series circuit;

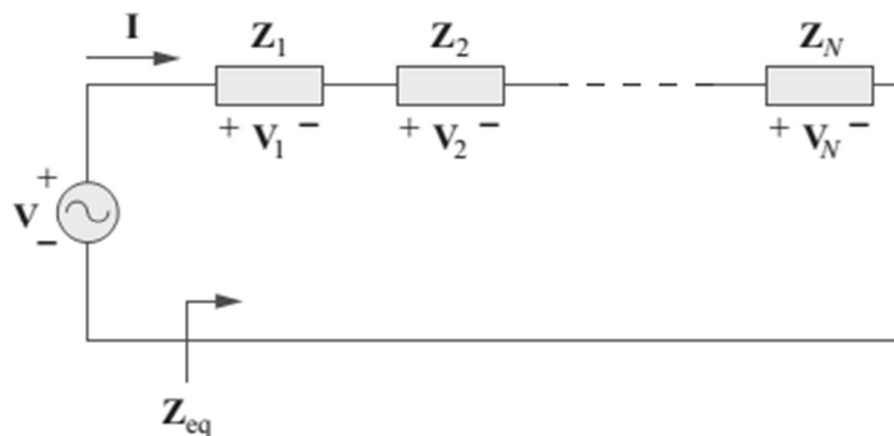


$$\mathbf{Z}_{eq} = \mathbf{Z}_1 + \mathbf{Z}_2 + \cdots + \mathbf{Z}_N$$


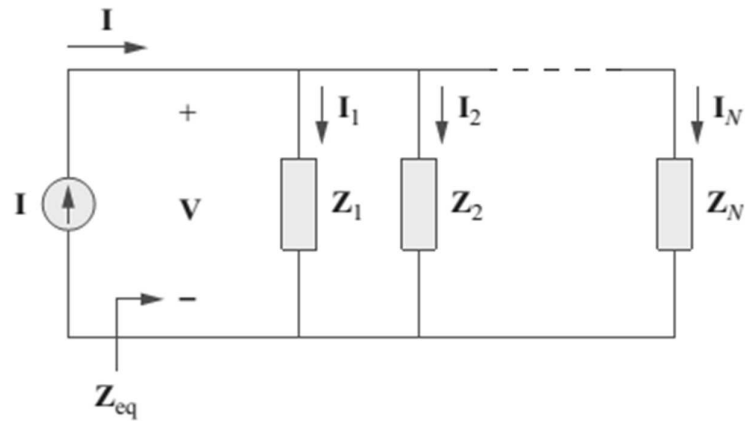
# IMPEDANCE COMBINATIONS

Equivalent impedance in parallel circuit;



$$\frac{1}{Z_{eq}} = \frac{I}{V} = \frac{1}{Z_1} + \frac{1}{Z_2} + \dots + \frac{1}{Z_N}$$

# IMPEDANCE COMBINATIONS


Voltage and current division rules are also equally applicable for series and parallel circuits;

$$V_1 = \frac{Z_1}{Z_1 + Z_2} V, \quad V_2 = \frac{Z_2}{Z_1 + Z_2} V$$

$$I_1 = \frac{Z_2}{Z_1 + Z_2} I, \quad I_2 = \frac{Z_1}{Z_1 + Z_2} I$$
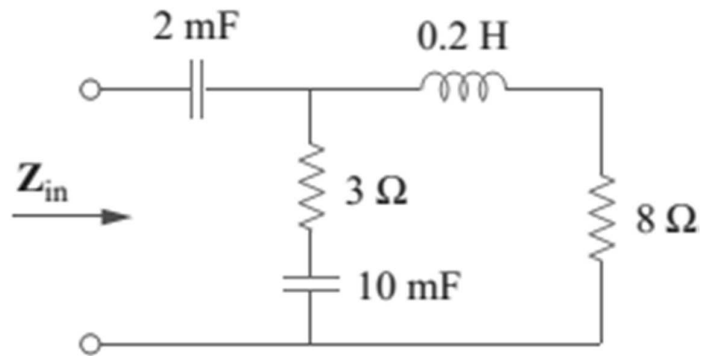
## PROBLEMS

Find equivalent impedance at  $\omega=50$  rad/s.



## REFERENCES

Fundamentals of Electric Circuits (4<sup>th</sup> Edition)

Charles K. Alexander, Matthew N. O. Sadiku

Chapter 09 – Sinusoids and Phasors (9.1 – 9.7)

Exercise Problems: 9.1 – 9.70

Do exercise problem yourself.