

Question ①

$$q_v = 10 \sin(4\pi t) \quad \text{mC}$$

$$v = 2 \cos(4\pi t) \quad \text{V}$$

①

$$p = v i$$

$$= v \cdot \frac{dq_v}{dt} = [2 \cos(4\pi t)] \cdot \frac{d}{dt} [10 \sin(4\pi t)]$$

$$= 2 \cos(4\pi t) \cdot 10 \cos(4\pi t) \cdot 4\pi$$

$$p = 80\pi \cos^2(4\pi t)$$

$$p \Big|_{0.5} = 80\pi \cos^2\left(\frac{4\pi}{2}\right)$$

$$p \Big|_{0.5} = 80\pi = 251.33 \text{ mW}$$

②

$$\text{Energy} = \int_0^{0.6} p \cdot dt$$

$$= \int_0^{0.6} 80\pi \cos^2(4\pi t) dt$$

$$= \int_0^{0.6} 40\pi [1 + \cos(8\pi t)] \cdot dt$$

$$= 40\pi \left[t + \frac{\sin(8\pi t)}{8\pi} \right]_0^{0.6}$$

$$= 40\pi \left[0.6 + \frac{1}{8\pi} \sin(8\pi \times 0.6) \right]$$

$$E = 78.34 \text{ mJ}$$

Question (2)

(A) Nodal Analysis

Node 2:
$$\frac{V_1 - V_2}{2} + 5 = \frac{V_2 - V_3}{2}$$

$$V_1 - V_2 + 10 = V_2 - V_3$$

$$V_1 - 2V_2 + V_3 = -10 \quad \text{--- (1)}$$

Super Node:

$$\frac{V_1}{4} + \frac{V_3}{8} + \frac{V_1 - V_2}{2} = \frac{V_2 - V_3}{2}$$

$$2V_1 + V_3 + 4V_1 - 4V_2 = 4V_2 - 4V_3$$

$$4V_1 + 2V_1 + 8V_2 + 5V_3 = 0$$

$$6V_1 + 8V_2 + 5V_3 = 0 \quad \text{--- (2)}$$

Mesh:


$$V_1 - V_3 = -10$$

$$V_1 - V_3 = -10 \quad \text{--- (3)}$$

| |
|----------------------|
| $V_1 = 10 \text{ V}$ |
| $V_2 = 20 \text{ V}$ |
| $V_3 = 20 \text{ V}$ |

Question ②

③ Mesh Analysis.

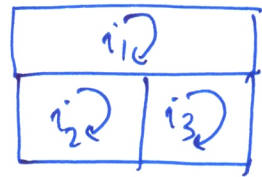

Mesh 1: $-10 + 4i_1 - 2i_2 - 2i_3 = 0$.

$$4i_1 - 2i_2 - 2i_3 = 10 \quad \text{--- (1)}$$

Super Mesh: $6i_2 + 10i_3 - 2i_1 - 2i_1 = 0$

$$-4i_1 + 6i_2 + 10i_3 = 0 \quad \text{--- (2)}$$

Node '0':

$$i_3 = i_2 + 5$$

$$i_2 - i_3 = -5 \quad \text{--- (3)}$$

$$i_1 = \frac{5}{2}, \quad i_2 = -\frac{5}{2}, \quad i_3 = \frac{5}{2}$$

$$V_1 = -4i_2$$

$$= -4\left(-\frac{5}{2}\right) \Rightarrow \boxed{V_1 = 10 \text{ V}}$$

$$V_2 = V_1 + 2(i_2 - i_1) = 10 + 2\left(-\frac{5}{2} - \frac{5}{2}\right)$$

$$= 10 + 10 = 20 \Rightarrow \boxed{V_2 = 20 \text{ V}}$$



$$V_3 = 8(i_3) = 8\left(\frac{5}{2}\right) \Rightarrow \boxed{V_3 = 20 \text{ V}}$$

Question ③

Source 1:

$$V_{o1} = \frac{3}{3+3} (40)$$

$$V_{o1} = 20 \text{ V}$$

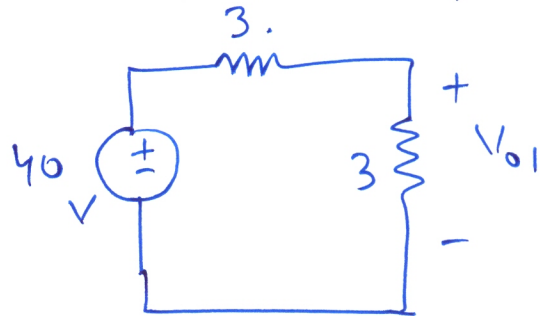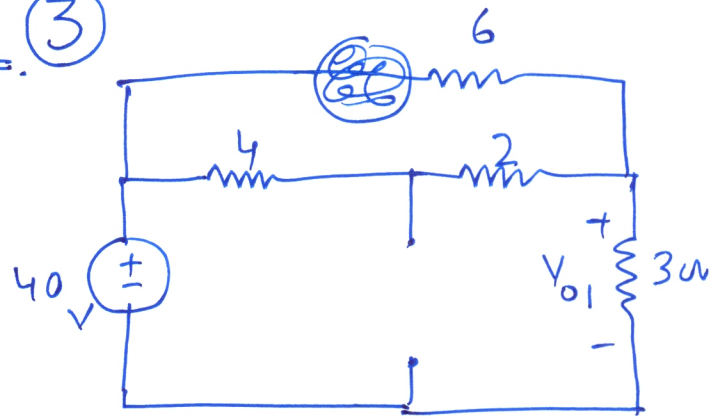

Source 2:

Nodal:-

Node 1:

$$\frac{V_1 - V_2}{2} + \frac{V_1}{4} = 2$$

$$2V_1 - 2V_2 + V_1 = 8$$

$$3V_1 - 2V_2 = 8 \quad \text{--- (1)}$$

Node 2:

$$\frac{V_1 - V_2}{2} = \frac{V_2}{3} + \frac{V_2}{6}$$


$$3V_1 - 3V_2 = 2V_2 + V_2$$

$$3V_1 - 6V_2 = 0 \quad \text{--- (2)}$$

Subtracting ① & ②; $4V_2 = 8$

$$V_2 = 2 \text{ V}$$



$$V_{o2} = 2 \text{ V}$$

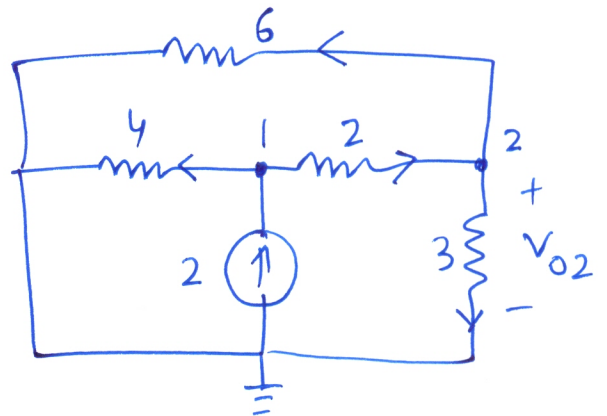

Source 3

$$V_{03} = -3 \left[\frac{3}{3+3} \times 4 \right]$$

$$V_{03} = -6 \text{ V}$$

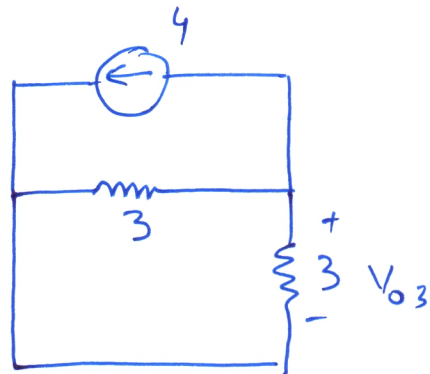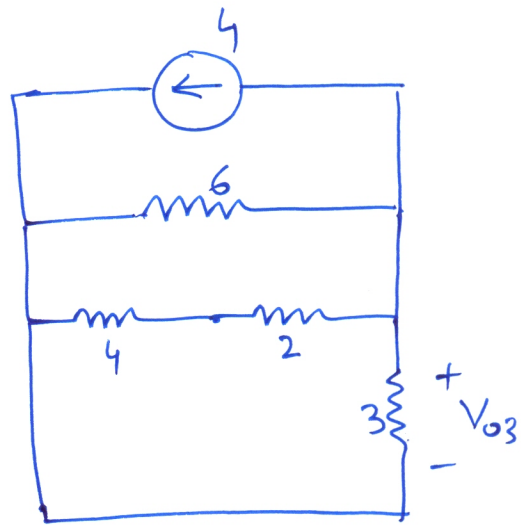

$$V_0 = V_{01} + V_{02} + V_{03}$$

$$V_0 = 20 + 2 - 6$$


$$V_0 = 16 \text{ V}$$

Question 4



(A) Thevenin Resistance: -



$$R_{th} = \frac{10 \times 5}{10 + 5}$$
$$= \frac{50}{15}$$

$$R_{th} = 10/3 \text{ } \Omega$$

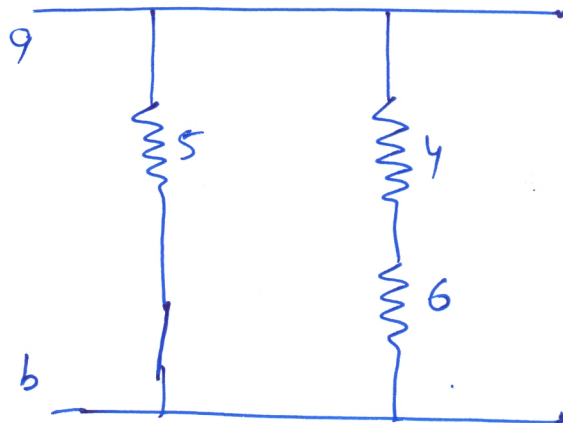


(B)

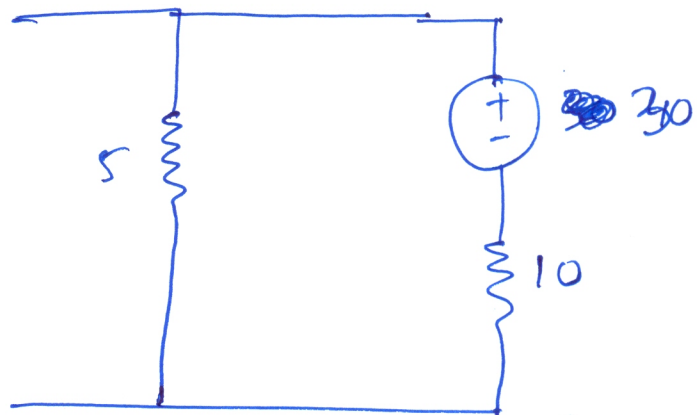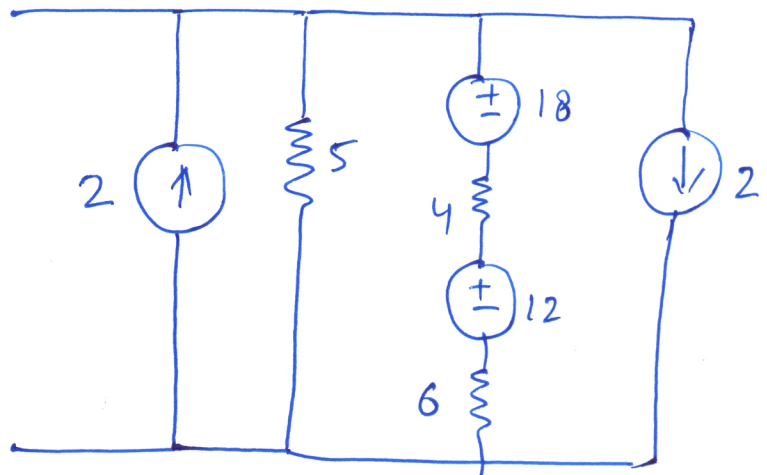


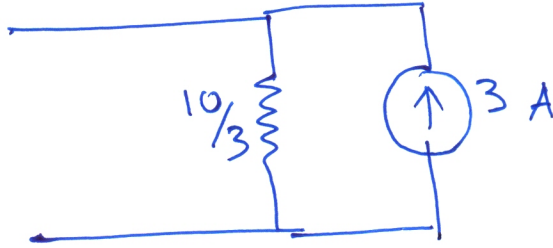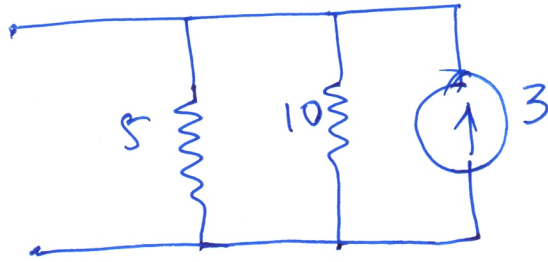


$$V_{th} = 10 \text{ V}$$

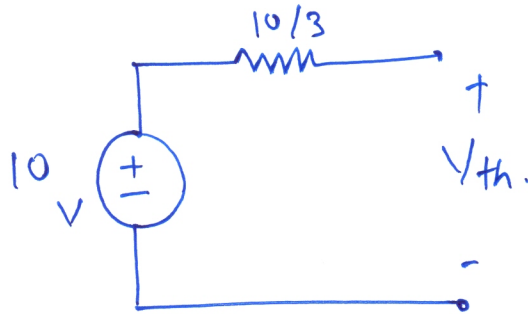

Thevenin's Equivalent:

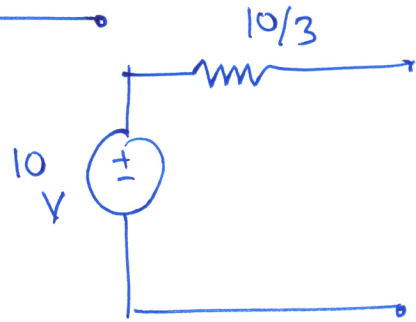

(C) Norton's Equivalent

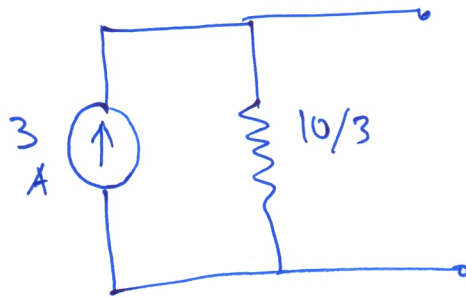

$$I_N = 3 \text{ A}$$

Question 5

$$-V_{out} = \frac{1}{4} (V_1 + V_2 + V_3 + V_4)$$

$$V_{out} = - \left[\frac{R_f}{R_1} V_1 + \frac{R_f}{R_2} V_2 + \frac{R_f}{R_3} V_3 + \frac{R_f}{R_4} V_4 \right]$$

$$-V_{out} = + \frac{R_f}{R_1} (V_1 + V_2 + V_3 + V_4). \quad \text{if } R_1 = R_2 = R_3 = R_4$$

& $R_f = 10 \text{ k}\Omega$.

$$\frac{R_f}{R_1} = \frac{1}{4}$$

$$\frac{10 \text{ k}}{R_1} = \frac{1}{4}$$

$$\Rightarrow \boxed{R_1 = 40 \text{ k}\Omega}$$

