

Lab Assignment # 1

Instructions

- Due Date for Assignment is **14-03-2013**.
- No assignment will be accepted after the due date.
- You must complete your work **individually** and you are not allowed to **take help from** your fellow student.

Task

Connect the circuit according to the given scheme on **breadboard** and run a toggle program on BAR LED.

